

EECS151 : Introduction to Digital Design and ICs


Lecture 15 – Logical Effort

Bora Nikolić

Samsung Foundry Promises Gate All-Around in '22

October 14, 2021, EETimes - Samsung Foundry recently held its Foundry Forum where it revealed some details of its semiconductor process roadmaps and fab expansion. Samsung is being most aggressive pursuing the next generation of transistor technology, with plans to reach mass production ahead of TSMC and Intel. Samsung's 3-nanometer process will use the gate-all-around (GAA) transistor structure, which the foundry calls MBCFET (Multi-bridge channel FET) and will be in production first half of 2022. TSMC will wait another generation until its N2 process to deliver GAA some time in 2023.

Samsung GAA transistor, MBCFET™

 

EETimes

Nikolić Fall 2021

Berkeley

Review

- Delay is a linear function of R and C
- Delay optimization is critical to improve the frequency of the circuit.
- The dimensions of a transistor affect its capacitance and resistance.
- We use RC delay model to describe the delay of a circuit.

EECS151 L15 LOGICAL EFFORT

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

Berkeley

Minimizing Logic Delay

How Do We Optimize the Delay?

 - How fast can a pipelined processor run?
- What is the fastest adder?



Nikolić Fall 2021


Berkeley

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

Berkeley

Inverter RC Delay

 

- $t_p = R_{eq}(C_p + C_L) = R_{eq}(C_{in}/\gamma + C_L)$
 - $\gamma = 1$ (closer to 1.2 in recent processes)
- $t_p = R_{eq}C_{in}(1 + C_L/C_{in}) = \tau_{INV}(1 + f)$
 - Propagation delay is proportional to fanout
- Normalized Delay = $1 + f$


$$\text{Fanout} = f = C_L/C_{in}$$

$$t_p = \tau_{INV}(1 + f)$$

Generalizing to Arbitrary Gates


- Delay has two components: $d = f + p$
- h : effort delay = gh (a.k.a. stage effort)
 - Again has two components
- g : logical effort
 - Measures relative ability of gate to deliver current
 - $g = 1$ for inverter
- f : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
- p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

Inverter Delay

 

- Parasitic p is the ratio of intrinsic capacitance to an inverter
 - $p(\text{inverter}) =$
- Logical Effort g is the ratio of input capacitance to an inverter
 - $g(\text{inverter}) =$
- Electrical Effort h is the ratio of the load capacitance to the input capacitance
 - $h(\text{inverter}) =$
- Delay = $p + h = p + g * f = 1 + f$

NAND2 Gate

 

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021


Berkeley

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

Berkeley

Logical Effort of NAND2 Gate

 


- In velocity-saturated devices I_{on} of a stack is $2/3$ (not a half) of two devices
 - So the correct upscaling factor is 1.5 (not 2)
- We will use 2, as it makes calculations easier

EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



NOR2 Gate

 


EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



Example: Inverter Chain

 


Logical Effort: $g =$
 Electrical Effort: $f =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$
 Total Delay: $d_{total} =$

EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



Optimize Delay of an Inverter Chain

 

Given C_{in}, C_L ($F = C_L / C_{in}$)

How to optimally size inverter chain to minimize delay?

...There are $N-1$ unknowns: C_2, C_3, \dots, C_N

$d = (1 + C_2 / C_{in}) + (1 + C_3 / C_2) + \dots + (C_L / C_N)$

Solution: All delays are equal, $C_2 / C_{in} = C_3 / C_2 = \dots = C_L / C_N$

$$\frac{C_{i+1}}{C_i} = \sqrt[N]{\frac{C_L}{C_{in}}}$$

$$C_i = \sqrt{C_{i+1} C_{i-1}}$$


EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$
 Electrical Effort: $f =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$


EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$
 Electrical Effort: $f = 4$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = 5$

Fanout-of-4 is commonly used to normalize the circuit delay across technologies

EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021




Multi-stage Logic Networks

- Logical effort generalizes to multistage networks

Path Logical Effort $G = \prod g_i$

Path Electrical Effort $F = \frac{C_{out-path}}{C_{in-path}}$

 Path Effort $H = \prod h_i = \prod g_i f_i$



EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



Branching Effect

$$b = \frac{C_{on path} + C_{off path}}{C_{on path}} \quad B = \prod b_i$$

$$G = 1$$

$$F = 90 / 5 = 18$$


$$GF = 18$$

$$f_1 = (15 + 15) / 5 = 6$$

$$f_2 = 90 / 15 = 6$$

$$B = 2$$

$$F = g_1 g_2 h_1 h_2 = 36 = BGH$$

 

EECS151 L15 LOGICAL EFFORT

Hkaidi Fall 2021



Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{h} = g_i f_i = H^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NH^{\frac{1}{N}} + P$$


- And we can find the gate sizes that result in optimal delay

Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

 


Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter


$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

 


Best Stage Effort

 - How many stages should a path use?
 - To drive given capacitance



 - Define best stage effort $\rho = F^{\frac{1}{N}}$
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = e = 2.718$
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$
- Choose 4 – less stages, less energy



Logical Efforts Method

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$


$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Example: Optimize Delay

 

$$g = 1, f = a$$

$$g = 3/2, f = b/a$$

$$g = 4/2, f = c/b$$

$$g = 1, f = 5/c$$

Effective fanout, $F =$

$G =$

$H =$

$h =$

$a =$

$b =$

Example: What is the fastest NAND8?

Administrivia


- Homework 6 due this week
- Projects (ASIC and FPGA) start this week

Logical Effort Design Examples

- For which F should we buffer?



- Sizing inverter fork

 

EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

25 Berkeley


EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

26 Berkeley

A modern technology is mostly wires

 - Transistors are little things under the wires
- Many layers of wires
- Wires are as important as transistors
 - Speed and power



EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

27 Berkeley

Wire Resistance

- ρ = resistivity ($\Omega \cdot \text{m}$)


$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

- R_{\square} = sheet resistance (Ω / \square)

- \square is a dimensionless unit(!)

- Count number of squares

 - $R = R_{\square} * (\# \text{ of squares})$




EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

28 Berkeley

Wire Capacitance

 - Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$



EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

29 Berkeley


EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

30 Berkeley

Wire RC Model

 - Wires are a distributed system
 - Approximate with lumped element models
- 3-segment pi-model is accurate to 3% in simulation




EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

31 Berkeley

Elmore Delay for RC Tree

 

$$t_{pd} \approx \sum_{\text{nodes } i} R_{i \rightarrow \text{source}} C_i$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$

EECS151 L15 LOGICAL EFFORT

Hkulić Fall 2021

32 Berkeley


Wires




Wire Delay



Example: RC Delay with Wire and Gate

 

Logical Effort with Wires

 

Summary

- Two delay components in logical effort:
 - Parasitic delay (p)
 - Effort delay (F)
 - Logical effort (g): intrinsic complexity of the gate
 - Electrical effort (h): load capacitance dependent
- Wires are modelled as RC
 - Most commonly just C for hand analysis