

# EECS 151/251A

## SP2022 Discussion 7

GSI: Yikuan Chen, Dima Nikiforov


Slides modified from Zhenghan Lin's and Harrison Liew's slides

# Agenda

- Inverter Delay – continue from last week's
- Logical Effort
- Elmore Delay
 
## Loaded Inverter Delay

$$\begin{aligned} t_{p,inv} &= \ln 2 \cdot R_{eq} (C_{p,tot} + C_L) \\ &= \ln 2 \cdot R_{eq} C_{p,tot} \left( 1 + \frac{C_L}{C_{p,tot}} \right) \\ &= \ln 2 \cdot R_{eq} C_{p,tot} \left( 1 + \frac{C_L}{\gamma C_{in}} \right) \\ &= \ln 2 \cdot R_{eq} C_{p,tot} \left( 1 + \frac{f}{\gamma} \right) \\ &= \ln 2 \cdot \tau_{inv} \left( 1 + \frac{f}{\gamma} \right) \end{aligned}$$



- Intrinsic vs. Extrinsic delay
  - Intrinsic  $\tau_{inv}$  independent of sizing
- Fanout **f** =  $C_L / C_{in}$
- Generalizable to any CMOS gate

# Inverter Chain Sizing

- Goal: minimize path delay
  - Assume 1<sup>st</sup> inverter has unit size ( $C_{in,1} = 1$ )



- Path delay:

$$D = t_{p1} + \dots + t_{pN} = (1 + f_1) + \dots + (1 + f_N)$$

- Path fanout  $F = \frac{C_L}{C_{in}}$

- Solution

  - Take partial derivatives w.r.t  $C_2, \dots, C_N$
- Get  $f_1 = f_2 = \dots = f_N$
- Min. path delay =  $Nf + N = N \sqrt[N]{F} + N$
- Size backwards






# Logical Effort


 
# Logical Effort, Parasitic Delay

- For any gate,  $D(\text{gate}) = LE \cdot FO + P$
- Logical Effort
  - $LE$ , Also defined as  $g$  in  $t_{p,\text{gate}} = \tau_{\text{inv}}(p + \frac{gf}{\gamma})$
  - $LE \equiv \frac{R_{eq,\text{gate}}C_{in,\text{gate}}}{R_{eq,\text{equiv}}C_{in,\text{inv}}}$ , i.e. ratio of  $C_{in,\text{gate}}$  to  $C_{in,\text{inv}}$  of a unit inverter with the same output current
  - Key to calculating LE: size the transistors to have the same  $R_{eq}$  as a unit inverter
- Parasitic Delay
  - Also defined as  $p$  in  $t_{p,\text{gate}} = \tau_{\text{inv}}(p + \frac{gf}{\gamma})$
  - Only difference from LE is that  $p$  looks at the ratio of  $C_{out,\text{gate}}$  to  $C_{out,\text{inv}}$  (intrinsic capacitance)



  
## PMOS/NMOS Resistance

- In lecture,  $LE_{NAND2} = LE_{NOR2} = \frac{3}{2}$ . What if  $R_{on,p} = K \cdot R_{on,n}$ ?


 
## Minimizing Path Delay

- Path Logical Effort:  $G = g_1 \cdot g_2 \cdot \dots \cdot g_N$
- Path fanout  $F = C_L / C_{in}$
- Branching, **b**
  - Extra loading factor  $b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}$
  - Add b to total path effort  $H = GFB$
- Solution is similar to single-branch inverter chain, except:
  - Calculate an “**effective fanout**” for each stage:  $EF = {}^N\sqrt{H}$
  - Size each stage such that  $EF = g_i \cdot f_i$ . You can control  $f_i$  by sizing!
  - Min. path delay =  $N * {}^N\sqrt{H} + \sum p_i$






## Logic Path with Branch - Example

$$LE_{NAND2} = LE_{NOR2} = \frac{3}{2}$$


$$LE_{NAND3} = LE_{NOR3} = 2$$

 


## Logic Path w/ Branch Example

$$LE_{NAND2} = LE_{NOR2} = \frac{3}{2}$$

$$LE_{NAND3} = LE_{NOR3} = 2$$

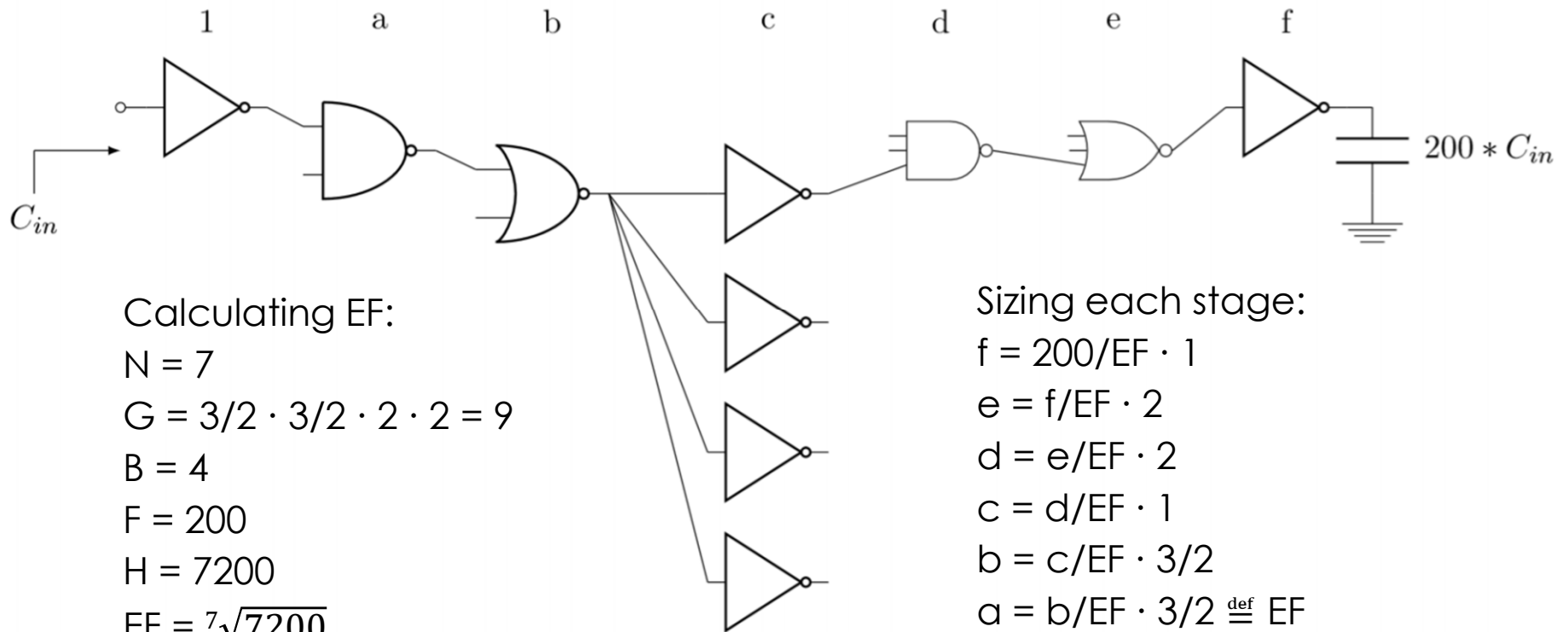
 
## Elmore Delay – “All the R’s for that C” or “All the C’s by that R”



$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$

Approximately the dominant RC time constant of a network


R's can be:

- Gate equivalent resistance  $R_{eq}$
- Wire resistance  $R = R_{\square} \cdot \# \text{ squares}$

C's can be:

- Gate  $C_{in}$  and  $C_p$ , load  $C_L$
- Wire plate & fringing capacitance

■  $\pi$  - model

 


Think of it 2 equivalent ways:

- $\sum [C_i \cdot (\text{sum of } R\text{'s charging } C_i)]$
- $\sum [R_i \cdot (\text{sum of } C\text{'s that } R_i \text{ charges})]$
 
## Elmore Example

- What parameters do we need?
- Draw the equivalent circuit Elmore RC model
- Calculate delay to  $V_a$



## Elmore Example


- What parameters do we need?

$$C_{in}, C_p, R_{on,p}, R_{on,n}, R_{wire}, C_{pp}, C_{fr}$$

- Draw the equivalent circuit Elmore RC model

- Calculate delay to  $V_a$

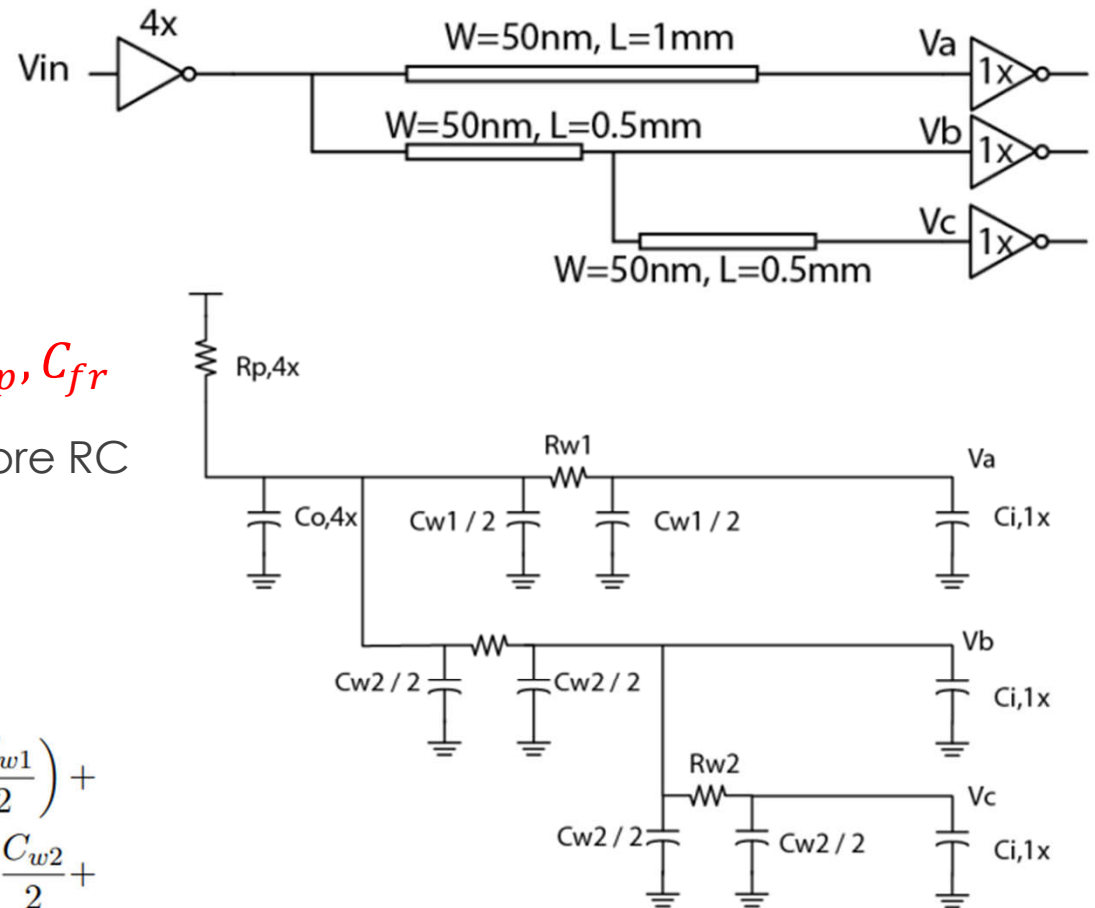
$$t_{p,a} = \ln 2 \cdot R_{w1} \cdot \left( C_{i,1x} + \frac{C_{w1}}{2} \right) + \ln 2 \cdot R_{p,4x} \cdot \left( C_{i,1x} + \frac{C_{w1}}{2} + C_{i,1x} + \frac{C_{w2}}{2} + \frac{C_{w2}}{2} + C_{i,1x} + \frac{C_{w2}}{2} + \frac{C_{w2}}{2} + \frac{C_{w1}}{2} + C_{o,4x} \right)$$


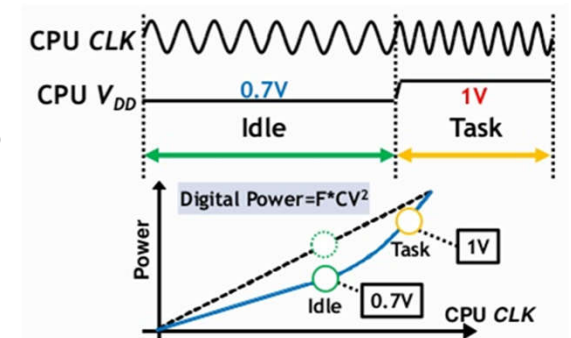
# Power/Energy in Digital Circuits


- Fundamentally, charging/discharging capacitors (gate, parasitic, load) through resistances (PMOS, NMOS, wires)
  - Capacitors draw  $CV^2$  joules from supply over 1 charge/discharge cycle
    - $\frac{1}{2}CV^2$  dissipated in PMOS as heat when charging
    - $\frac{1}{2}CV^2$  stored on capacitor, then dissipated in NMOS when discharging
- Dynamic power =  $P_{switching} = \alpha CV^2 f$ 
  - How to minimize each term?
  - Minimizing which terms reduces total energy consumed?
- Static power = leakage  $\rightarrow$  wasted energy!

Dynamic Voltage and Frequency Scaling (DVFS)


 
## Energy Example

- Initially:  $A = 1$ ,  $C = 1$ ,  $\text{Out} = 0$
- Energy pulled from supply when  $B = 1 \rightarrow 0$ ?
- Then, how much energy dissipated when  $C = 1 \rightarrow 0$ ?



## Energy Example

- Initially:  $A = 1$ ,  $C = 1$ ,  $\text{Out} = 0$
- Energy pulled from supply when  $B = 1 \rightarrow 0$ ?

Out can only be charged to  $V_{DD} - V_{th,n}$   
because NMOS passes "bad 1"

$$E = C_L V_{DD} (V_{DD} - V_{th,n})$$

- Then, how much energy dissipated when  $C = 1 \rightarrow 0$ ?

Out is discharged to  $|V_{th,p}|$  because  
PMOS passes "bad 0"

$$E = \frac{1}{2} * C_L * \left[ (V_{DD} - V_{th,n})^2 - V_{th,p}^2 \right]$$

