

inst.eecs.berkeley.edu/~eecs151

EECS151 : Introduction to Digital Design and ICs

Lecture 24 – Decoders

Bora Nikolić




Happy 50th birthday Intel 4004!

The Intel 4004 is a [4-bit central processing unit](#) (CPU) released by [Intel Corporation](#) in 1971. Sold for US\$60, it was the first commercially produced [microprocessor](#), and the first in a [long line of Intel CPUs](#). Launched November 15, 1971.

www.wikipedia.org
 
<https://www.intel.com/content/www/us/en/history/museum-story-of-intel-4004.html>



EECS151/251A L24 DECODERS

Nikolić Fall 2021

1



1

Review

- Dense memories are built as arrays of memory elements
 - SRAM is a static memory
- SRAM has unique combination of density, speed, power
- SRAM cells sized for stability and writeability
- SRAM and regfile cells can have multiple R/W ports

EECS151/251A L24 DECODERS

Nikolić Fall 2021

2



2



Memory Decoders

EECS151/251A L24 DECODERS


Nikolić Fall 2021

3

3

Decoder Design Example

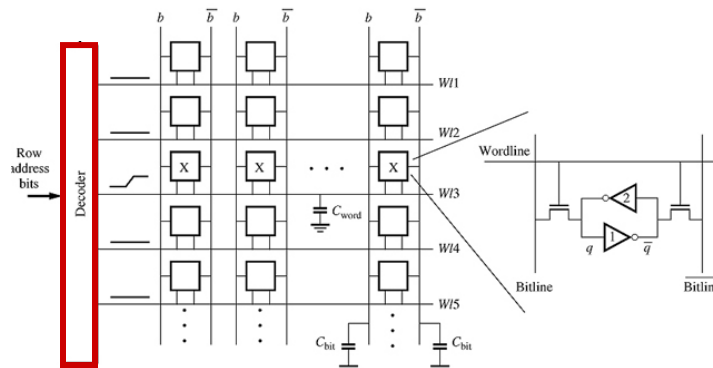- Look at decoder for 256x256 memory block (8KBytes)




EECS151/251A L24 DECODERS

Nikolić Fall 2021

4

Possible Decoder

 - 256 8-input AND gates
 - Each built out of a tree of NAND gates and inverters
- Need to drive a lot of capacitance (SRAM cells and wordline wire)
 - What's the best way to do this?



EECS151/251A L24 DECODERS


Nikolić Fall 2021

5 Berkeley UNIVERSITY OF CALIFORNIA

5

Possible AND8

 - Build 8-input NAND gate using 2-input gates and inverters
- Is this the best we can do?
- Is this better than using fewer NAND4 gates?



EECS151/251A L24 DECODERS


Nikolić Fall 2021

6 Berkeley UNIVERSITY OF CALIFORNIA

6

 Problem Setup

- Goal: Build fastest possible decoder with static CMOS logic
- What we know
 - Basically need 256 AND gates, each one of them drives one word line



EECS151/251A L24 DECODERS

Nikolić Fall 2021



7

Problem Setup (1)

- Each wordline has 256 cells connected to it
- $C_{WL} = 256 \cdot C_{cell} + C_{wire}$
 - Ignore wire for now
- Assume that decoder input capacitance is $C_{address} = 4 \cdot C_{cell}$

EECS151/251A L24 DECODERS

Nikolić Fall 2021



8

Problem Setup (2)

- Each address bit drives $2^8/2$ AND gates
 - A0 drives $1/2$ of the gates, A0_b the other $1/2$ of the gates
- Total fanout on each address wire is:

$$F = \Pi B \frac{C_{load}}{C_{in}} = 128 \frac{(256 C_{cell})}{4 C_{cell}} = 2^7 \frac{(2^8 C_{cell})}{2^2 C_{cell}} = 2^{13}$$

EECS151/251A L24 DECODERS

Nikolić Fall 2021



9

Decoder Fan-Out

- F of 2^{13} means that we will want to use more than $\log_4(2^{13}) = 6.5$ stages to implement the AND8
- Need many stages anyways
 - So what is the best way to implement the AND gate?
 - Will see next that it's the one with the most stages and least complicated gates


EECS151/251A L24 DECODERS

Nikolić Fall 2021



10

8-Input AND

 

EECS151/251A L24 DECODERS

Nikolić Fall 2021


 Berkeley
 UNIVERSITY OF CALIFORNIA

11

11

8-Input AND

 - Using 2-input NAND gates
 - 8-input gate takes 6 stages
- Total G is $(3/2)^3 \approx 3.4$
- So H is $3.4 \cdot 2^{13}$ – optimal N of ~ 7.4



EECS151/251A L24 DECODERS

Nikolić Fall 2021


 Berkeley
 UNIVERSITY OF CALIFORNIA

12

12


Decoder So Far

 - 256 8-input AND gates
 - Each built out of tree of NAND gates and inverters
- Issue:
 - Every address line has to drive 128 gates (and wire) right away
 - Forces us to add buffers just to drive address inputs



13

Look Inside Each AND8 Gate

 

14

Predecoders

- Use a single gate for each of the shared terms
 - E.g., from $A_0, \overline{A_0}, A_1, \text{ and } \overline{A_1}$, generate four signals: $A_0A_1, \overline{A_0}A_1, A_0\overline{A_1}, \overline{A_0}\overline{A_1}$
- In other words, we are decoding smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding


EECS151/251A L24 DECODERS

Nikolić Fall 2021



15

Predecoder and Decoder

 

EECS151/251A L24 DECODERS


Nikolić Fall 2021



16

Predecode Options

 - Larger predecode usually better:
 - More stages before the long wires
 - Decreases their effect on the circuit
 - Fewer number of long wires switches
 - Lower power
- Easier to fit 2-input gate into cell pitch



EECS151/251A L24 DECODERS

Nikolić Fall 2021

17 Berkeley



17

Administrivia

- Homework 10 posted on Friday, due 11/22
 - No homework during Thanksgiving
- Project checkpoints #2/#3 this week
- Next week:
 - Class lab and discussion on Monday
 - No classes/labs/discussions Tu and We

EECS151/251A L24 DECODERS

Nikolić Fall 2021

18 Berkeley



18



Building Larger Arrays

EECS151/251A L24 DECODERS

Nikolić Fall 2021

19

Berkeley
UNIVERSITY OF CALIFORNIA

19

Building Larger Custom Arrays

4kB	Dec	4kB	4kB	Dec	4kB
Col, I/O	Pre-Dec	Col, I/O	Col, I/O	Pre-Dec	Col, I/O
4kB	Dec	4kB	4kB	Dec	4kB
4kB	Dec	4kB	4kB	Dec	4kB
Col, I/O	Pre-Dec	Col, I/O	Col, I/O	Pre-Dec	Col, I/O
4kB	Dec	4kB	4kB	Dec	4kB

- Each subarray is 2-8kB
- Hierarchical decoding
- Peripheral overhead is 30-50%
- Delay is wire dominated
- Scratchpads, caches, TLBs

EECS151/251A L24 DECODERS

Nikolić Fall 2021

20


Berkeley
UNIVERSITY OF CALIFORNIA

20

Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

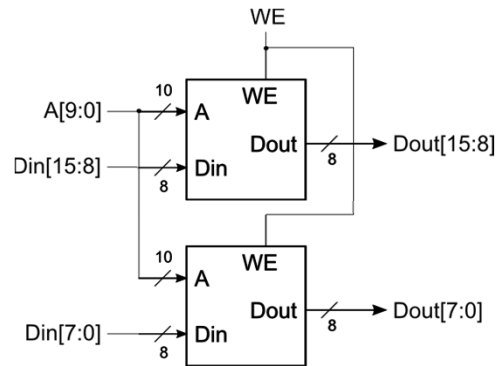Increasing the width. Example: given 1Kx8, want 1Kx16



EECS151/251A L24 DECODERS

Nikolić Fall 2021

21

Berkeley




21

Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

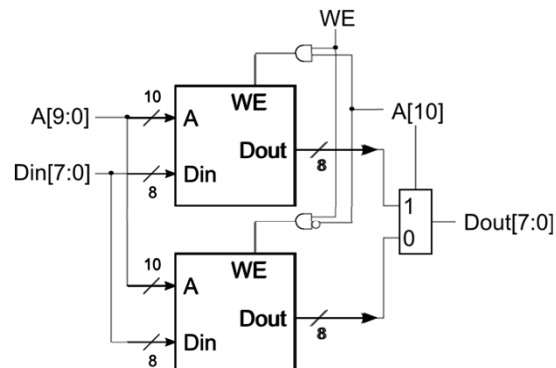Increasing the depth. Example: given 1Kx8, want 2Kx8



EECS151/251A L24 DECODERS

Nikolić Fall 2021

22

Berkeley




22

Adding Ports to Primitive Memory Blocks

Adding a read port to a simple dual port (SDP) memory.

 Example: given 1Kx8 SDP, want 1 write & 2 read ports.



EECS151/251A L24 DECODERS

Nikolić Fall 2021

23




23

Adding Ports to Primitive Memory Blocks

How to add a write port to a simple dual-port memory.

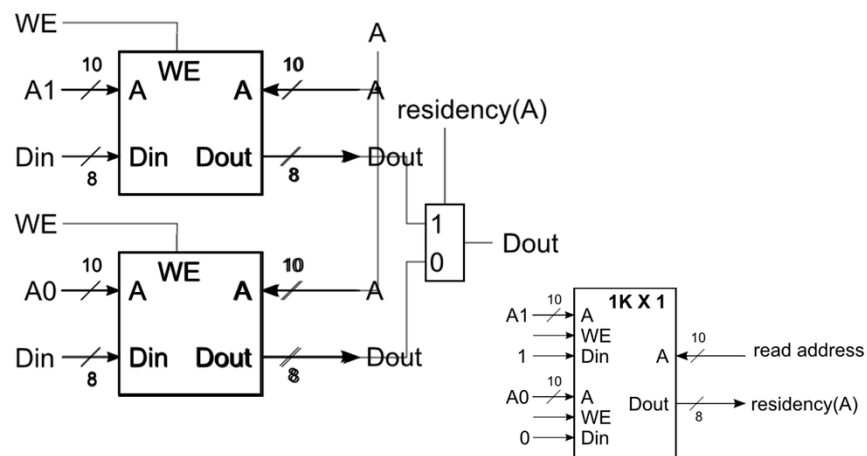Example: given 1Kx8 SDP, want 1 read & 2 write ports.




EECS151/251A L24 DECODERS

Nikolić Fall 2021

24



24



Caches

EECS151/251A L24 DECODERS

Nikolić Fall 2021

25 Berkeley UNIVERSITY OF CALIFORNIA

25

Caches (Review from 61C)

- **Two Different Types of Locality:**
 - **Temporal locality (Locality in time):** If an item is referenced, it tends to be referenced again soon.
 - **Spatial locality (Locality in space):** If an item is referenced, items whose addresses are close by tend to be referenced soon.
- **By taking advantage of the principle of locality:**
 - Present the user with as much memory as is available in the cheapest technology.
 - Provide access at the speed offered by the fastest technology.
- **DRAM is slow but cheap and dense:**
 - Good choice for presenting the user with a BIG memory system
- **SRAM is fast but expensive and not as dense:**
 - Good choice for providing the user FAST access time.

EECS151/251A L24 DECODERS

Nikolić Fall 2021


26 Berkeley UNIVERSITY OF CALIFORNIA

26

 Example: 1 KB Direct Mapped Cache with 32-B Blocks

For a 2^N -byte cache:

- The uppermost $(32 - N)$ bits are always the Cache Tag
- The lowest M bits are the byte-select offset (Block Size = 2^M)



EECS151/251A L24 DECODERS

Nikolić Fall 2021

27

Berkeley




27

Fully Associative Cache

Fully Associative Cache

- Ignore cache Index for now
- Compare the Cache Tags of all cache entries in parallel (expensive...)
- Example: Block Size = 32 B blocks, we need N 27-bit comparators

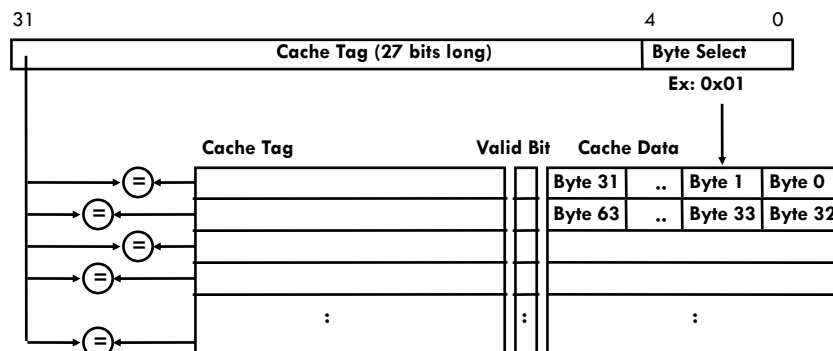By definition: Conflict Miss = 0 for a fully associative cache



EECS151/251A L24 DECODERS

Nikolić Fall 2021

28

Berkeley



28


Set Associative Cache

N-way set associative: N entries for each Cache Index

- N direct mapped caches operate in parallel

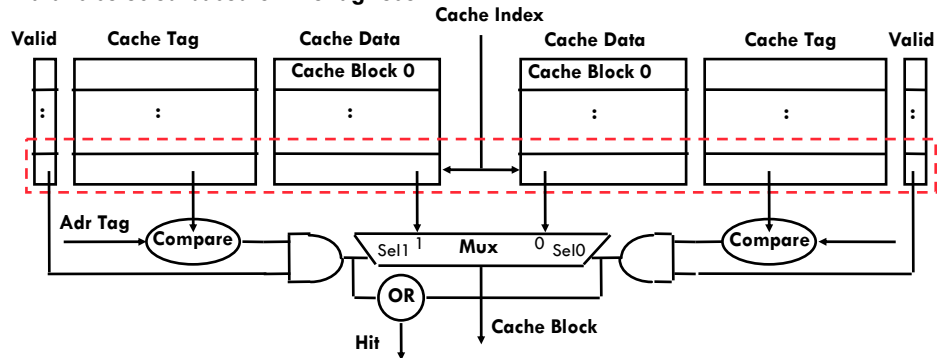Example: Two-way set associative cache

- Cache Index selects a “set” from the cache
- The two tags in the set are compared to the input in parallel
- Data is selected based on the tag result



EECS151/251A L24 DECODERS

Nikolić Fall 2021

29

29


Disadvantage of Set Associative Cache

N-way Set Associative Cache versus Direct Mapped Cache:

- N comparators vs. 1
- Extra MUX delay for the data
- Data comes **AFTER** Hit/Miss decision and set selection

In a direct mapped cache, Cache Block is available **BEFORE Hit/Miss:**

 - Possible to assume a hit and continue. Recover later if miss.



EECS151/251A L24 DECODERS

Nikolić Fall 2021

30

30

Block Replacement Policy

- Direct-Mapped Cache
 - index completely specifies position which position a block can go in on a miss
- N-Way Set Assoc
 - index specifies a set, but block can occupy any position within the set on a miss
- Fully Associative
 - block can be written into any position
- Question: if we have the choice, where should we write an incoming block?
 - If there's a valid bit off, write new block into first invalid.
 - If all are valid, pick a replacement policy
 - rule for which block gets "cached out" on a miss.

EECS151/251A L24 DECODERS

Nikolić Fall 2021

31



31

Block Replacement Policy: LRU

- LRU (Least Recently Used)
 - Idea: cache out block which has been accessed (read or write) least recently
 - Pro: temporal locality → recent past use implies likely future use: in fact, this is a very effective policy
 - Con: with 2-way set assoc, easy to keep track (one LRU bit); with 4-way or greater, requires more complicated hardware and more time to keep track of this

EECS151/251A L24 DECODERS

Nikolić Fall 2021

32



32

Summary

- Memory decoding is done hierarchically
 - Wire-limited in large arrays
- Multiple cache levels make memory appear both fast and big
- Direct mapped and set-associative cache