

inst.eecs.berkeley.edu/~eecs151

# EECS151 : Introduction to Digital Design and ICs


## Lecture 15 – Logical Effort

Bora Nikolić


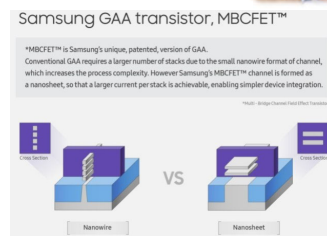
### Samsung Foundry Promises Gate All-Around in '22

October 14, 2021, EETimes - Samsung Foundry recently held its Foundry Forum where it revealed some details of its semiconductor process roadmaps and fab expansion. Samsung is being most aggressive pursuing the next generation of transistor technology, with plans to reach mass production ahead of TSMC and Intel. Samsung's 3-nanometer process will use the gate-all-around (GAA) transistor structure, which the foundry calls MBCFET (Multi-bridge channel FET) and will be in production first half of 2022. TSMC will wait another generation until its N2 process to deliver GAA some time in 2023.



EETimes

Nikolić Fall 2021

1 Berkeley UNIVERSITY OF CALIFORNIA

EECS151 L15 LOGICAL EFFORT

1

## Review

- Delay is a linear function of R and C
- Delay optimization is critical to improve the frequency of the circuit.
- The dimensions of a transistor affect its capacitance and resistance.
- We use RC delay model to describe the delay of a circuit.

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

2 Berkeley UNIVERSITY OF CALIFORNIA

2



## Minimizing Logic Delay

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

 3 Berkeley  
 UNIVERSITY OF CALIFORNIA

3
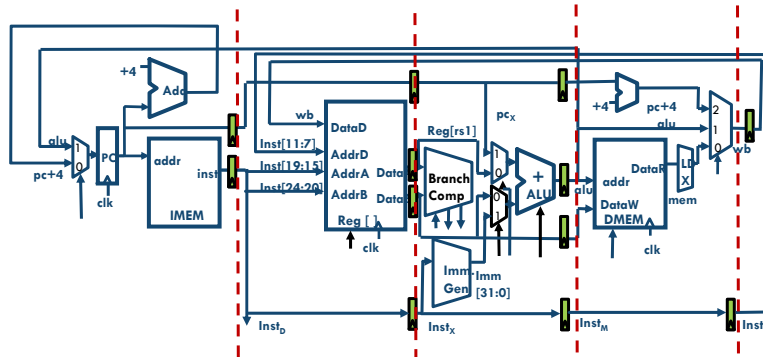
## How Do We Optimize the Delay?

- How fast can a pipelined processor run?
- What is the fastest adder?




EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

 4 Berkeley  
 UNIVERSITY OF CALIFORNIA

4

## Inverter RC Delay

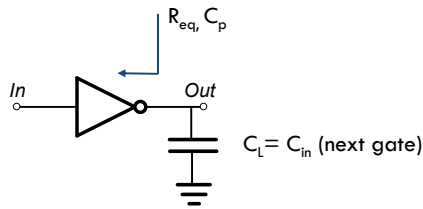

- $t_p = R_{eq}(C_p + C_L) = R_{eq}(C_{in}/\gamma + C_L)$ 
  - $\gamma = 1$  (closer to 1.2 in recent processes)
- $t_p = R_{eq}C_{in}(1 + C_L/C_{in}) = \tau_{INV}(1 + f)$ 
  - Propagation delay is proportional to fanout
- Normalized Delay =  $1 + f$

$$\text{Fanout} = f = C_L/C_{in}$$

$$t_p = \tau_{INV}(1 + f)$$

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

5



5

## Generalizing to Arbitrary Gates

- Delay has two components:  $d = h + p$
- $h$ : effort delay =  $gf$  (a.k.a. stage effort)
  - Again has two components
- $g$ : logical effort
  - Measures relative ability of gate to deliver current
  - $g = 1$  for inverter
- $f$ : electrical effort =  $C_{out} / C_{in}$ 
  - Ratio of output to input capacitance
  - Sometimes called fanout
- $p$ : parasitic delay
  - Represents delay of gate driving no load
  - Set by internal parasitic capacitance

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

6



6

## Inverter Delay

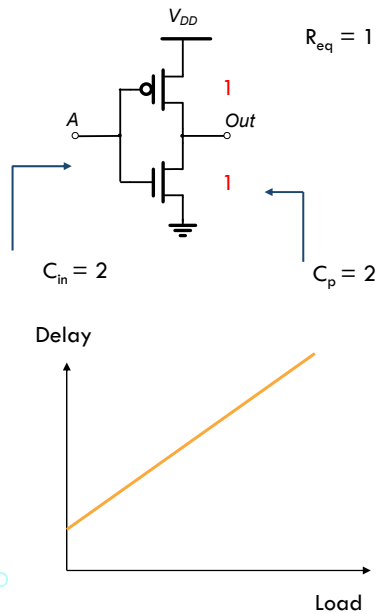

- Parasitic  $p$  is the ratio of intrinsic capacitance to an inverter
  - $p(\text{inverter}) =$
- Logical Effort  $g$  is the ratio of input capacitance to an inverter
  - $g(\text{inverter}) =$
- Electrical Effort  $h$  is the ratio of the load capacitance to the input capacitance
  - $h(\text{inverter}) =$
- Delay  $= p + h = p + g * f = 1 + f$

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

7



7

## NAND2 Gate

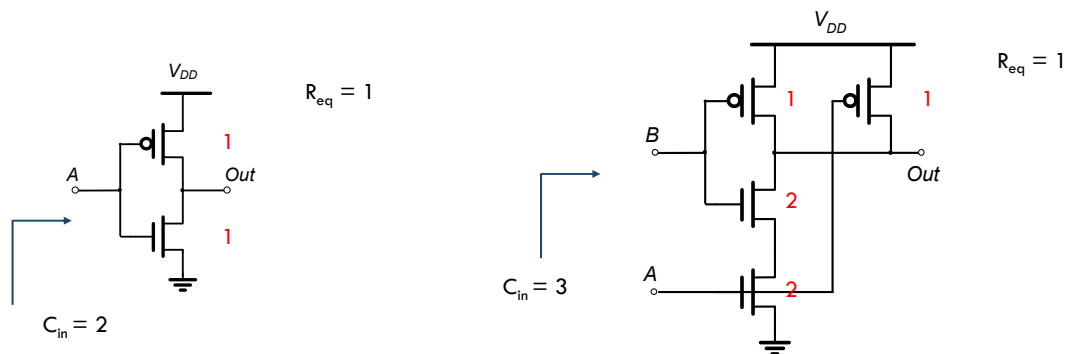

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

8



8

## Logical Effort of NAND2 Gate

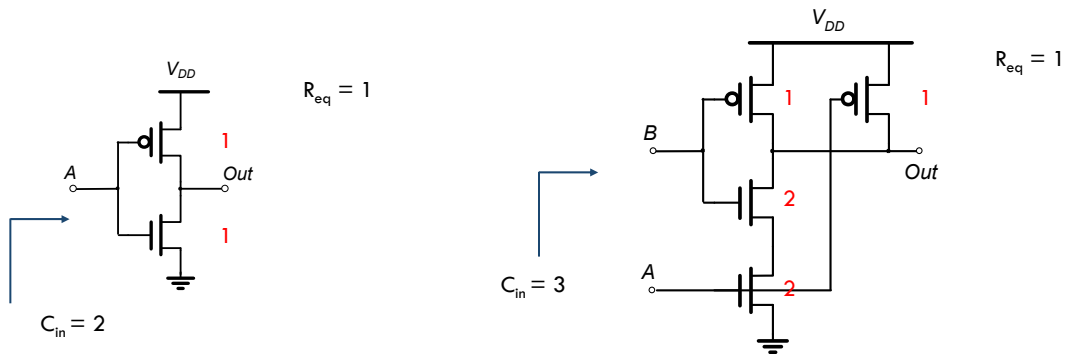

- In velocity-saturated devices  $I_{on}$  of a stack is  $2/3$  (not a half) of two devices
  - So the correct upsizing factor is 1.5 (not 2)
- We will use 2, as it makes calculations easier


EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

9 Berkeley UNIVERSITY OF CALIFORNIA

9

## NOR2 Gate

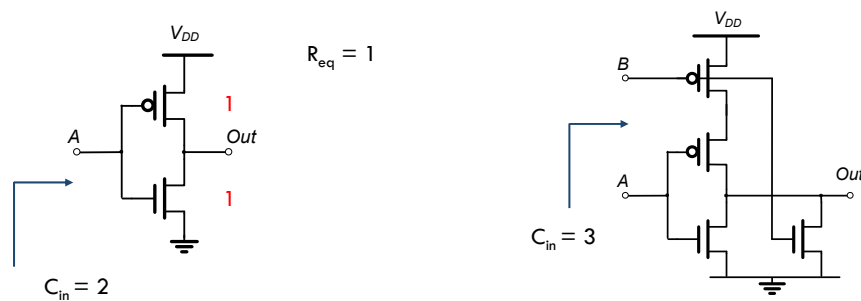


EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

10 Berkeley UNIVERSITY OF CALIFORNIA

10

## Example: Inverter Chain

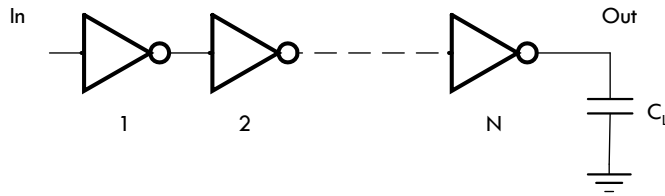

Logical Effort:  $g =$

Electrical Effort:  $f =$

Parasitic Delay:  $p =$

Stage Delay:  $d =$

Total Delay:  $d_{\text{total}} =$

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

11



11

## Optimize Delay of an Inverter Chain

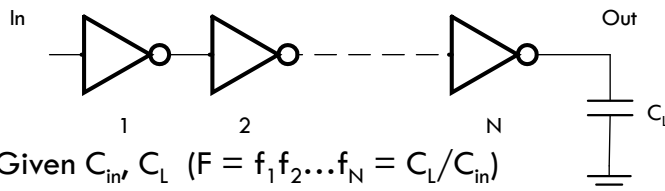

Given  $C_{\text{in}}, C_L$  ( $F = f_1 f_2 \dots f_N = C_L / C_{\text{in}}$ )

How to optimally size inverter chain to minimize delay?

...There are  $N-1$  unknowns:  $C_2, C_3, \dots, C_N$

$d = (1 + C_2 / C_{\text{in}}) + (1 + C_3 / C_2) + \dots + (C_L / C_N)$

Solution: All delays are equal,  $C_2 / C_{\text{in}} = C_3 / C_2 = \dots = C_L / C_N$

$$\frac{C_{i+1}}{C_i} = \sqrt[N]{\frac{C_L}{C_{\text{in}}}}$$

$$C_i = \sqrt{C_{i+1} C_{i-1}}$$

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021


12



12
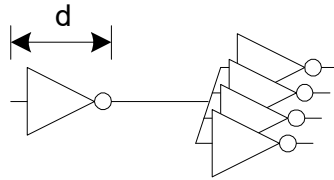
## Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g =$

Electrical Effort:  $f =$

Parasitic Delay:  $p =$

Stage Delay:  $d =$

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021 13


Berkeley



13
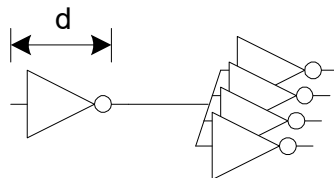
## Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g = 1$

Electrical Effort:  $f = 4$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 5$

Fanout-of-4 is commonly used to  
normalize the circuit  
delay across technologies

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021 14

Berkeley



14


## Multi-stage Logic Networks

- Logical effort generalizes to multistage networks

- Path Logical Effort**  $G = \prod g_i$

- Path Electrical Effort**  $F = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

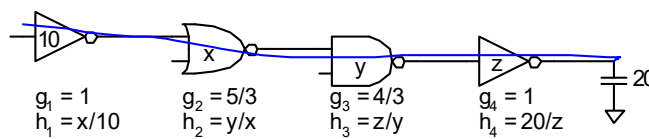- Path Effort**  $H = \prod h_i = \prod g_i f_i$



EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

15 Berkeley UNIVERSITY OF CALIFORNIA

15

## Branching Effect

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}} \quad B = \prod b_i$$

$$G = 1$$

$$F = 90 / 5 = 18$$


$$GF = 18$$

$$f_1 = (15 + 15) / 5 = 6$$

$$f_2 = 90 / 15 = 6$$

$$B = 2$$

$$F = g_1 g_2 h_1 h_2 = 36 = BGH$$

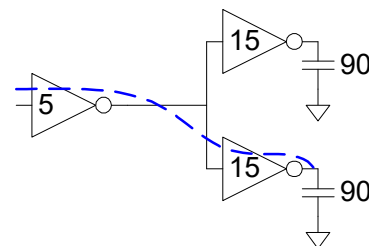

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

16 Berkeley UNIVERSITY OF CALIFORNIA

16



## Designing Fast Circuits

$$D = \sum d_i = H + P$$

- Delay is smallest when each stage bears same effort

$$\hat{h} = g_i f_i = H^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NH^{\frac{1}{N}} + P$$

- And we can find the gate sizes that result in optimal delay

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

17

Berkeley




17

## Example: Best Number of Stages

- How many stages should a path use?
  - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

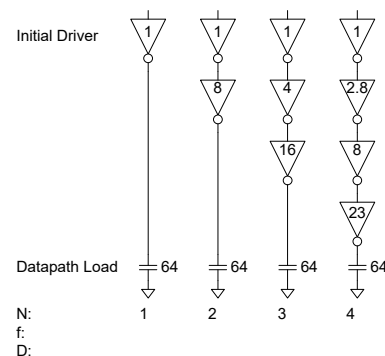

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

18

Berkeley




18

## Example: Best Number of Stages

- How many stages should a path use?
  - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

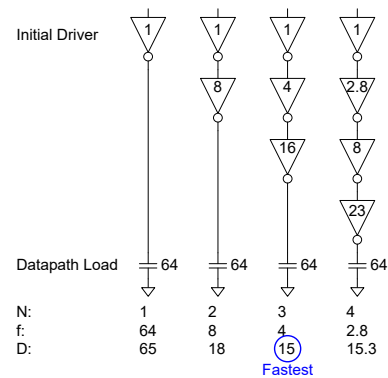

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

19



Berkeley



19
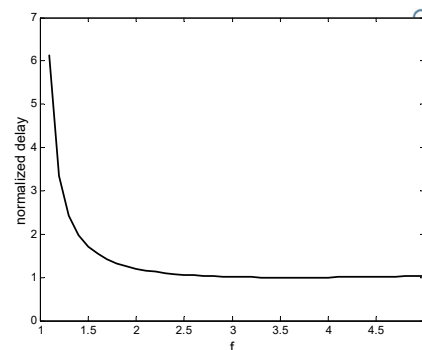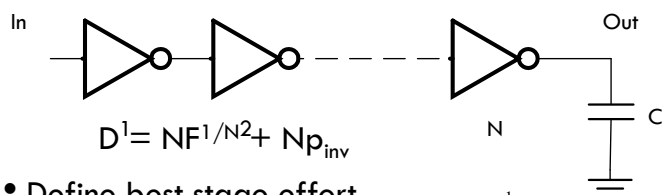
## Best Stage Effort

- How many stages should a path use?
  - To drive given capacitance



- Define best stage effort  $\rho = F^{1/N}$
- Neglecting parasitics ( $p_{inv} = 0$ ), we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , solve numerically for  $\rho = 3.59$
- Choose 4 – less stages, less energy
- Extends to any logic path with  $h = 4$

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

20

Berkeley



20

## Logical Efforts Method

- 1) Compute path effort  $H = GBF$
- 2) Estimate best number of stages  $N = \log_4 H$
- 3) Sketch path with N stages  $D = NH^{\frac{1}{N}} + P$
- 4) Estimate least delay  $\hat{h} = H^{\frac{1}{N}}$
- 5) Determine best stage effort  $C_{in_i} = \frac{g_i C_{out_i}}{\hat{h}}$
- 6) Find gate sizes

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

21



21

## Example: Optimize Delay

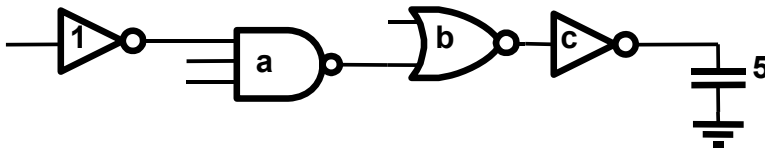

$$\begin{array}{llll} g = 1 & g = 4/2 & g = 3/2 & g = 1 \\ f = a & f = b/a & f = c/b & f = 5/c \end{array}$$

Effective fanout,  $F =$  $G =$  $H =$  $h =$  $a =$  $b =$ 


EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

22



22





## Example: What is the fastest NAND8?


EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

23 Berkeley UNIVERSITY OF CALIFORNIA



23





## Administrivia

- Homework 6 due this week
- Projects (ASIC and FPGA) start this week

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021



24 Berkeley UNIVERSITY OF CALIFORNIA




24

## Logical Effort Design Examples

- For which  $F$  should we buffer?

 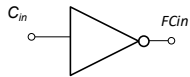

- Sizing inverter fork

 

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

25

Berkeley  
UNIVERSITY OF CALIFORNIA

25



## Wires

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021


26

Berkeley  
UNIVERSITY OF CALIFORNIA

26
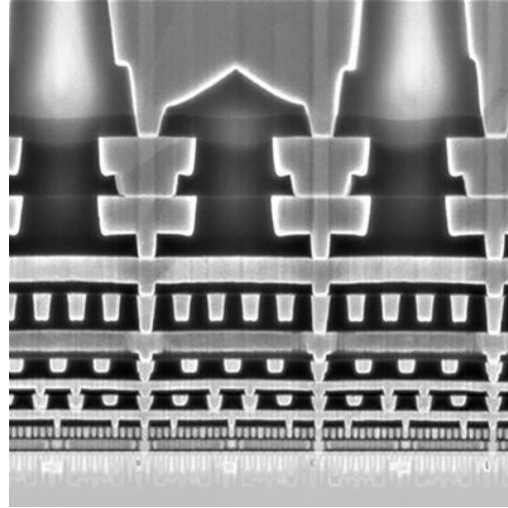
## A modern technology is mostly wires

- Transistors are little things under the wires
- Many layers of wires
- Wires are as important as transistors
  - Speed and power



EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

27


Berkeley



27
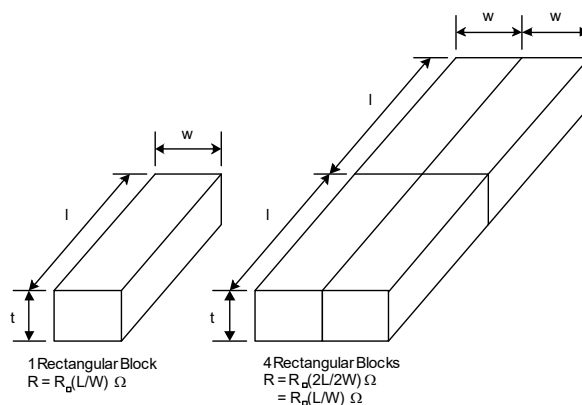
## Wire Resistance

- $\rho$  = resistivity ( $\Omega \cdot \text{m}$ )
- $$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$
- $R_{\square}$  = sheet resistance ( $\Omega/\square$ )
  - $\square$  is a dimensionless unit(!)
- Count number of squares
  - $R = R_{\square} * (\text{\# of squares})$



EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

28


Berkeley



28
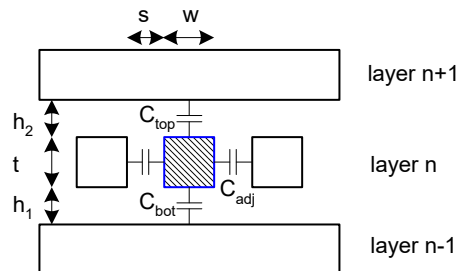
## Wire Capacitance

- Wire has capacitance per unit length
  - To neighbors
  - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$



29




## Wire Delay

30
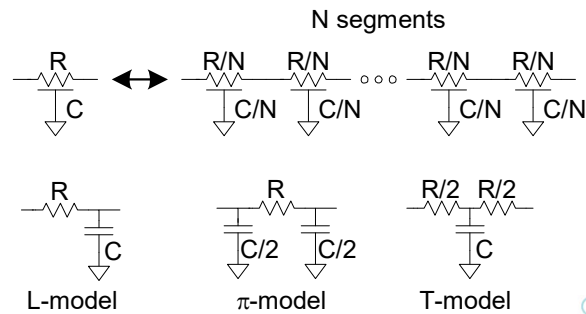
## Wire RC Model

- Wires are a distributed system
  - Approximate with lumped element models
- 3-segment pi-model is accurate to 3% in simulation




EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

31 Berkeley UNIVERSITY OF CALIFORNIA

31

## Elmore Delay for RC Tree

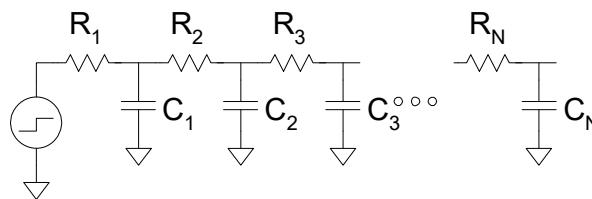

$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

32 Berkeley UNIVERSITY OF CALIFORNIA

32



### Example: RC Delay with Wire and Gate

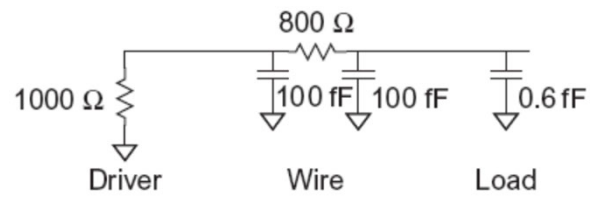

EECS151 L15 LOGICAL EFFORT


Nikolić Fall 2021

33



33

### Logical Effort with Wires

 

EECS151 L15 LOGICAL EFFORT

Nikolić Fall 2021

34



34

## Summary

- Two delay components in logical effort:
  - Parasitic delay ( $p$ )
  - Effort delay ( $F$ )
    - Logical effort ( $g$ ): intrinsic complexity of the gate
    - Electrical effort ( $h$ ): load capacitance dependent
- To minimize the delay all stages should have the same effort ( $h$ )
- Ideal effort is 4
- Wires are modelled as RC
  - Most commonly just  $C$  for hand analysis