

## EECS 151/251A Homework 2

Due Friday, Feb 11<sup>th</sup>, 2022


### Problem 1: Moment of Truth Table

Please translate the following expressions/sentence/diagram into a truth table (you don't have to simplify the expressions in your solution)

(a)  $Y = \overline{A\overline{B}} + \overline{\overline{A}BC} + \overline{C}$

(b) If A, then either both B and C or neither, else not B.

(c)

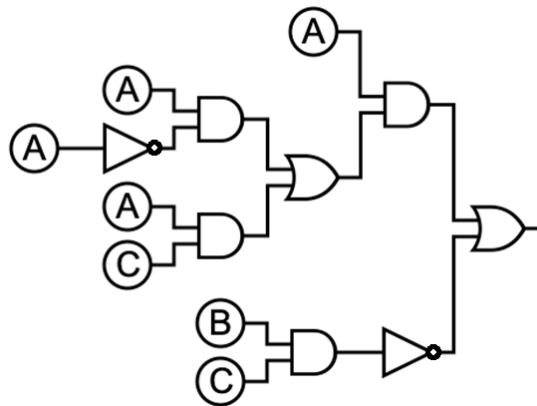

### Problem 2: Boo...lean

Simplify the following expression to minterms (sum of product) expression (hint: you might want to consider starting with De Morgan's Law)

$$Y = \overline{(DC + (\overline{DC} + B\overline{A})D)} + B(\overline{A + \overline{C}})$$

### Problem 3: K for Karnaugh Map

Derive the minterm/maxterm expressions for the following K-maps, whichever is simplified the most

(a)

CD \ AB	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	0
10	0	0	0	0

(b)

CD \ AB	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	0	1
10	1	1	0	1

(c)

CD \ AB	00	01	11	10
00	0	1	0	0
01	0	1	1	1
11	0	1	0	0
10	0	1	0	0

#### Problem 4: Mealy or Moore

Identify whether the following diagram represents a Mealy Machine or a Moore Machine, and then convert it to the other type (Mealy to Moore, Moore to Mealy)

