

EECS 151/251A

SP2022 Discussion 6

GSI: DIMA NIKIFOROV, YIKUAN CHEN

Agenda





- MOS
- CMOS
- Inverters/Inverter Chain

MOS

Metal Oxide Semiconductor (MOS) Transistors

- Used to be made in a planar process
 - Wafer is usually p-doped
 - 3 main contacts
 - Gate
 - Source
 - Drain
 - Gate controls current flow from Source to Drain


resistor

    

Metal Oxide Semiconductor (MOS) Transistors


- MOS turns “on” when voltage applied across gate-source
- Voltage causes top layer of silicon to invert types, connecting S to D

MOSFET
↓
Field Effect

 


Metal Oxide Semiconductor (MOS) Transistors

 
- MOS transistors are non-ideal switches
 - $0 < R_{ON} \ll R_{OFF} < \infty$
- NMOS
 - The *source* of NMOS always at *lower* voltage
 - Ideal for passing *low* voltage (0, gnd)
- PMOS
 - The *source* of PMOS always at *higher* voltage
 - Ideal for passing high voltage (1, vdd)
- The 'effective' source node can change depending on the voltage at the MOS' terminals






MOS

 

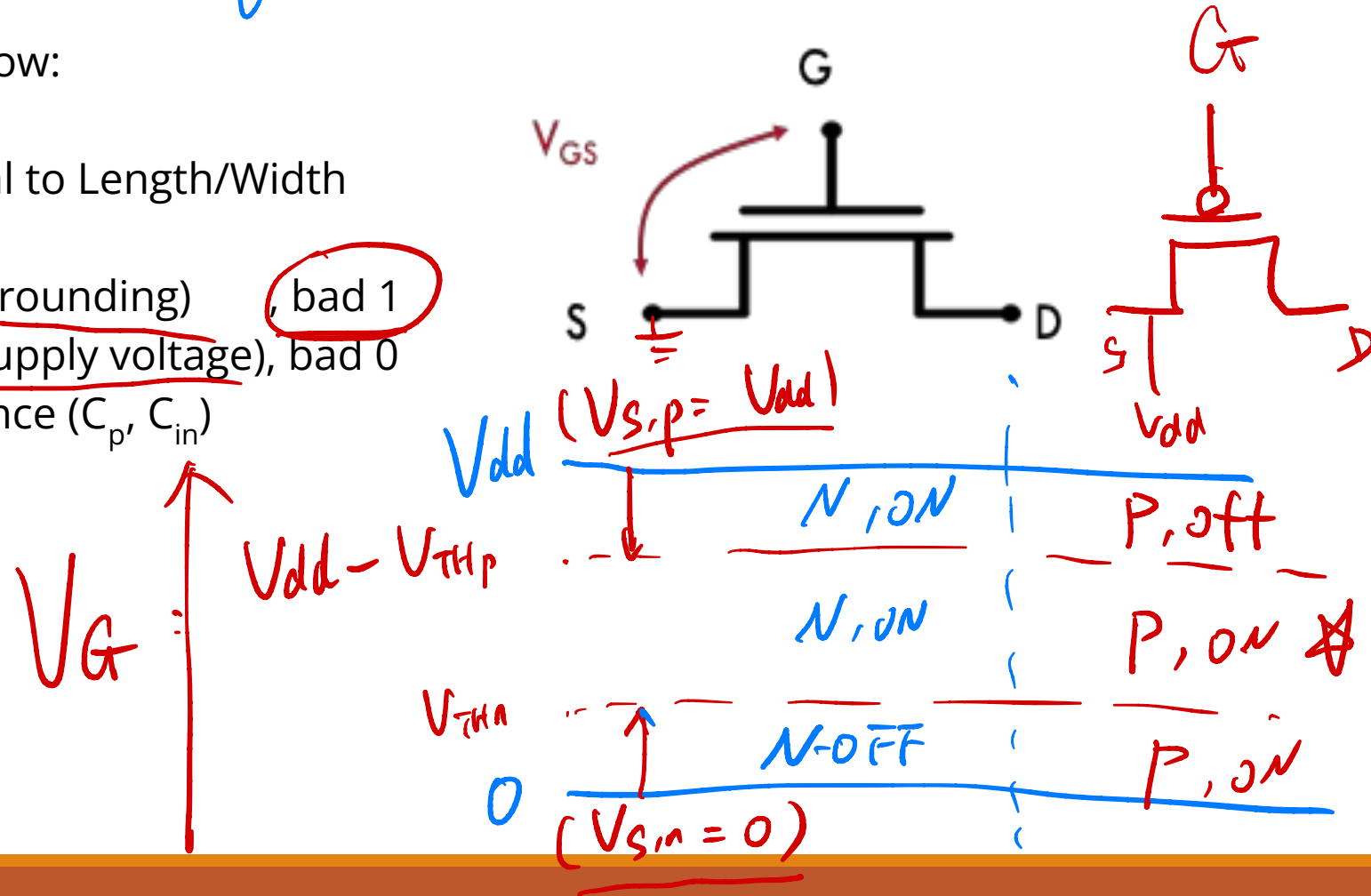- In this class, you only need to know:
 - MOS switch model
 - On-resistance is proportional to Length/Width
 - Difference of NMOS/PMOS
 - NMOS: good for passing 0 (grounding), bad 1
 - PMOS: good for passing 1 (supply voltage), bad 0
 - Simplified parasitic capacitance (C_p , C_{in})




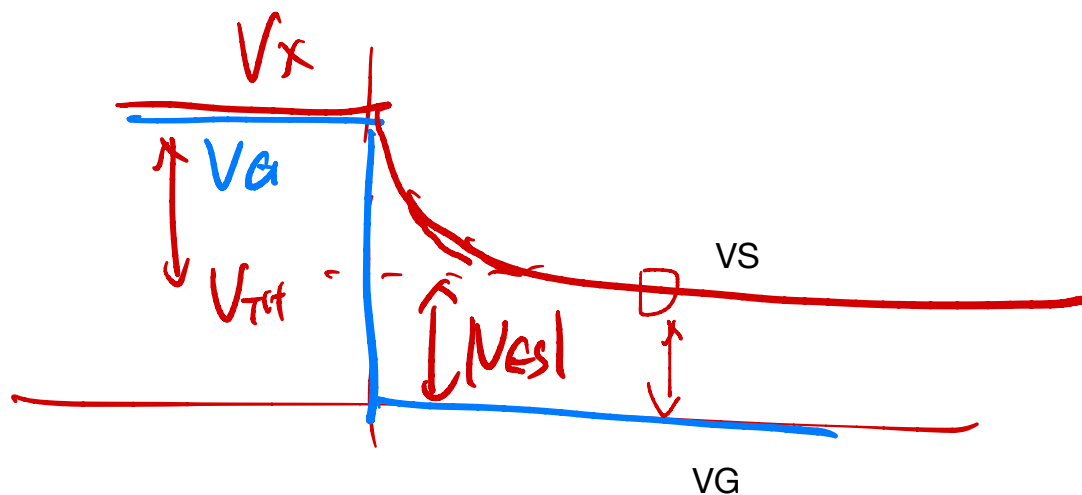
 
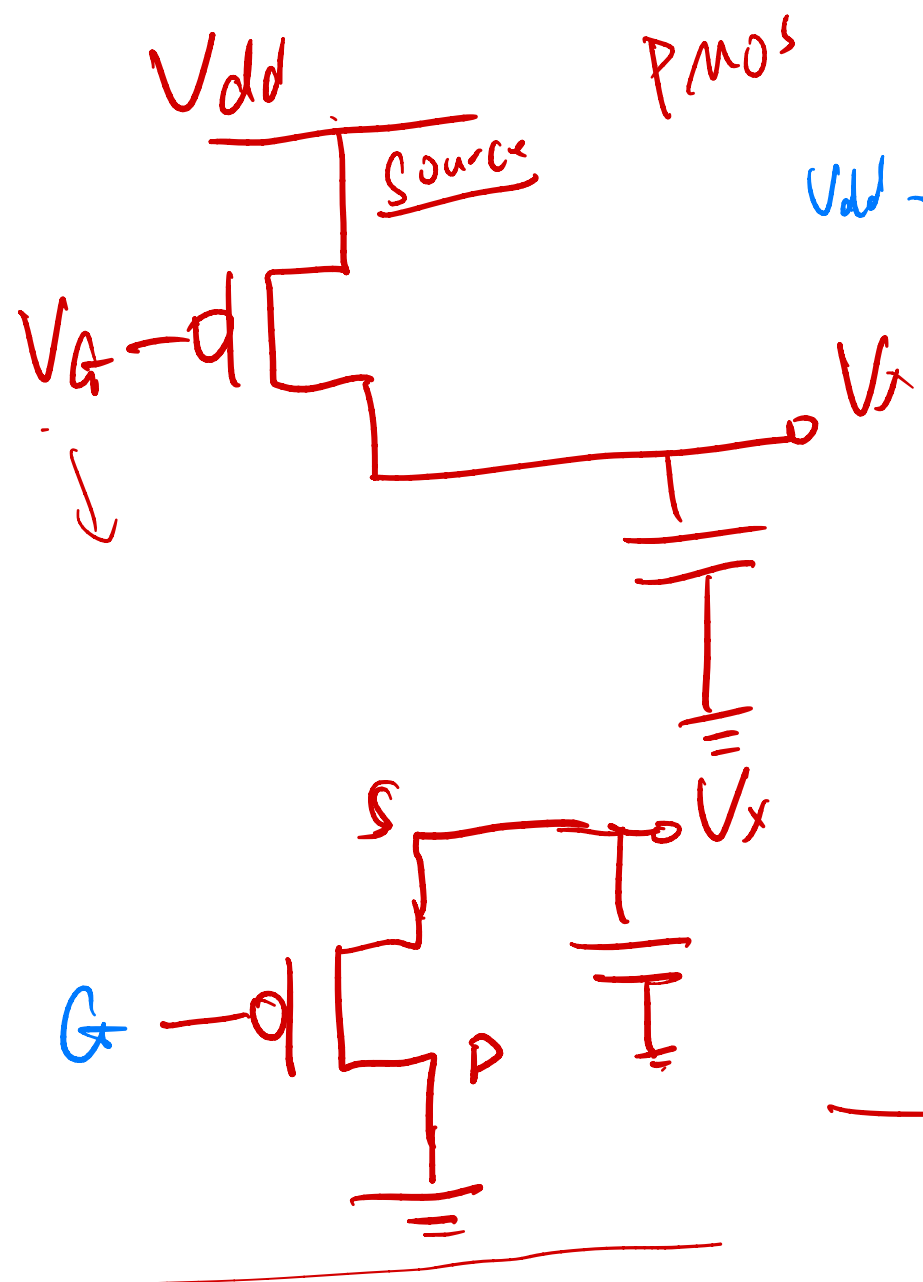


$|V_G - V_S| > |V_{TH}| \rightarrow$ channel forms, charge can flow

CMOS



CMOS Inverter

    - Complementary Metal Oxide Semiconductor
 - Inverter has 1 NMOS and 1 PMOS
- NMOS and PMOS each have an “on” and “off” resistance
- Voltage Transfer Curve (VTC)
 - Mid/switching-point is a function of PMOS vs NMOS strength




CMOS Margins

  - Noisy, but still want 1s and 0s (digital)
 - "Restoration" / "regeneration" property



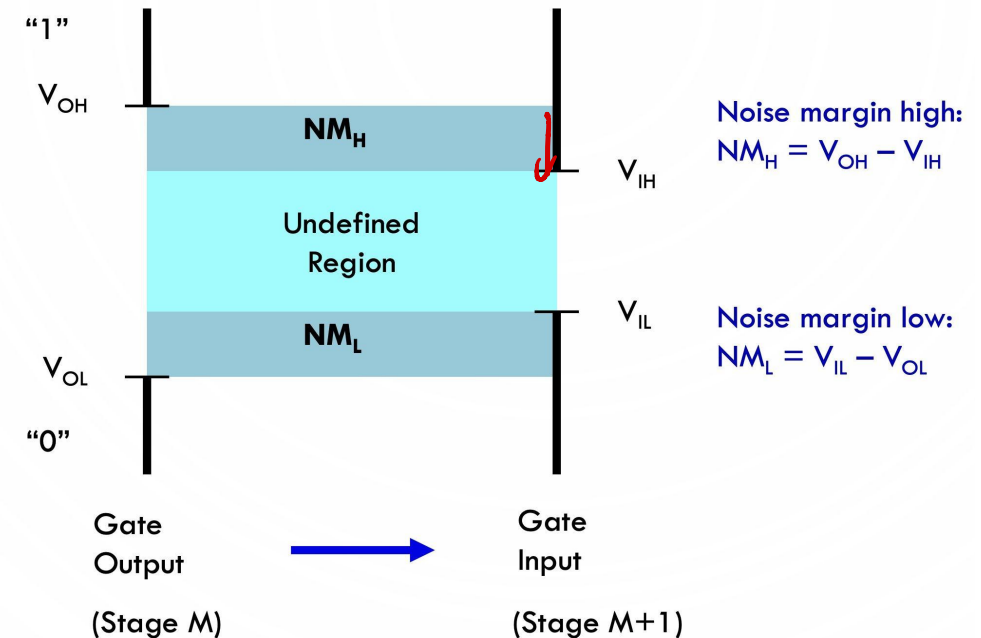- Noise margins
 - The amount of noise that can be tolerated such that the signal can be correctly interpreted by the next gate
 - Eg. in a chain of inverters




CMOS Exercise

- Implement a NAND gate in CMOS:

CMOS Inverters

Impact of Inverter Sizing
 
$$\underline{\underline{\tau}} \propto \underline{\underline{R \cdot C}}$$



- $C_{in} \propto \underline{\underline{WL}}$, $C_p \propto W$
 - C_{in} dominated by $C_{g,pmos} + C_{g,nmos}$
 - $C_p = \gamma C_{in}$. C_p is dominated by $C_{d,pmos} + C_{d,nmos}$. $\gamma \approx 1$.
- $R_{eq} \propto L/W$ $R = \frac{\rho \cdot L}{A}$
- Inverter usually sized for $t_{p,LH} = t_{p,HL}$
 - How is $\underline{\underline{W_p : W_n}}$ a function of $\underline{\underline{\rho_p : \rho_n}}$?
- How does the RC delay change if:
 - Either $\underline{\underline{W_p}}$ or $\underline{\underline{W_n}}$ doubled?
 - Both $\underline{\underline{W_p}}$ and $\underline{\underline{W_n}}$ doubled?



$$\begin{aligned} R_{on} \cdot C &= R_{on} \cdot C \\ R_p &= R_n \\ \rho_p \cdot \frac{L_p}{W_p \cdot t} &= \rho_n \cdot \frac{L_n}{W_n \cdot t} \\ \frac{W_p}{W_n} &= \frac{\rho_n}{\rho_p} \end{aligned}$$

$$\tau = R_{eq} \cdot C$$

Loaded Inverter Delay

$$\begin{aligned}
 t_{p,inv} &= \ln 2 \cdot R_{eq} (C_{p,tot} + C_L) \\
 &= \ln 2 \cdot R_{eq} C_{p,tot} \left(1 + \frac{C_L}{C_{p,tot}} \right) \\
 &= \ln 2 \cdot R_{eq} C_{p,tot} \left(1 + \frac{C_L}{\gamma C_{in}} \right) \\
 &= \ln 2 \cdot R_{eq} C_{p,tot} \left(1 + \frac{f}{\gamma} \right) \\
 &= \ln 2 \cdot \tau_{inv} \left(1 + \frac{f}{\gamma} \right)
 \end{aligned}$$

$$C_p = C_{in} \cdot \delta$$

  

- Intrinsic vs. Extrinsic delay
 - Intrinsic τ_{inv} independent of sizing
- Fanout $f = C_L / C_{in}$
- Generalizable to any CMOS gate

Inverter Chain Sizing



- Goal: minimize path delay
 - Assume 1st inverter has unit size ($C_{in,1} = 1$)

- Path delay $D = t_{p1} + \dots + t_{pN} = \underline{(1 + f_1)} + \dots + \underline{(1 + f_N)}$

- Path fanout $F = C_L / C_{in}$

- Solution

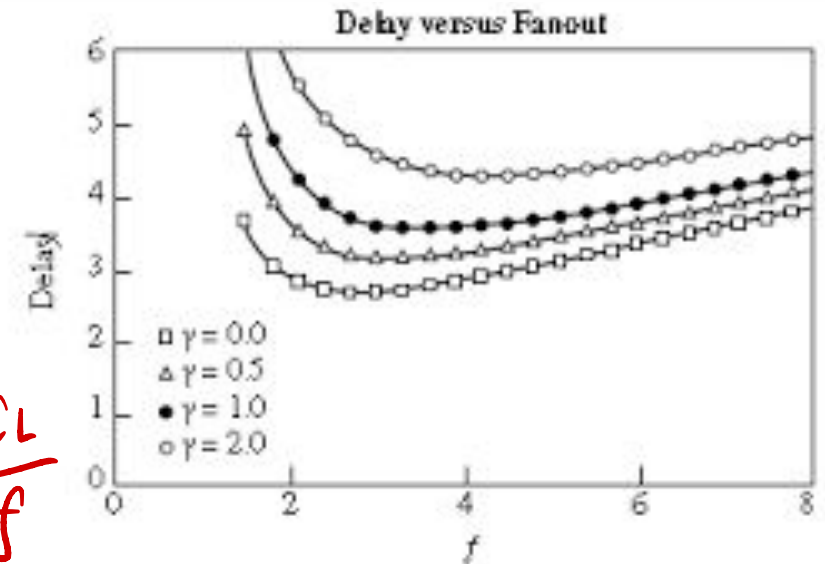 - Take partial derivatives w.r.t C_2, \dots, C_N
- Get $f_1 = f_2 = \dots = f_N$
- Min. path delay = $\underline{Nf + N} = N \sqrt[N]{F} + N$
- Size backwards



$$= \frac{C_{in, last}}{f} = \frac{C_L}{f}$$

Questions?