

inst.eecs.berkeley.edu/~eecs151

EECS151 : Introduction to Digital Design and ICs

Lecture 14 – Gate Delays


Bora Nikolić



Moore's Law Could Ride EUV for 10 More Years

September 30, 2021, EETimes - ASML plans to introduce new extreme ultraviolet (EUV) lithography equipment that will extend the longevity of Moore's Law for at least ten years, according to executives at the world's only supplier of the tools, which are crucial for the world's most advanced silicon.

Starting in the first half of 2023, the company plans to offer customers equipment that takes EUV numerical aperture (NA) higher to 0.55 NA from the existing 0.33 NA. The company believes that the new equipment will help chip makers reach process nodes well beyond the current threshold (2nm) for at least another 10 years, according to ASML vice president Teun van Gogh, in an interview with EE Times.

 

EETimes

EECS151 L13 DELAY

Nikolić Fall 2021

1

1

Review

- CMOS allows for convenient switch level abstraction
- CMOS pull-up and pull-down networks are complementary
 - Graph models for CMOS gates
- Transistor sizing affects gate performance

EECS151 L13 DELAY

Nikolić Fall 2021

2

2



CMOS Sizing

EECS151 L13 DELAY



Nikolić Fall 2021

 3 Berkeley
 UNIVERSITY OF CALIFORNIA


3

Transistor Sizing

- Impact of W_p/W_n on VTC

  

- In the past, $W_p > W_n$ (see Rabaey, 2nd ed)
- In modern processes (finFET), $W_p = W_n$

- Weak dependence on W_p/W_n

EECS151 L13 DELAY

Nikolić Fall 2021

 4 Berkeley
 UNIVERSITY OF CALIFORNIA


4



CMOS Delay


EECS151 L13 DELAY

Nikolić Fall 2021

 5 Berkeley
 UNIVERSITY OF CALIFORNIA

5

Capacitances

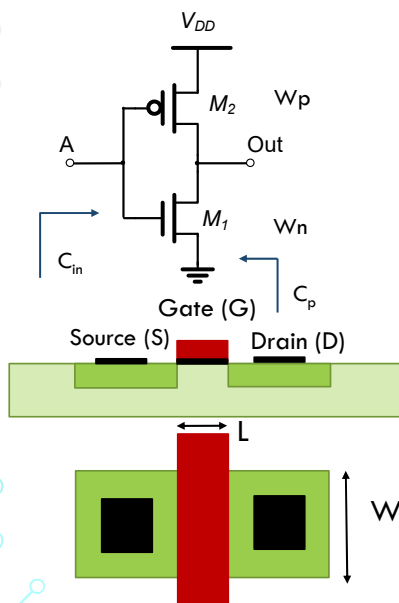

- C_{in} is largely set by the gate cap
 - $\sim WL$
 - $2xW = 2xC_{in}$
 - It is non-linear, but we will ignore that

- C_p is largely set by the drain cap
 - $\sim W$ (drain area/perimeter)
 - $2xW = 2xC_p$

$$C_p = \gamma C_{in}$$

EECS151 L13 DELAY


Nikolić Fall 2021

 6 Berkeley
 UNIVERSITY OF CALIFORNIA

6

Gate Sizing

 - Doubling the gate size (by doubling W_s):



- Doubles C_{in}
- Halves equivalent gate resistance
- Doubles C_p

EECS151 L13 DELAY


Nikolić Fall 2021

7 Berkeley UNIVERSITY OF CALIFORNIA



7

Inverter Delay

- How to time this?

 

  - Each gate has an R_{eq} and drives C_{in} of the next gate




EECS151 L13 DELAY


Nikolić Fall 2021

8 Berkeley UNIVERSITY OF CALIFORNIA


8

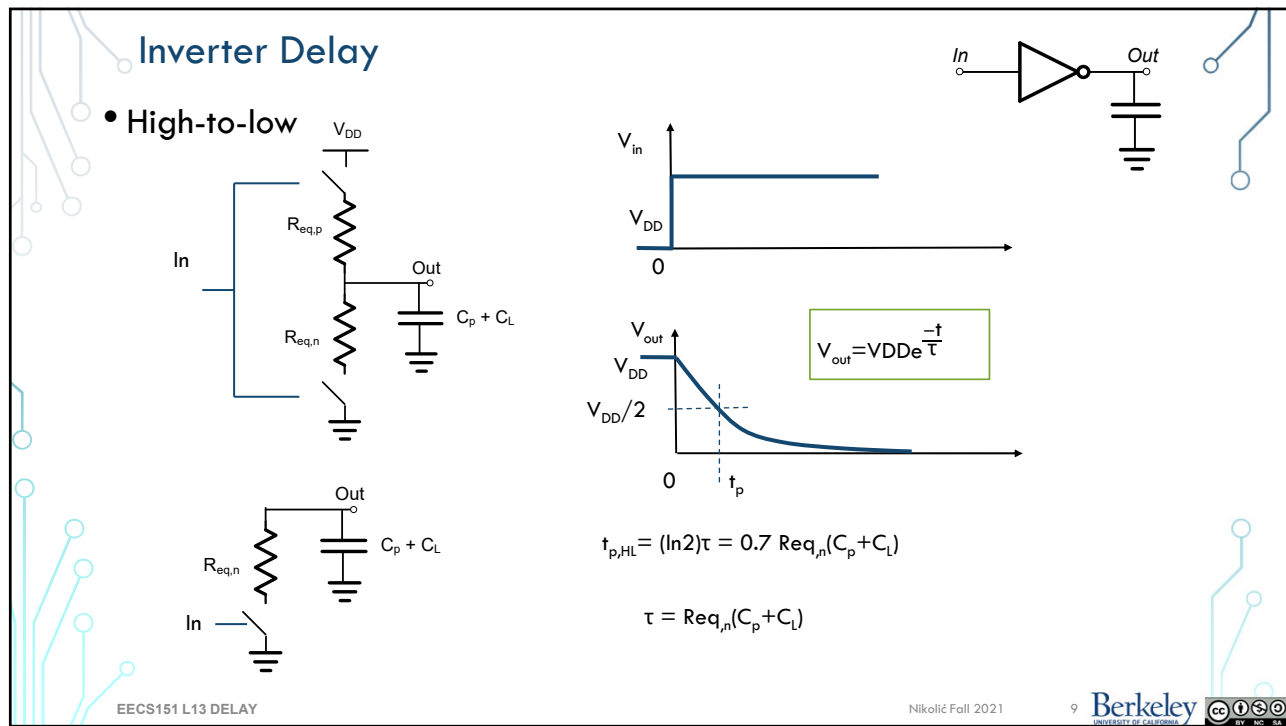


9

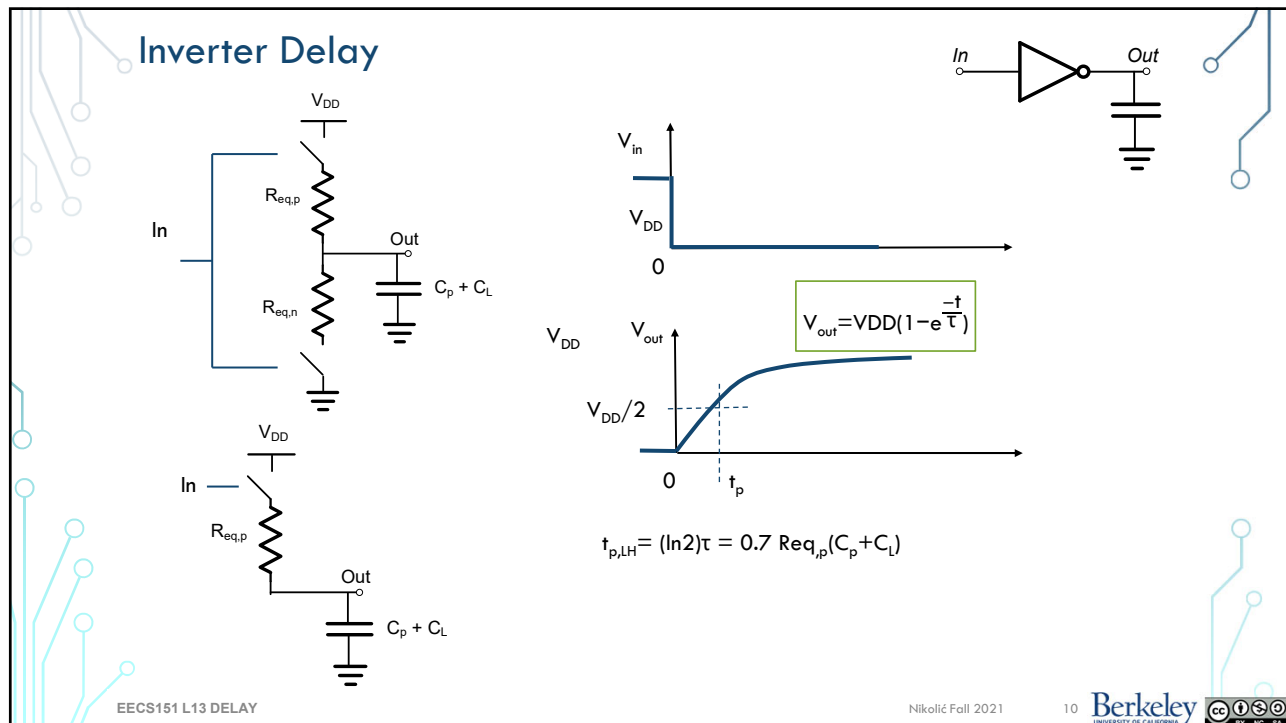

10

 

11

 

12


Optimal P/N Sizing

- Increasing W_p :

- Reduces R_p , increases $C_{in,p}$
- Reduces $t_{p,LH}$
- Increases $t_{p,HL}$

- Optimum

 - $W_p/W_n = 2$ in older technologies, with velocity saturation (like 130nm)
- $W_p/W_n = 1.6$ in technologies with strained silicon (e.g. 28nm)
- $W_p/W_n = 1$ in finFET technologies



EECS151 L13 DELAY

Nikolić Fall 2021




13



13

Impact of Rise/Fall times

- Impacts the $I_{DS}-V_{DS}$ trajectory

   

EECS151 L13 DELAY

Nikolić Fall 2021


14



14

Impact of Rise/Fall times


- Impacts the I_{DS} - V_{DS} trajectory

 

15

Impact of Supply Voltage


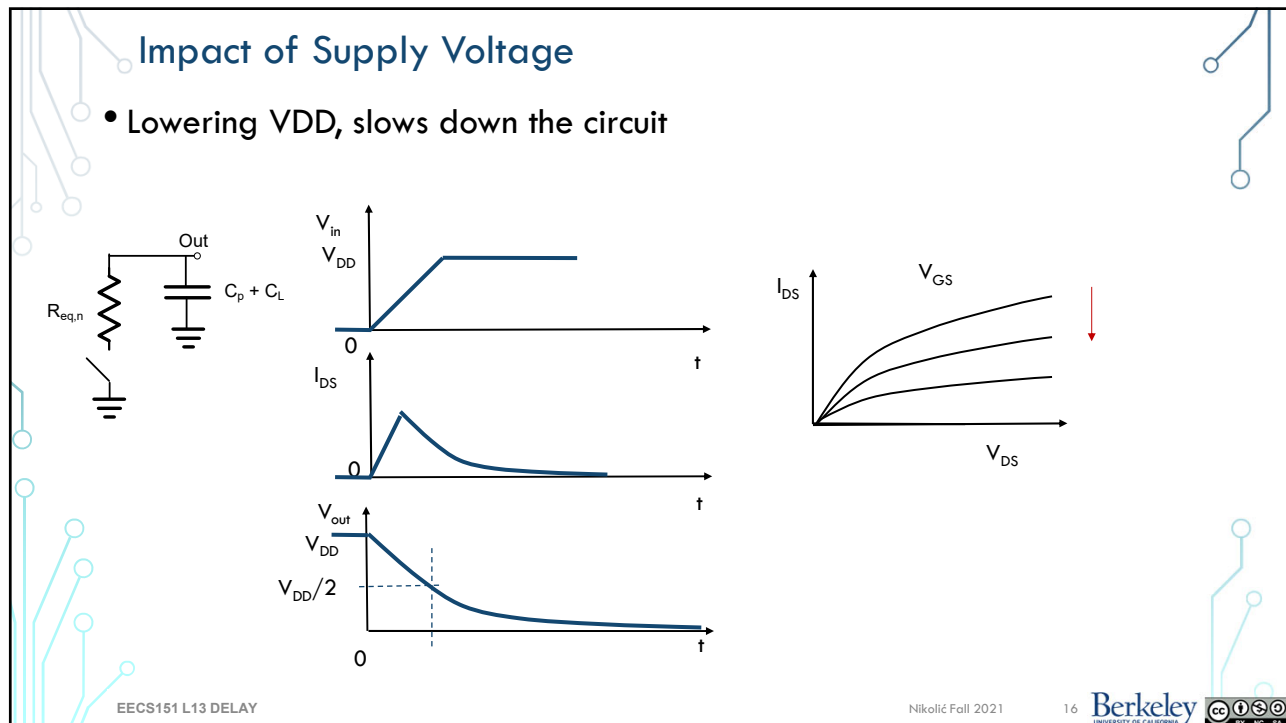
- Lowering V_{DD} , slows down the circuit



16

Quiz: Inverter Delay

  - If we double the load capacitance, assuming the default V_{out} shown in blue, which of the following waveforms shows the new V_{out} ?



EECS151 L13 DELAY

Nikolić Fall 2021

17 Berkeley



17



Sizing CMOS Gates

EECS151 L13 DELAY


Nikolić Fall 2021

18 Berkeley



18

Sizing for equal output resistance

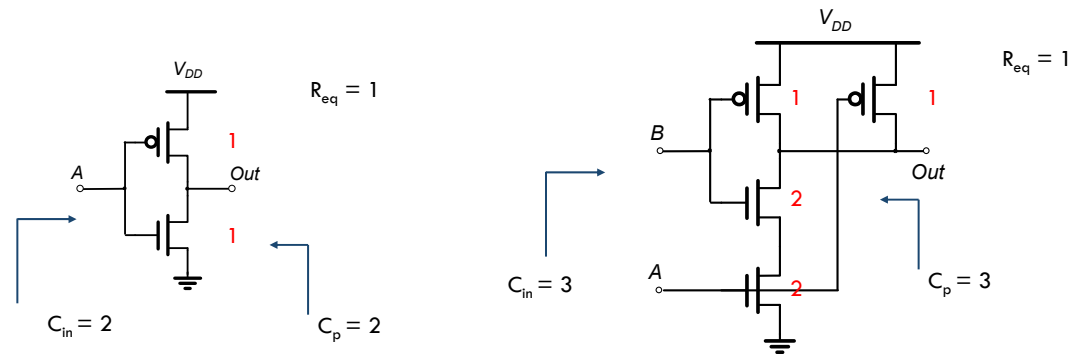

- In velocity-saturated devices I_{on} of a stack is $2/3$ (not a half) of two devices
 - So the correct upscaling factor is 1.5 (not 2)
- We will use 2, as it makes calculations easier

EECS151 L13 DELAY

Nikolić Fall 2021


19

Berkeley



19

Other Gates, NOR2, NAND3

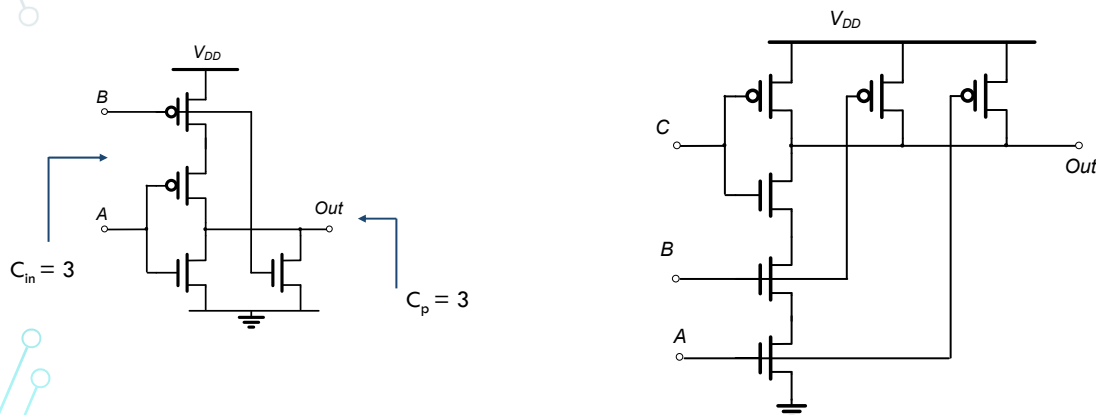

EECS151 L13 DELAY

Nikolić Fall 2021


20

Berkeley



20

Stack Ordering

 

- Critical path goes on top of stack

EECS151 L13 DELAY

Nikolić Fall 2021

21



21

Administrivia

- Homework 5 due this week
- Lab 6 (last) this week
- Projects start next week
- There is still time to apply for undergrad scholarships in SoC design!
- Have you thought about doing undergrad research?

EECS151 L13 DELAY

Nikolić Fall 2021

22



22



Minimizing Logic Delay


EECS151 L13 DELAY

Nikolić Fall 2021

23 Berkeley UNIVERSITY OF CALIFORNIA

23

Inverter RC Delay

 

- $t_p = R_{eq}(C_p + C_L) = R_{eq}(C_{in}/\gamma + C_L)$
 - $\gamma = 1$ (closer to 1.2 in recent processes)
- $t_p = R_{eq}C_{in}(1 + C_L/C_{in}) = \tau_{INV}(1 + f)$
 - Propagation delay is proportional to fanout
- Normalized Delay = $1 + f$

$$\text{Fanout} = f = C_L/C_{in}$$

$$t_p = \tau_{INV}(1 + f)$$

EECS151 L13 DELAY

Nikolić Fall 2021

24 Berkeley UNIVERSITY OF CALIFORNIA

24

Generalizing to Arbitrary Gates

- Delay has two components: $d = f + p$
- f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
- g : logical effort
 - Measures relative ability of gate to deliver current
 - $g = 1$ for inverter
- h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
- p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

EECS151 L13 DELAY


Nikolić Fall 2021

25



25

Inverter Delay

 

- Parasitic p is the ratio of intrinsic capacitance to an inverter
 - $p(\text{inverter}) =$
- Logical Effort g is the ratio of input capacitance to an inverter
 - $g(\text{inverter}) =$
- Electrical Effort h is the ratio of the load capacitance to the input capacitance
 - $h(\text{inverter}) =$
- Delay = $p + f = p + g * h = 1 + f$


EECS151 L13 DELAY

Nikolić Fall 2021


26



26

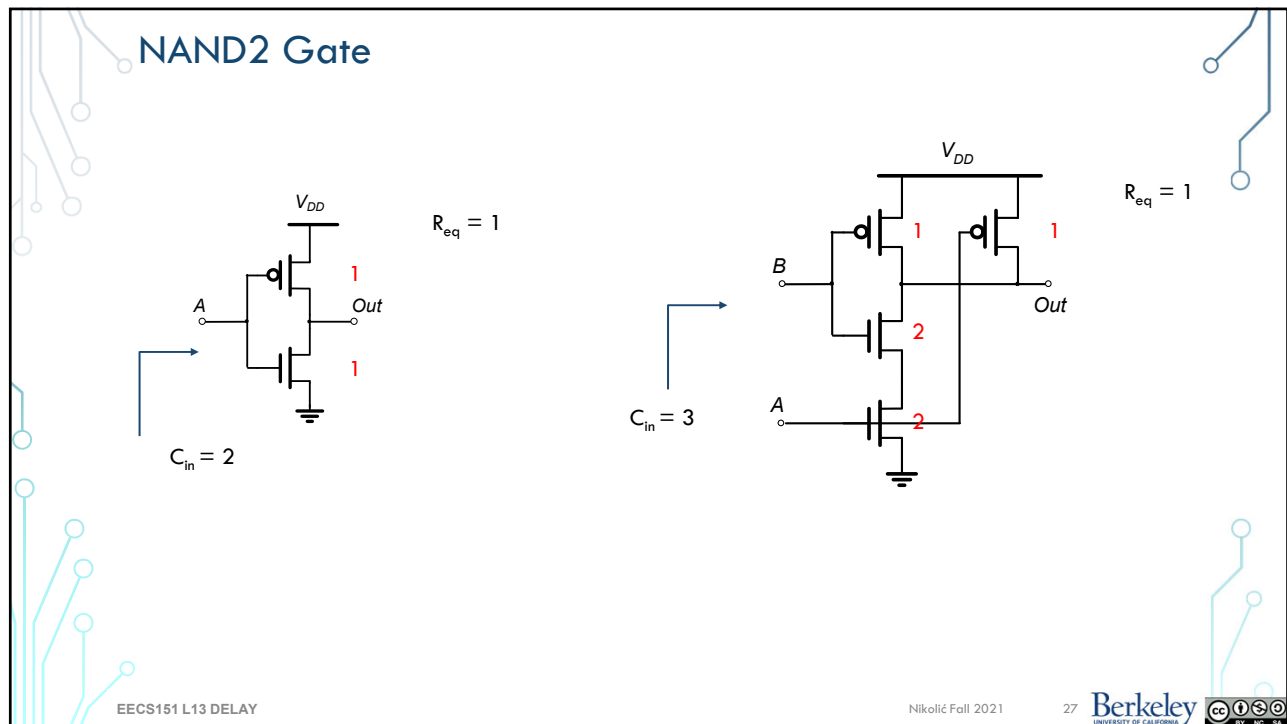

27

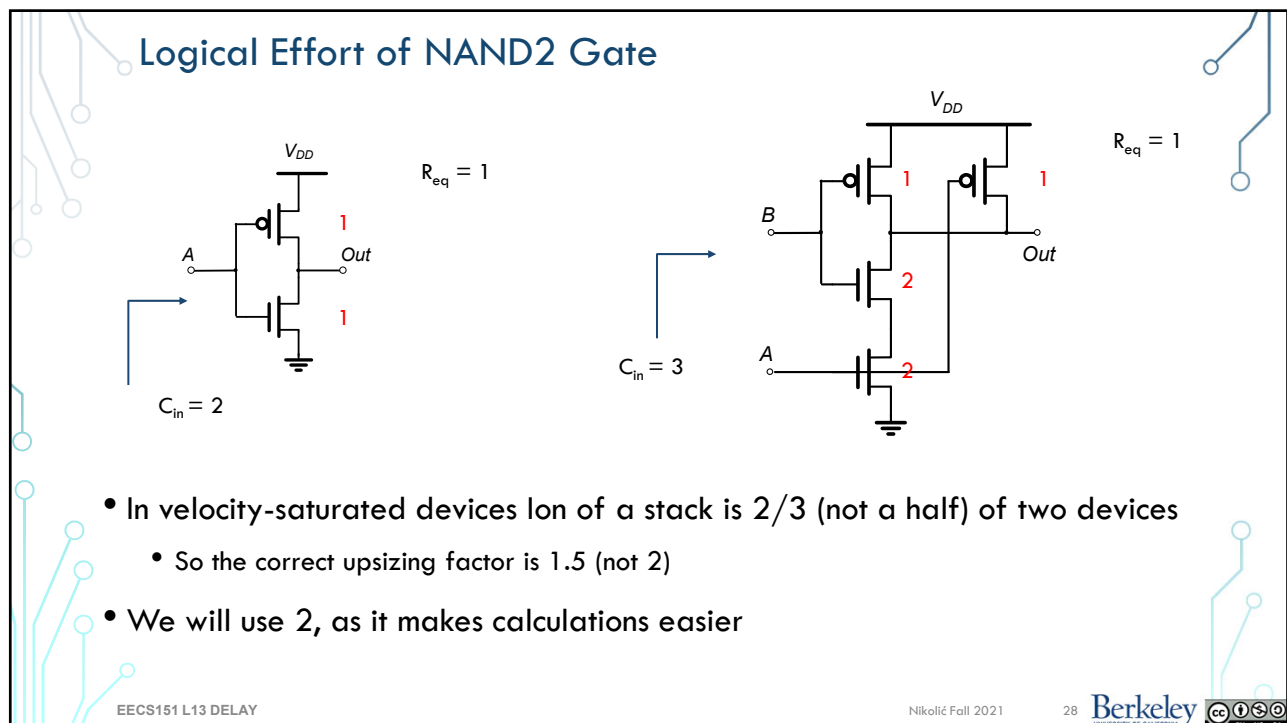

28

NOR2 Gate

$R_{eq} = 1$

$C_{in} = 2$

$C_{in} = 3$

EECS151 L13 DELAY

Nikolić Fall 2021

29 Berkeley UNIVERSITY OF CALIFORNIA

29

Example: Inverter Chain

Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

Total Delay: $d_{total} =$


EECS151 L13 DELAY

Nikolić Fall 2021

30 Berkeley UNIVERSITY OF CALIFORNIA

30

Example: Inverter Chain

 

Logical Effort: $g = 1$
 Electrical Effort: $h = 1$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = 2$
 Total Delay: $d_{\text{total}} = 2*N$

EECS151 L13 DELAY


Nikolić Fall 2021

31 Berkeley UNIVERSITY OF CALIFORNIA

31

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$


EECS151 L13 DELAY

Nikolić Fall 2021 Berkeley UNIVERSITY OF CALIFORNIA

32

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

EECS151 L13 DELAY

Nikolić Fall 2021



33


Multi-stage Logic Networks

- Logical effort generalizes to multistage networks

• *Path Logical Effort* $G = \prod g_i$

• *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 • *Path Effort* $F = \prod f_i = \prod g_i h_i$



EECS151 L13 DELAY

Nikolić Fall 2021

34



34

Branching Effect

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}} \quad B = \prod b_i$$

$$G = 1$$

$$H = 90 / 5 = 18$$


$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$B = 2$$

$$F = g_1 g_2 h_1 h_2 = 36 = BGH$$

 

EECS151 L13 DELAY

Nikolić Fall 2021

35

Berkeley



35

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

EECS151 L13 DELAY

Nikolić Fall 2021

36

Berkeley




36

Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

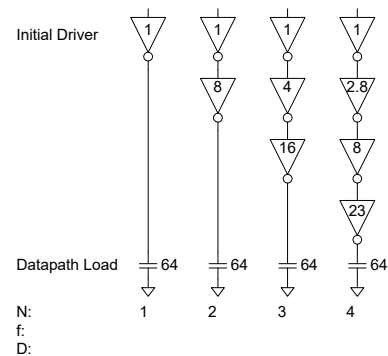

EECS151 L13 DELAY

Nikolić Fall 2021

37




37

Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

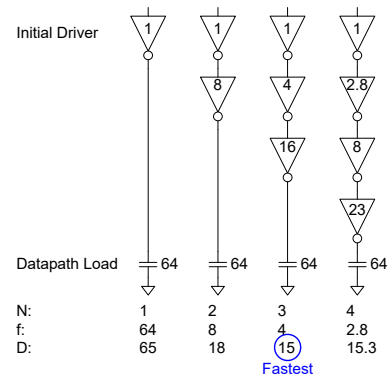

EECS151 L13 DELAY

Nikolić Fall 2021


38



38

Best Stage Effort

 - How many stages should a path use?
 - To drive given capacitance



- Define best stage effort
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = e = 2.718$
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$
- Choose 4 – less stages, less energy

EECS151 L13 DELAY

Nikolić Fall 2021

39



39

Logical Efforts Method

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

EECS151 L13 DELAY

Nikolić Fall 2021

40



40

Summary

- Delay is a linear function of R and C
- Delay optimization is critical to improve the frequency of the circuit.
- The dimensions of a transistor affect its capacitance and resistance.
- We use RC delay model to describe the delay of a circuit.
- Two delay components:
 - Parasitic delay (p)
 - Effort delay (F)
 - Logical effort (g): intrinsic complexity of the gate
 - Electrical effort (h): load capacitance dependent