 


# EECS 151/251A Homework 6

Due Friday, April 1<sup>st</sup>, 2022

## Problem 1: Not So Much Effort

Consider a NAND3 gate that drives one of the input of a NAND2 gate:




For this problem, assume you have a reference inverter with  $W_P = W_N = 1$  and  $R_p = R_n = R_{eq}$ . This technology has  $\gamma \equiv \frac{C_d}{C_g} = 1.5$ .

- Assume PMOS has unit size (“1”). Draw the transistor-level schematic for the circuit above and size all the NMOS transistors such that the equivalent delay of each gate without load is the same as a reference inverter.
- What is the Logical Effort of each gate? Show your steps.
- Now let the second NAND gate drive a load  $C_L$ . Assume the PMOS of the reference inverter has gate capacitance  $C_g$ . Write the delay from A to the output driving  $C_L$ .
 
## Problem 2: More Effort

Consider the following multi-stage network. The two inverters in the last stage are identical.



Again, assume you have a reference inverter with  $W_P = W_N = 1$  and  $R_p = R_n = R_{eq}$ . This technology has  $\gamma \equiv \frac{C_d}{C_g} = 1.5$ .

- (a) The input capacitance of A is  $C_{in}$  and the load  $C_L = 48 * C_{in}$ . Determine the path effort from A to the output load  $C_L$ .
- (b) Determine the optimum stage effort (SE) that results in minimum delay.
- (c) Express the minimum delay in terms of the intrinsic delay of the reference inverter,  $\tau_{inv}$ .
- (d) Based on your answers above, find the optimum input capacitance of the gates of each stage on the critical path.