



# EECS151 : Introduction to Digital Design and ICs

## Lecture 6 – Combinational Logic

Bora Nikolić



September 14, 2021. Apple announces A15

- Bionic processor
- 6 cores
- New GPU
- New neural engine
- ...

 


Image source: Apple

Nikolić, Fall 2021



### Review

- Sequential logic uses flip-flops and (sometimes) latches
- Flip-flops and latches are inferred in Verilog
  - Always blocks
- Practice is the best way to learn a new language...
- Blocking and non-blocking assignments



Nikolić, Fall 2021




### Combinational Logic


 
### Combinational Logic


- The outputs depend *\*only\** on the current values of the inputs.
- Memoryless: compute the output values using the current inputs.



Nikolić, Fall 2021



### Combinational Logic Example

 

Truth Table Description:

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


Boolean Equations:

$$\begin{aligned}\text{Out} &= A \text{ OR } B \\ &= A + B\end{aligned}$$

Gate Representations:



### Relationship Among Representations

 

Nikolić, Fall 2021




### Boolean Algebra


 
### Boolean Algebra Background

- Logic: The study of the principles of reasoning.
- The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
  - His variables took on TRUE, FALSE.
- Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits.



georgeboole.com  
Digitized by Google



<http://hdl.handle.net/1721.1/11173>



Nikolić, Fall 2021



## Boolean Algebra Fundamentals

- Two elements {0, 1}
- Two binary operators: AND ( $\cdot$ ) OR ( $+$ )
- One unary operator: NOT ( $'$ ,  $\neg$ )



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1



A	Out
0	1
1	0

## Axioms of Boolean Algebra

Axiom	Dual	Name
$B = 0 \text{ if } B \neq 1$	$B = 1 \text{ if } B \neq 0$	Binary field
$\overline{\overline{0}} = 1$	$\overline{\overline{1}} = 0$	NOT
$0 \cdot 0 = 0$	$1 + 1 = 1$	AND/OR
$1 \cdot 1 = 1$	$0 + 0 = 0$	AND/OR
$0 \cdot 1 = 0 \cdot 1 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

In mathematical logic, axioms are given  
Anything else can be derived from these axioms  
Each axiom has a dual

## Boolean Operations

- Given two variables (A, B), 16 logic functions

A	B	$F_0$	$F_1$	$F_2$	$F_3$	$F_4$	$F_5$	$F_6$	$F_7$	$F_8$	$F_9$	$F_{10}$	$F_{11}$	$F_{12}$	$F_{13}$	$F_{14}$	$F_{15}$
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

## Boolean Algebra Theorems

- Null elements, identities:
  - $A+0=A$ ,  $A \cdot 1=A$
  - $A+1=1$ ,  $A \cdot 0=0$
- Idempotency:
  - $A+A=A$ ,  $A \cdot A=A$
- Complements:
  - $A+A'=1$ ,  $A \cdot A'=0$
- Involution:
  - $(A')'=A$
- Commutativity:
  - $A+B=B+A$ ,  $A \cdot B=B \cdot A$
- Associativity:
  - $(A+B)+C=A+(B+C)=A+B+C$
  - $(A \cdot B) \cdot C=A \cdot (B \cdot C)=A \cdot B \cdot C$
- Distributivity:
  - $A \cdot (B+C)=(A \cdot B)+(A \cdot C)$
  - $A+(B \cdot C)=(A+B) \cdot (A+C)$
- Covering:
  - $A \cdot (A+B)=A$ ,  $A+(A \cdot B)=A$
- Consensus
  - $(A \cdot B)+(A' \cdot C)+(B \cdot C)=(A \cdot B)+(A' \cdot C)$

Literals are variables or their complements

## Proving Distributive Law

- $A \cdot (B+C) = (A \cdot B) + (A \cdot C)$

A	B	C	$(B+C)$	$A \cdot (B+C)$	$(A \cdot B)$	$(A \cdot C)$	$(A \cdot B) + (A \cdot C)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

## Proving Distributive Law


- $A \cdot (B+C) = (A \cdot B) + (A \cdot C)$

A	B	C	$(B+C)$	$A \cdot (B+C)$	$(A \cdot B)$	$(A \cdot C)$	$(A \cdot B) + (A \cdot C)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1


## DeMorgan's Law

- Theorem for complementing a complex function.

$$(A + B)' = A' \cdot B'$$

 

$$(A \cdot B)' = A' + B'$$

 


A	B	A'	B'	$(A+B)'$	$A' \cdot B'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

A	B	A'	B'	$(A \cdot B)'$	$A' + B'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0


## DeMorgan's Law

- Procedure for complementing a complex function.

$$(A + B)' = A' \cdot B'$$

 

$$(A \cdot B)' = A' + B'$$

 

A	B	A'	B'	$(A+B)'$	$A' \cdot B'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

A	B	A'	B'	$(A \cdot B)'$	$A' + B'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

## Canonical Forms

### Two types:

- Sum of Products (SOP)
- Product of Sums (POS)

### Sum of Products

- a.k.a Disjunctive normal form, minterm expansion
- Minterm: a product (AND) involving all inputs
- SOP: Summing minterms for which the output is True

Minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'b'c'	0	1	0	0	1
a'b'c	0	1	1	1	0
a'b'c'	1	0	0	1	0
a'b'c	1	0	1	1	0
a'b'c'	1	1	0	1	0
a'b'c	1	1	1	1	0

One product (and) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

## Sum of Products (cont.)

- Canonical Forms are usually not minimal:
- Example:

$$f = a'bc + ab'c' + ab'c + abc' + abc \quad (xy' + xy = x)$$

$$= a'bc + ab' + ab$$

$$= a'bc + a$$

$$= a + bc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

$$= a'b' + a'bc'$$

$$= a' (b' + bc')$$

$$= a' (b' + c')$$

$$= a'b' + a'c'$$

$$a + a'b = a + b$$

- Recall distributive theorem
- $$a+bc = (a+b)(a+c)$$

## Canonical Forms

### Two types:

- Sum of Products (SOP)
- Product of Sums (POS)

### Product of Sums:

- a.k.a. conjunctive normal form, maxterm expansion
- Maxterm: a sum (OR) involving all inputs
- POS: Product (AND) maxterms for which the output is FALSE
- Can obtain POSs from applying DeMorgan's law to the SOPs of F (and vice versa)

Maxterms	a	b	c	f	f'
a+b+c	0	0	0	0	1
a+b+c'	0	0	1	0	1
a+b'+c	0	1	0	0	1
a+b'+c'	0	1	1	1	0
a'+b+c	1	0	0	1	0
a'+b+c'	1	0	1	1	0
a'+b'+c	1	1	0	1	0
a'+b'+c'	1	1	1	1	0

One sum (or) term for each 0 in f:

$$f = (a+b+c)(a+b+c')(a+b'+c)$$

$$f' = (a+b'+c')(a'+b+c)(a'+b+c')$$

$$(a'+b'+c)(a+b+c')$$

## Quiz

- Derive the product-of-sums form of  $\bar{Y}$  based on the truth table.

$$a) \bar{Y} = (A + B)(A + \bar{B})$$

$$b) \bar{Y} = A\bar{B} + AB$$

$$c) \bar{Y} = \bar{A}\bar{B} + \bar{A}B$$

A	B	Y	$\bar{Y}$
0	0	0	1
0	1	0	1
1	0	1	0
1	1	1	0

## Boolean Simplification



## Example: Full Adder (FA) Carry out

$$co = a'bc + ab'c + abc' + abc$$

$$= a'bc + ab'c + abc' + abc + abc$$

$$= a'bc + abc + ab'c + abc' + abc$$

$$= (a' + a)bc + ab'c + abc' + abc$$

$$= (1)bc + ab'c + abc' + abc$$

$$= bc + ab'c + abc' + abc + abc$$

$$= bc + ab'c + abc + abc' + abc$$

$$= bc + a(b' + b)c + abc' + abc$$

$$= bc + a(1)c + abc' + abc$$

$$= bc + ac + ab(c' + c)$$

$$= bc + ac + ab(1)$$

$$= bc + ac + ab$$

c	b	c	s	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Why do Boolean simplification?

- Minimize number of gates in circuit
  - Gates take area
- Minimize amount of wiring in circuit
  - Wiring takes space and is difficult to route
  - Physical gates have limited number of inputs
- Minimize number of gate levels
  - Faster is better
- How to systematically simplify Boolean logics?
  - Use tools!

## Practical methods for Boolean simplification

- Still based on Boolean algebra, but more systematic
- 2-level simplification -> multilevel
- Key tool: The Uniting Theorem

$$ab' + ab = a(b' + b) = a(1) = a$$

ab	f
00	0
01	0
10	1
11	1

- b values change within rows
- a values don't change
- b is eliminated, a remains

$$f = ab' + ab = a(b' + b) = a$$

## Karnaugh Map Method

- K-map is an alternative method of representing the truth table and to help visual the adjacencies.

ab

a	0	1
b	0	1
c	0	1

cd

ab	00	01	11	10
00				
01				
11				
10				

Note: "Gray code" labeling.

ab	00	01	11	10
00				
01				
11				
10				

## Karnaugh Map Method

- Adjacent groups of 1's represent product terms

OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Karnaugh Map

	A	0	1
B	0	0	1
1	1	1	1

$$F = A + B$$

## Karnaugh Map Method

1. Draw K-map of the appropriate number of variables.
2. Fill in map with function values from truth table.
3. Form groups of 1's.
  - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
  - ✓ Form as large as possible groups and as few groups as possible.
  - ✓ Groups can overlap (this helps make larger groups)
  - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
  - The term includes the "constant" variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Karnaugh Map

	A	0	1
B	0	0	1
1	1	1	1

$$F = A + B$$

## Karnaugh Map Method

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = A + B$$

	A	0	1
BC	00	0	1
01	0	1	1
11	1	1	1
10	1	1	1

## Product-of-Sums Version

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
  - the term includes the "constant" variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.

ab

cd	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$


## Karnaugh Maps with Don't Cares

- Don't cares (x's) in the truth table can be either 0's or 1's

		AB			
		00	01	11	10
CD	00	1	1	X	1
	01	1	0	X	1
	11	1	1	X	X
	10	1	0	X	X
 
## Sequential logic

- Combinational logic:
  - Memoryless: the outputs only dependent on the current inputs.
- Sequential logic:
  - Memory: the outputs depend on both current and previous values of the inputs.
    - Distill the prior inputs into a smaller amount of information, i.e., states.
  - State: the information about a circuit
    - Influences the circuit's future behavior
    - Stored in Flip-flops and Latches
  - Finite State Machines:
    - Useful representation for designing sequential circuits
    - As with all sequential circuits: output depends on present and past inputs
    - We will first learn how to design by hand then how to implement in Verilog.




## Finite-State Machines


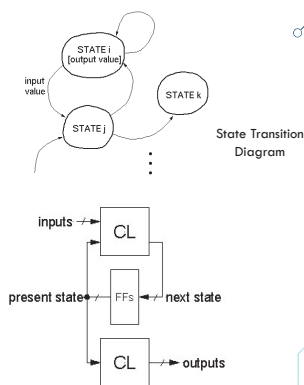
## Finite State Machines

- A sequential circuit which has
  - External inputs
  - Externally visible outputs
  - Internal states
- Consists of:
  - State register
    - Stores current state
    - Loads previously calculated next state
    - # of states  $\leq 2^{\text{# of FFs}}$
  - Combinational logic
    - Computes the next state
    - Computes the outputs



33 Berkeley

## FSM Example


- Cat Brain (Simplified...)
  - Inputs:
    - Feeding
    - Petting
  - Outputs:
    - Eyes: open or close
    - Mouth: open or close
  - States:
    - Eating
    - Sleeping
    - Annoyed...



34 Berkeley
 
## FSM State Transition Diagram


- States:
  - Circles
- Outputs:
  - Labeled in each state
- Inputs:
  - Arcs



35 Berkeley

## FSM Symbolic State Transition Table

Current State	Inputs	Next State
Eat	Feeding	Eat
Eat	Petting	Sleep
Sleep	Feeding	Sleep
Sleep	Petting	Annoyed
Annoyed	Feeding	Eat
Annoyed	Petting	Annoyed

 


36 Berkeley

## FSM Encoded State Transition Table

State	Encoding
Eat	00
Sleep	01
Annoyed	10

Current State		Input	Next State	
S1	S0	X	S1'	S0'
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0

 


Current State	Inputs	Next State
Eat	Feeding	Eat
Eat	Petting	Sleep
Sleep	Feeding	Sleep
Sleep	Petting	Annoyed
Annoyed	Feeding	Eat
Annoyed	Petting	Annoyed

37 Berkeley

## FSM Output Table

State	Encoding
Eat	00
Sleep	01
Annoyed	10

Current State		Outputs	
S1	S0	E	M
0	0	1	1
0	1	0	0
1	0	1	0

 

38 Berkeley

$$S0' = \overline{S1}S0X + \overline{S1}S0\overline{X} = \overline{S1}(S0X + S0\overline{X}) = \overline{S1}(S0 \oplus X)$$


$$S1' = \overline{S1}S0X + S1S0X = (S1 \oplus S0)X$$

Outputs		Encoding
Eyes	Mouth	
Open	Open	11
Close	Close	00
Open	Close	10

$$E = S1S0 + \overline{S1}S0 = S0$$

$$M = \overline{S1}S0$$

## FSM Gate Representation

 

$$S1' = X(S0 \oplus S1)$$

$$S0' = \overline{S1}(S0 \oplus X)$$

$$E = S0$$

$$M = \overline{S1}S0$$

39 Berkeley

## Summary

- Combinational logic:
  - The outputs only depend on the current values of the inputs (memoryless)
  - The functional specification of a combinational circuit can be expressed as:
    - A truth table
    - A Boolean equation
- Boolean algebra
  - Deal with variables that are either True or False
  - Map naturally to hardware logic gates
  - Use theorems of Boolean algebra and Karnaugh maps to simplify equations
- Finite state machines: Common example of sequential logic
- Common job interview questions ☺

40 Berkeley