

# EECS 151/251A

## SP2022 Discussion #2

---

GSI: DIMA NIKIFOROV, YIKUAN CHEN

# Agenda

---

- Administrivia
- More Verilog
- Testbenches
- Combinational Logic

# Administrivia

---

- Thoughts on hybrid instruction/labs?
- Homework 2 posted

# More Verilog

---

# Blocking vs. Nonblocking

---

## Blocking:


```
reg c, out;
wire a, b, d;
always @(*) begin
    c = a | b;
    out = c & d;
end
```

## Non-Blocking:

```
reg c, out;
wire a, b, clk;
always @(posedge clk) begin
    //use val of 'out' before clk edge
    c <= out | a;
    //use val of 'c' before clk edge
    out <= c & b;
end
```

- Don't mix blocking and nonblocking!
- When would you use either one?
 
# Race Conditions: Synthesis vs. Simulation



Want: a register pipeline

Determine:

1. Does it *synthesize* correctly?
2. Does it *simulate* correctly?
  - Note: always blocks may simulate in any order
3. Is it good coding practice?

Candidate #1:

```
always @(posedge clk) begin
    q1 = d;
    q2 = q1;
    q3 = q2;
end
```

Candidate #4:

```
always @(posedge clk) q1 = d;
always @(posedge clk) q2 = q1;
always @(posedge clk) q3 = q2;
```

Candidate #2:

```
always @(posedge clk) begin
    q3 = q2;
    q2 = q1;
    q1 = d;
end
```

Candidate #5:

```
always @(posedge clk) q3 = q2;
always @(posedge clk) q2 = q1;
always @(posedge clk) q1 = d;
```

Candidate #3:

```
always @(posedge clk) begin
    q1 <= d;
    q2 <= q1;
    q3 <= q2;
end
```

Candidate #6:

```
always @(posedge clk) q1 <= d;
always @(posedge clk) q2 <= q1;
always @(posedge clk) q3 <= q2;
```


# Testbenches

---
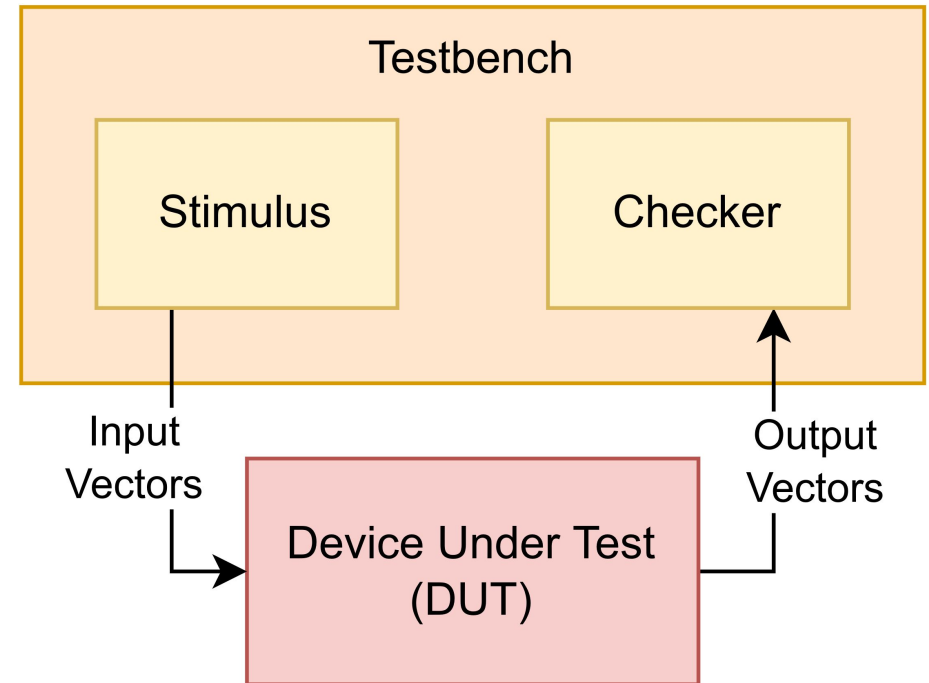
# What's a Testbench?

---

- Tool to verify that design behaves as specified
- Generate inputs to drive design
- Compare outputs against expected results





# Example Testbench

---

```
`timescale 1 ns / 1 ps

module my_tb();

    reg tb_in;
    wire tb_out;
    reg tb_clk;

    integer i=0;

    initial clk = 0;
    always #(`CLOCK_PERIOD/2) clk <= ~clk;

    my_module dut (.clk(tb_clk), .in(tb_in), .out(tb_out));

    initial begin
        // Drive inputs and check here
    end

endmodule
```

# What Makes a Good Testbench?

- Code coverage:
  - Statements
  - Branches
  - Toggles
  - States
- Functional coverage
  - Features/Requirements





```
module adder (  
    input signed [63:0] A,  
    input signed [63:0] B,  
    output signed [63:0] Y,  
    output zero, negative  
);  
always @(*) begin  
    Y = A + B;  
    negative = Y[63];  
    if (Y == 64'b0) begin  
        zero = 1'b1;  
    end else begin  
        zero = 1'b0;  
    end  
end  
  
endmodule
```

# Combinational Logic

---
    
# Boolean Algebra: DeMorgan's

- First step towards logic simplification
- Recall:  $(x+y)' = x'y'$  ,  $(xy)' = x'+y'$
- Bubble = inversion (NOT)
- Steps for a single gate:
  1. Swap AND for OR & vice versa
  2. Backward pushing: add bubbles to inputs
  3. Forward pushing: add bubbles to output




# Canonical Forms

---


- Sum of Products (SoP):

 - $\bar{B}C + A\bar{B} + \bar{A}B\bar{C}$




- Sum of Products (SoP):

 - $(\bar{B} + \bar{C})(\bar{A} + \bar{B})(A + B + C')$



# Truth Tables

---

 

<i><b>A</b></i>	<i><b>B</b></i>	<i><b>C</b></i>	<i><b>Out</b></i>
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Truth Tables

A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


SoP

PoS

# 2-input K-Map

---

$$F(A,B) = \bar{A}B + AB + A\bar{B}$$

 



 
# 4-input K-Map

---

$$\begin{aligned} F(A,B) = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}c\bar{D} \\ & + \\ & \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \\ & AB\bar{C}\bar{D} + ABC\bar{D} + \\ & A\bar{B}CD + A\bar{B}\bar{C}\bar{D} + \\ & ABCD \end{aligned}$$



# Questions?

---