




EECS151 : Introduction to Digital Design and ICs

Lecture 11 – CMOS

Bora Nikolić

Intel Unveils Second-Generation Neuromorphic Chip

October 5, 2021, Intel has unveiled its second-generation neuromorphic computing chip, Loihi 2, the first chip to be built on its Intel 4 process technology. Designed for research into cutting-edge neuromorphic neural networks, Loihi 2 brings a range of improvements. They include a new instruction set for neurons that provides more programmability, allowing spikes to have integer values beyond just 1 and 0, and the ability to scale into three-dimensional meshes of chips for larger systems.

 

Intel's Loihi 2 second-generation neuromorphic processor. (Source: Intel)

EETimes

Nikolić, Fall 2021

1 Berkeley

EECS151 L12 CMOS2

Review

- Core FPGA building blocks:
 - Configurable Logic Blocks (CLBs)
 - Configurable Interconnect
 - Switch boxes
- Modern FPGA Designs:
 - BRAMs, DSPs, and AI Engines
- CMOS process is used for producing chips
 - Planar bulk process used up to 28nm node
 - finFET and FDSOI used below the 22nm node

EECS151 L12 CMOS2

Nikolić, Fall 2021


2 Berkeley

MOS Transistors





MOS Transistors

Symbol

 


P-type

PMOS

  

 - Devices are symmetrical
 - NMOS: Drain is at higher voltage
 - PMOS: Source is at higher voltage



EECS151 L12 CMOS2

Hibiki, Fall 2021



3 Berkeley

Hibiki, Fall 2021



4 Berkeley

Different Kinds of MOS Transistors

Planar bulk CMOS

  

FinFET

  

Intel 10nm IEDM 2017

EECS151 L12 CMOS2

Hibiki, Fall 2021

5 Berkeley

Transistor Dimensions are Quantized

- FinFET widths are discrete ($W = kW_{\text{unit}}$)
 - k is an integer
- Lengths are quantized because of lithography
 - Also are quantized lower metal layers, contacts...



EECS151 L12 CMOS2

Hibiki, Fall 2021


6 Berkeley

Ohm's Law

Resistors

  

Physical resistors

 


$$R = \rho \frac{L}{TW}$$


- In a planar process, designer controls W and L

Series and Parallel


With two identical resistors, R

 

Equivalent to doubling length

 

Equivalent to doubling width

 

EECS151 L12 CMOS2


Hibiki, Fall 2021

7 Berkeley


Hibiki, Fall 2021

8 Berkeley

An n-Channel MOS Transistor

 


 Polysilicon gate, dielectric, and substrate form a capacitor.
When $V_{GS} < V_{Th}$ transistor is off




$V_{DS} > 0$, transistor leaks
 $I_{DS} \sim nA$

An n-Channel MOS Transistor

 


When $V_{GS} < V_{Th}$ transistor is off


 


$V_G > V_{Th}$ small region near the surface turns from p-type to n-type.
nFet is on.
Current is proportional to V_{DS}


An n-Channel MOS Transistor

 

V_{DS} and V_{GS} change I_{DS}

  

 $V_{GS} < V_{Th}$ transistor saturates
($V_{DS} > V_{GS} - V_{Th}$)




MOS Transistors



• NMOS Transistor I-V characteristics





Old transistor

 

~7nm transistor

  

  
Nearly linear
 $I_{DS} \sim K(V_{GS} - V_{Th})$




Variable resistor!

Velocity Saturation

 • Carrier velocity in the channel saturates



 - All submicron transistors are velocity saturated
- Other effects (drain-induced barrier lowering) cause I_{DS} to increase in saturation



Administrivia

- Homework 5 will be posted later this week, due next week
- No lab this week
 - Lab 6 (last) after the midterm
- Midterm 1 on October 7, 7-8:30pm
 - You will be assigned a classroom
 - One double-sided page of notes allowed
 - Material includes FPGAs



MOS Transistor as a Switch



MOS Transistor as a Resistive Switch


MOS Transistor

A Switch!

  


- V_{GS} controls the switch
- (it also charges the channel capacitor)

ON/OFF Switch Model of MOS Transistor


 


A More Realistic Model

 


• It is a dimmer!

A Logic Perspective

  

AND and OR


• AND

 

$$F = AB$$

$$(F = AB + \bar{A} \cdot 0)$$

• OR

 

$$F = A+B$$

$$(F = A \cdot 1 + \bar{A}B)$$


• Keep in mind – single NMOS/PMOS transistors are imperfect switches!

• Turns off when $|V_{GS}| = |V_{Th}|$

Peer Instruction

• Switch logic

 • Which combination of inputs implements $F = AB$?



	R1	R2	R3	R4
a)	1	X	X	X
b)	0	X	X	X
c)	1	0	0	0
d)	1	1	1	0
e)	1	1	1	1
f)	None of the above			

Summary

• CMOS process is used for producing chips

• Planar bulk process used up to 28nm node

• finFET, FDSOI used below the 22nm node