



EECS151 : Introduction to Digital Design and ICs

Lecture 17 – Energy, Adders

Bora Nikolić

Brain implant bypasses the eyes to help blind users "see" images
 October 20, 2021, NewAtlas - While there are already eye implants that allow the blind to see simple patterns, Spanish scientists have recently had success with a different approach. They bypassed the eyes, producing perceivable images by directly stimulating the brain's visual cortex. The experimental system incorporates a forward-facing "artificial retina" mounted on an ordinary pair of glasses worn by the user. That device detects light from the visual field in front of the glasses, and converts it to electrical signals which are transmitted to a three-dimensional matrix of 96 micro-electrodes implanted in the user's brain.



The implanted intracortical microelectrode array allowed a blind test subject to perceive letters and silhouettes of shapes
 Association RUVID
 Nikolic Fall 2021

EECS151 L17 ADDERS



Review

- Wire contributes to delay, especially in modern technology
- We can use RC model to capture wire delays
- Energy becomes an increasingly important optimization goal
 - Dynamic energy
 - Static energy

EECS151 L17 ADDERS

Nikolic Fall 2021



Dynamic Power




Charging and Discharging a Capacitor

- When the gate output rises
 - Energy stored in capacitor is $E_C = \frac{1}{2} C_L V_{DD}^2$
 - But energy drawn from the supply is

$$E_{TDD} = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt$$

$$= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2$$

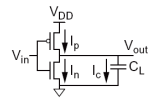- Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor
- When the gate output transitions HL
 - Energy in capacitor is dumped to GND
 - Dissipated as heat in the NMOS transistor



EECS151 L17 ADDERS

Nikolic Fall 2021



Dynamic Power Reduction


How can we limit switching power?

- Try to minimize:
 - Activity factor
 - Capacitance
 - Supply voltage
 - Frequency

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Reduce Activity Factor

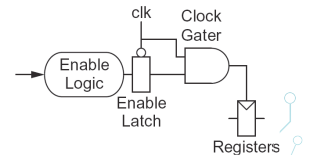- Clock gating
 - The best way to reduce the activity is to turn off the clock to registers in inactive blocks
 - Saves clock activity (clock $\alpha = 1$)
 - Eliminates all switching activity in the block
 - Requires determining if block will be used



EECS151 L17 ADDERS

Nikolic Fall 2021




Reduce Capacitance

- Gate capacitance
 - Fewer stages of logic
 - Smaller gate sizes
- Wire capacitance
 - Good floorplanning to keep communicating blocks close to each other

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Reduce Voltage/Frequency

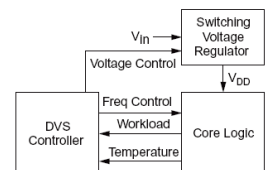- Run each block at the lowest possible voltage and frequency that meets performance requirements
- Voltage domains
 - Provide separate supplies to different blocks
- Dynamic voltage/frequency scaling
 - Adjust V_{DD} and f according to workload



EECS151 L17 ADDERS



Nikolic Fall 2021



Leakage Power



Subthreshold Leakage

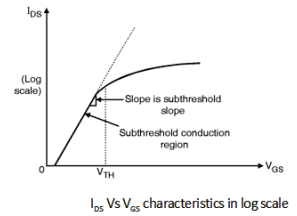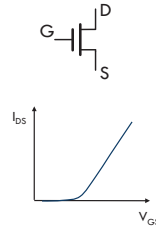

EECS151 L17 ADDERS

Nikolic Fall 2021



EECS151 L17 ADDERS

Nikolic Fall 2021




Power Gating

- Turn OFF power to blocks when they are idle to save leakage

- Use virtual V_{DD} (V_{DDV})
- Gate outputs to prevent invalid logic levels to next block

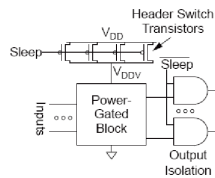- Voltage drop across sleep transistor degrades performance during normal operation
 - Size the transistor wide enough to minimize impact
- Switching wide sleep transistor costs dynamic power
 - Only justified when circuit sleeps long enough



Example: Power Management

- Power states

	C0 HFM	C0 LFM	C1/C2	C4	C6
Core Voltage	ON	ON	ON	ON	ON
Core Clock	ON	ON	OFF	OFF	OFF
PLL	ON	ON	ON	OFF	OFF
L1 Caches	ON	ON	Flushed	Flushed	OFF
L2 Caches	ON	ON	ON	Partial Flush	OFF
Wake-Up Time	active	active	< 1 μ s	< 30 μ s	< 100 μ s
Power	ON	ON	ON	ON	ON

Administrivia

- Homework 7 due this week
 - No new homework next week
- All labs need to be checked off by this week!
- Projects (ASIC and FPGA) started
- Midterm 2 is on November 4 at 7pm
 - Review session this Wednesday at 7pm




Binary Adders

Binary Adder


- Adders
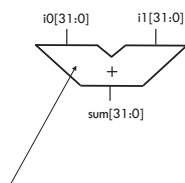
```
module add32(i0,i1,sum);
input [31:0] i0,i1;
output [31:0] sum;
assign sum = i0 + i1;
endmodule
```



What's inside?
Depends on:
- Performance/power requirements
- Number of bits

Single-Bit Full-Adder

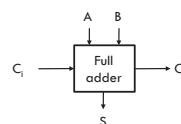

A	B	C_{in}	C_o	S	Carry Status
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Carry status = {generate, propagate, delete}

EECS151 L17 ADDERS

Nikolic Fall 2021




EECS151 L17 ADDERS

Nikolic Fall 2021



Single-Bit Full Adder

- Logic equations

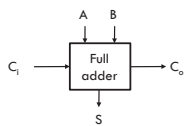

$$S = A \oplus B \oplus C_i$$

$$S = A \bar{B} \bar{C}_i + \bar{A} B \bar{C}_i + \bar{A} \bar{B} C_i + A B C_i$$

$$C_o = A B + B C_i + A C_i$$


Static CMOS Full Adder

- Direct mapping of logic equations

$$C_o = A B + B C_i + A C_i$$

$$\bar{C}_o = \bar{A} \bar{B} + \bar{C}_i (\bar{A} + \bar{B})$$
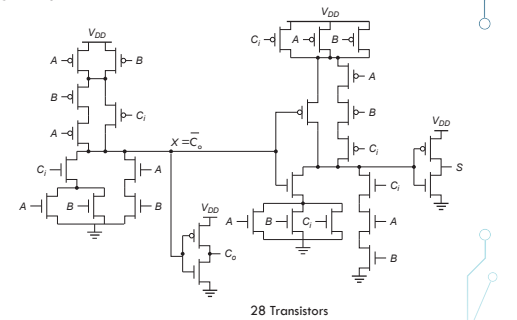
$$S = A B C_i + (A + B + C_i) \bar{C}_o$$



28 Transistors

Express Sum and Carry as a function of P, G, D

- Define generate, propagate and delete as functions of A, B

- Will use two at a time

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A + B \text{ (or } A \oplus B)$$

$$\text{Delete} = \bar{A} \bar{B}$$


$$C_o = A B + B C_i + A C_i = G + P C_i$$

Can also derive expressions for C_o based on D and P

A	B	C_m	G	P	K	C_o	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	X	0	1	0
		1				1	1

The Ripple-Carry Adder

- 4-bit adder

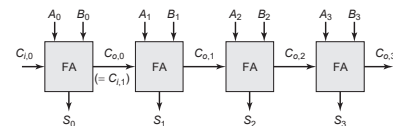


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit


Inversion Property

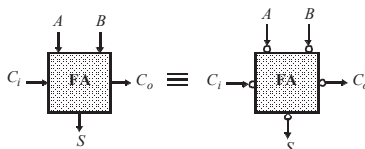

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

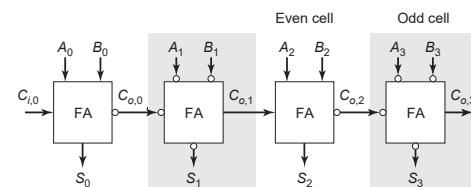Minimize Critical Path by Reducing Inverting Stages




Exploit Inversion Property

A Better Structure: The Mirror Adder

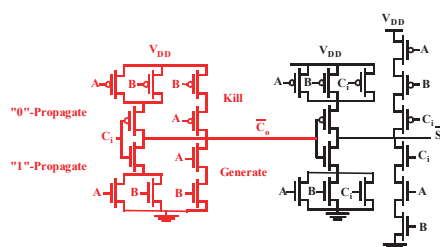

24 transistors

Sizing the Mirror Adder

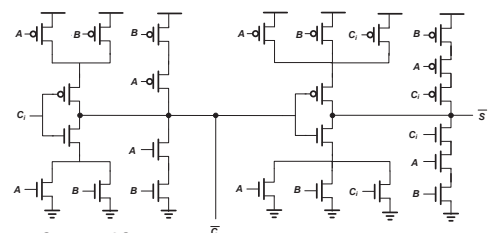

$$C_{\text{load}} = C_{C_i} + x = 2C_{C_i}$$



$$\rightarrow C_{C_i} =$$

- Reduce size of Generate and Delete stacks to reduce diffusion loading

The Mirror Adder

- The NMOS and PMOS chains are **completely symmetrical**.
A maximum of two series transistors in the carry-generation stack.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be smaller.
- The transistors connected to C_i are placed closest to the output.
- Minimize the capacitance at node C_o .


Transmission Gate Full Adder

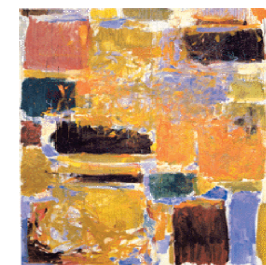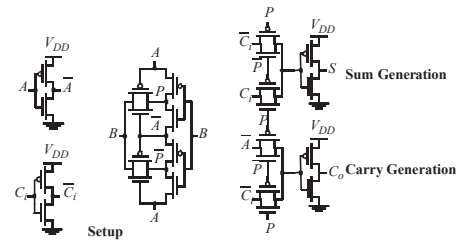

Carry Bypass Adders


Carry-Bypass Adder

- Also called 'carry skip'

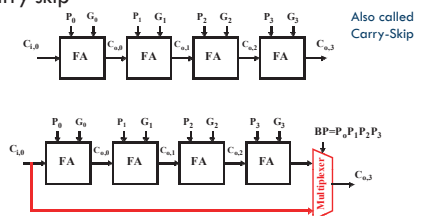


Idea: If $(P_0 \text{ and } P_1 \text{ and } P_2 \text{ and } P_3 = 1)$ then $C_{o3} = C_{i0}$, else "kill" or "generate".

Carry-Bypass Adder (cont.)

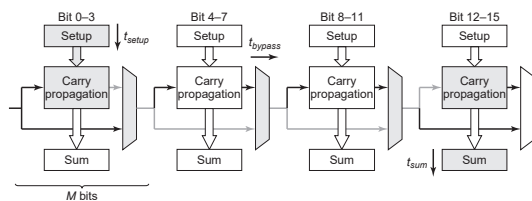


$$t_{\text{adder}} = t_{\text{setup}} + M_{\text{carry}} + (N/M-1)t_{\text{bypass}} + (M-1)t_{\text{carry}} + t_{\text{sum}}$$

Carry Ripple versus Carry Bypass

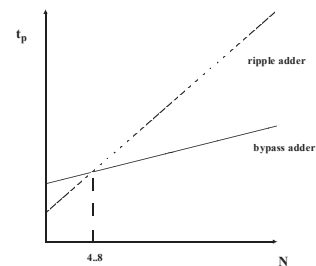

- Depends on technology, design constraints

To Design a Faster Carry-Bypass Adder

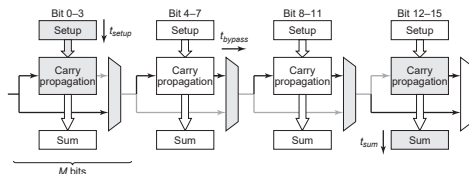

Faster Carry-Bypass


- Uniform groups of 4 are optimal
- Uniform groups >4 are optimal
- Uniform groups <4 are optimal
- Increasing group size with higher bit position
- Wider groups around mid bit positions are optimal

www.yellkey.com/cover




Carry-Select Adders


Carry-Select Adder

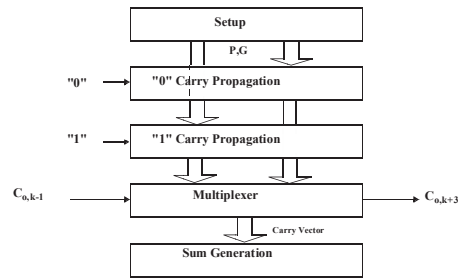

Carry Select Adder: Critical Path

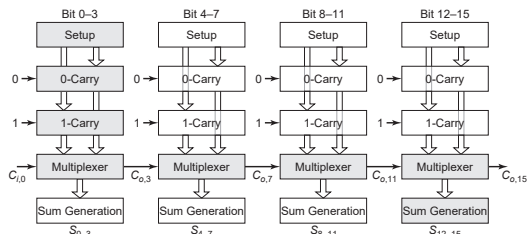


Linear Carry Select

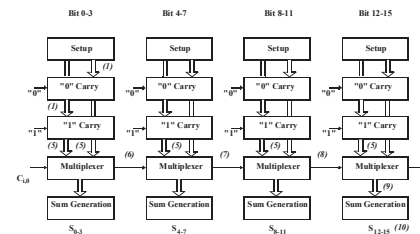


$$t_{add} = t_{setup} + \frac{(N)}{M} t_{carry} + M t_{mux} + t_{sum}$$

Square Root Carry Select

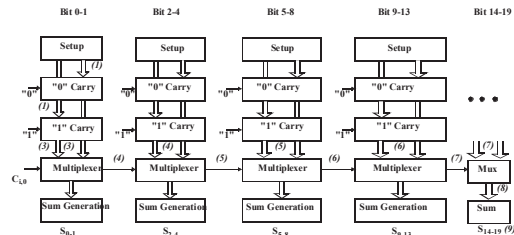

$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N}) t_{mux} + t_{sum}$$

Adder Delays - Comparison

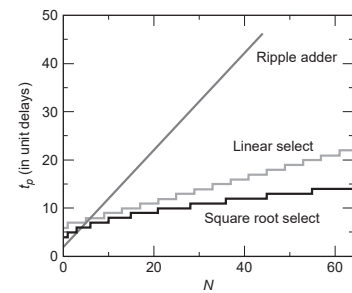

Summary

- Binary adders are a common building block of digital systems
- Carry is in the critical path
- Mirror adders cells are commonly found in libraries
- Ripple-carry adder is the least complex, lowest energy
- Carry-bypass, carry-select are usually faster than ripple-carry for bitwidths > 8