




## EECS151 : Introduction to Digital Design and ICs

## Lecture 13 – CMOS Logic

Bora Nikolić
 
## Qualcomm Takes on Nvidia for MLPerf Inference Title

October 1, 2021, EETimes, Sally Ward-Foxton - The latest round of MLPerf AI inference benchmark scores are in. Nvidia has dominated both MLPerf training and inference results since the beginning, but in this round Qualcomm appears to be close on Nvidia's tail when it comes to data center/edge server inference.



Qualcomm Cloud AI100 PCIe and M.2 cards (Source: Qualcomm)

EETimes

Nikolić Fall 2021

1 Berkeley

## Review

- CMOS process is used for producing chips
  - Planar bulk process used up to 28nm node
  - finFET, FDSOI used below the 22nm node
- Switch-level abstraction for MOS transistors

EECS151 L12 CMOS2





Nikolić Fall 2021

2 Berkeley

## MOS Switch



## MOS Switch

    

EECS151 L12 CMOS2

Nikolić Fall 2021

3 Berkeley

EECS151 L12 CMOS2

Nikolić Fall 2021



4 Berkeley

## CMOS Inverter



## CMOS Inverter

- Simple DC behavior
  - Schematic

  

• Switch model

$$V_{OL} = 0$$

$$V_{OH} = V_{DD}$$

EECS151 L12 CMOS2

Nikolić Fall 2021


5 Berkeley

EECS151 L12 CMOS2

Nikolić Fall 2021

6 Berkeley


## Voltage Transfer Characteristic (VTC)

 



$$V_A = V_{GS,n} = V_{DD} - V_{SG,p}$$

$$I_{DS,n} = I_{SD,p}$$
 
$$V_{Out} = V_{DS,n} = V_{DD} - V_{SD,p}$$



## Voltage Transfer Characteristic (VTC)

  

- Can we change switching point ( $V_A$  for which  $V_{out} = V_{DD}/2$ )?

EECS151 L12 CMOS2

Nikolić Fall 2021

7 Berkeley

EECS151 L12 CMOS2

Nikolić Fall 2021

8 Berkeley


## Digital Circuits

- One logic representation
- Multiple libraries
- Layouts
  - Number of metal 'tracks'
  - More tracks, faster, but larger
  - Less tracks – more compact, but slower
- Transistor thresholds ( $V_{Th}$ ) (for each track height):
  - Regular (RVT)
  - Low (LVT)
    - Faster, higher power
    - Slower, lower power
  - High (HVT)
- Transistor lengths

Out =  $\bar{A}$


Truth table

A	Out
0	1
1	0

 
 
## Administrivia


- Homework 5 due this week
- Lab 6 (last) this week
- Projects start next week



## CMOS Logic

## Building logic from switches


Series

 

AND

$Y = X$  if A AND B

Parallel

 

OR

$Y = X$  if A OR B

(output undefined if condition not true)

## Logic using inverting switches


Series



NOR

$Y = X$  if  $\bar{A}$  AND  $\bar{B}$   
 $= \overline{A + B}$

Parallel

 


NAND


$Y = X$  if  $\bar{A}$  OR  $\bar{B}$   
 $= \overline{AB}$

(output undefined if condition not true)

## Static Complementary CMOS

 

 PUN and PDN are **dual** logic networks  
PUN and PDN functions are **complementary**




## Complementary CMOS Logic Style

- PUN is the **dual** to PDN (can be shown using DeMorgan's Theorems)

$$\overline{A + B} = \bar{A} \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$


- Static CMOS gates are always inverting

 

## Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


- PDN:  $G = AB \Rightarrow$  Conduction to GND
- PUN:  $F = \bar{A} + \bar{B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$
- $G(\ln_1, \ln_2, \ln_3, \dots) \equiv \overline{F(\ln_1, \ln_2, \ln_3, \dots)}$

## Example Gate: NOR


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of a 2 input NOR gate

 

## Complex CMOS Gate


$$OUT = D + A \cdot (B + C)$$

 


- Note: In scaled processes max #inputs is 3-4
- Max stack height is 2 or 3
 
## Stick Diagrams


Contains no dimensions  
Represents relative positions of transistors




## Stick Diagrams

 


## Two Versions of $C \cdot (A + B)$

 


## Consistent Euler Path

 


## OAI22 Logic Graph

 

## Example: $x = \overline{ab+cd}$

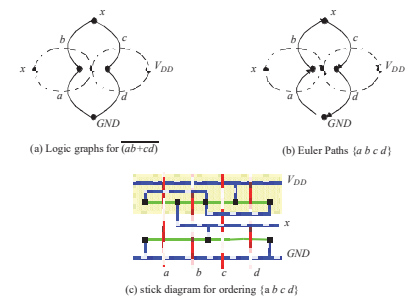


## Switch Limitations

 


 
## Transmission Gate

- Transmission gates are the way to build "switches" in CMOS.
- In general, both transistor types are needed:
  - nFET to pass zeros.
  - pFET to pass ones.
- The transmission gate is 'non-isolating'.



## Transmission-Gate Multiplexer

- Implementation

  

## CMOS Multiplexer

Sel	Y
0	A
1	B

Sel	Y
0	A
1	B

```


module comb(input a, b, sel,
            output reg y);
    always @(*) begin
        case (sel)
            1b'0: y <= a;
            1b'1: y <= b;
        endcase
    end
endmodule
    
```

## CMOS Sizing



## Transistor Sizing


- Optimal  $W_p/W_n$

 

- In the past,  $W_p > W_n$  (see Rabaey, 2<sup>nd</sup> ed)
- In modern processes (finFET),  $W_p = W_n$

 
## Gate Sizing

- Doubling the gate size (by doubling  $W_s$ ):




- Doubles  $C_{in}$
- Halves equivalent gate resistance
- Doubles  $C_p$

## CMOS Delay


 


## Inverter Delay

- How to time this?


 


  - Each gate has an  $R_{eq}$  and drives  $C_{in}$  of the next gate



## Inverter Delay



- High-to-low

  

$$t_{p,HL} = (\ln 2) \tau = 0.7 R_{eq,n} (C_p + C_L)$$


$$\tau = R_{eq,n} (C_p + C_L)$$

## Inverter Delay

  

$$t_{p,LH} = (\ln 2) \tau = 0.7 R_{eq,p} (C_p + C_L)$$

## Capacitances

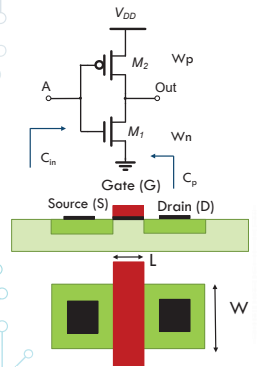

- $C_{in}$  is largely set by the gate cap

- $\sim WL$
- $2xW = 2xC_{in}$
- It is non-linear, but we will ignore that


- $C_p$  is largely set by the drain cap

- $\sim W$  (drain area/perimeter)
- $2xW = 2xC_p$

$$C_p = \gamma C_{in}$$

 
## Equivalent Resistances

- Transistor  $I_{DS}-V_{DS}$  trajectory
- Averaging produces  $R_{eq}$


 
## Equivalent Resistances


- Transistor  $I_{DS}-V_{DS}$  trajectory
- Averaging produces  $R_{eq}$



$$R_{eq} = (R_{eq,start} + R_{eq,mid}) / 2$$

 
## Impact of Rise/Fall times

- Impacts the  $I_{DS}-V_{DS}$  trajectory



 
## Impact of Rise/Fall times

- Impacts the  $I_{DS}-V_{DS}$  trajectory




## Impact of Supply Voltage

- Lowering VDD, slows down the circuit

 

EECS151 L12 CMOS2

 


Hkhalil Fall 2021

41


Berkeley
 
## Quiz: Inverter Delay

- If we double the load capacitance, assuming the default Vout shown in blue, which of the following waveforms shows the new Vout?



EECS151 L12 CMOS2

 

Hkhalil Fall 2021

42

Berkeley

## Summary

- CMOS allows for convenient switch level abstraction
- CMOS pull-up and pull-down networks are complementary
  - Graph models for CMOS gates
- Transistor sizing affects gate performance
- Delay is a linear function of R and C

EECS151 L12 CMOS2

Hkhalil Fall 2021

43

Berkeley