

EECS 151/251A

Discussion 1

Alisha Menon

8/30/21, 8/31/21, and 9/1/21

About me (Alisha Menon)

- 4th year PhD student advised by Jan Rabaey
- Research in hardware-efficient biomedical classification, devices and systems
- Hobbies: dance, biking, tennis



My job:

- To help **you** get the most out of this class!
- Discussion sections
 - Monday 3-4pm, social sciences building 170
 - Tuesday 8-9am, virtual
 - Wednesday 3-4pm, genetics and plant bio 107
 - Review the past week
 - Answer questions
 - Example problems
- Office hours
 - Alisha's: Monday 2-3pm
 - A GSI will have one everyday, times listed on course website:
 - <https://inst.eecs.berkeley.edu/~eecs151/fa21/>
- Piazza
 - Please contact GSIs here instead of email!
 - GSIs will try to respond within 24 hours

Recommendations for success

- Put the most effort into labs/project!
 - They make you a great **engineer**, not just a good IC student
 - Understand **abstraction** leverage it for productive design
 - Stay in circuit design: Apple shows you how desperate they are!!!
 - Choose partners wisely
 - Balance your strengths/weaknesses
- Homework stresses **understanding**, not correctness
 - Open-ended questions have higher weighting
- Stay up-to-date on industry & research trends!
 - IEEE [Computing](#) & [Semiconductors](#), [EE Times](#), [Semiconductor Engineering](#), [TechInsights](#)
 - IEEE [CAS](#) & [Computer](#) Societies, [ACM](#), etc.

Agenda

- Administrativa
- ASIC vs FPGA
- Simple logic gates
- Boolean logic problem
- Verilog intro

Administrativa


- Homework 1 will be posted this week
- Discussions are 3 times a week — please pick one
 - We have to account for capacity limitations this semester
- Labs are in Cory 111/117

ASIC vs FPGA

ASIC

- Application-Specific Integrated Circuit
- Use standard cells, SRAM, custom analog circuits

2-input NAND gate

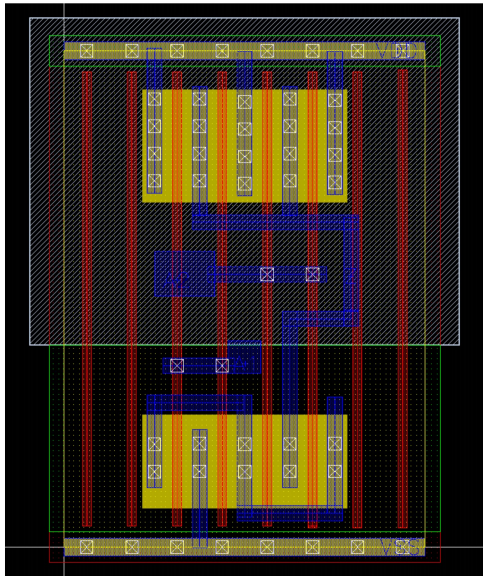

Metal: Blue

Transistors: Red + Yellow


Apple's A11 Bionic SoC



<https://www.macworld.com/article/3275567/iphone-ipad/apple-7nm-a12-chip-iphone.html>

FPGA

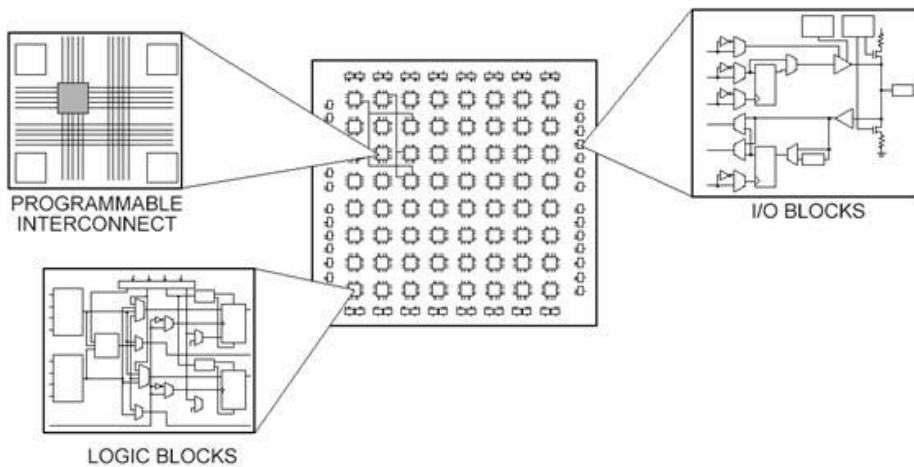- Field-Programmable Gate Array
- Use LUTs, block RAM, on-die IP cores



Typical FPGA Structure




Xilinx Virtex Family

ASIC vs FPGA


	ASIC	FPGA
Performance		
Design cost		
Per-unit cost		
Design time		
Custom blocks		
Job perspective		

Logic gates


Simple logic gates

 

a	b	c
0	0	
0	1	
1	0	
1	1	

 


a	b	c
0	0	
0	1	
1	0	
1	1	

 


a	b
0	
1	



a	b	c
0	0	
0	1	
1	0	
1	1	

 

a	b	c
0	0	
0	1	
1	0	
1	1	

 

a	b	c
0	0	
0	1	
1	0	
1	1	

- Logic gates are often the primitive elements out of which combinational logic circuits are constructed.
 - In some technologies, there is a one-to-one correspondence between logic gate representations and actual circuits (ASIC standard cells have gate implementations).
 - Other times, we use them just as another abstraction layer (FPGAs have no real logic gates).
- How about these gates with more than 2 inputs?
- Do we need all these types?

Boolean logic

$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

a	b	y
0	0	
0	1	
1	0	
1	1	

- What basic function does this represent?

Boolean expression standard forms

- Same truth table can have many gate realizations
- However, we can find standard forms for a boolean expression
- Two types:
 - Sum of Products (SOP)
 - Product of Sums (POS)

Sum of products using minterms

minterms	a	b	c	f
$a'b'c'$	0	0	0	1
$a'b'c$	0	0	1	1
$a'bc'$	0	1	0	1
$a'bc$	0	1	1	0
$ab'c'$	1	0	0	0
$ab'c$	1	0	1	0
abc'	1	1	0	0
abc	1	1	1	0

Product of sums using maxterms

Due to De Morgan's theorem: $(A+B+C)' = A' * B' * C'$

maxterms	a	b	c	f
$a+b+c$	0	0	0	1
$a+b+c'$	0	0	1	1
$a+b'+c$	0	1	0	1
$a+b'+c'$	0	1	1	0
$a'+b+c$	1	0	0	0
$a'+b+c'$	1	0	1	0
$a'+b'+c$	1	1	0	0
$a'+b'+c'$	1	1	1	0

Simplification – Boolean algebra laws

Operations with 0 and 1 (annulment/identity laws)	$x + 0 = x$ $x + 1 = 1$	$x \cdot 0 = 0$ $x \cdot 1 = x$
Idempotent law	$x + x = x$	$x \cdot x = x$
Involution (double negation) law	$\bar{\bar{x}} = x$	
Complementarity	$x + \bar{x} = 1$	$x \cdot \bar{x} = 0$
Commutativity	$x + y = y + x$	$x \cdot y = y \cdot x$
Associativity	$(x + y) + z = x + (y + z)$	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$
Distributivity	$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$	$x + (y \cdot z) = (x + y) \cdot (x + z)$
Simplification	$x \cdot y + x \cdot \bar{y} = x$ $x + x \cdot y = x$	$(x + y) \cdot (x + \bar{y}) = x$ $x \cdot (x + y) = x$

Example: $a'b'c' + a'b'c + a'bc'$

Verilog

Hardware description language (HDL)

- Used to describe a digital system for your tools to synthesize
- Keep reminding yourself: **I'm describing hardware**, I'm not writing a program!
- Always sketch out your circuit, even if just just at a high level (modules, ports, connections)
- Get hands on practice! Don't spend too much time only reading references

Verilog design types

- Structural Verilog
 - Directly describe the schematic in text format
 - Typically combinational logic circuits build out of basic gates and module instances
- Behavioral Verilog
 - Describe the desired functionality
 - Use assign statements for continuous assignment
 - Use always@ blocks to describe how a circuit behaves under certain conditions

Verilog modules


- Black box design unit with a specific purpose
- Designer specifies inputs, outputs, behavior
- Example: 2-input multiplexer

Wire vs. Register

- Wire

In ——— Out

- Register

 

Examples (with common syntax errors)

```
module mux2 (  
    input [1:0] in,  
    input select,  
    output out);  
assign out = (select = 1) ? in[1] : in[0]  
endmodule
```

```
module mux2_behav (in,out,out_b)  
    input [0:1] in;  
    input select;  
    output out;  
    output out_b;  
always @ (in)  
    if (select == 1)  
        out = in[1]  
        out_b = ~in[1]  
    else  
        out = in[0]  
        out_b = ~in[0]  
endmodule
```

Examples (corrected)

```
module mux2 (  
    input [1:0] in,  
    input select,  
    output out);  
  
    assign out = select ? in[1] : in[0];  
  
endmodule
```

```
module mux2_behav (in,select,out,out_b);  
    input [1:0] in;  
    input select;  
    output reg out;  
    output reg out_b;  
  
    always @ (*) begin  
        if (select == 1) begin  
            out = in[1];  
            out_b = ~in[1];  
        end else begin  
            out = in[0];  
            out_b = ~in[0];  
        end  
    end  
  
end  
  
endmodule
```