

EECS151 : Introduction to Digital Design and ICs

Lecture 21 – Dividers, Latches

Bora Nikolić



Pentium FDIV Bug (from Wikipedia)

The Pentium FDIV bug is a hardware bug affecting the floating-point unit (FPU) of the early Intel Pentium processors. Because of the bug, the processor would return incorrect binary floating point results when dividing certain pairs of high-precision numbers. The bug was discovered in 1994 by Thomas R. Nicely, a professor of mathematics at Lynchburg College. Missing values in a lookup table used by the FPU's floating-point division algorithm led to calculations acquiring small errors. While these errors would in most use-cases only occur rarely and result in small deviations from the correct output values, in certain circumstances the errors can occur frequently and lead to more significant deviations



Review

- Binary multipliers have three blocks:
 - Partial-product generation (NAND or Booth)
 - Partial-product compression (ripple-carry array, CSA or Wallace)
 - Final adder
- Multipliers are often pipelined
- Constant multipliers can be optimized for size/speed
- Shifters and crossbars are common building blocks in digital systems
 - Often require customization



Dividers

Pencil-And-Paper Division

	1512	quotient
divisor	3 4537	dividend
	3000	$\text{divisor} * q_i * 10^i$
	1537	partial remainder
	1500	
	0037	
	0030	
	0007	
	0006	
	0001	remainder

Division is an iterative process:

$$r(i) = r(i+1) - q_i * D * 10^i$$

We usually 'guess' q_i

Restoring Divider


- Assume $q_i = 1$
- Subtract divisor from r ; check if $r(i) \geq 0$
 - if $r(i) > 0$, guess was good ($q_i = 1$)
 - if $r(i) < 0$, restore the value by adding divisor, $q_i = 0$
- Shift divisor to right
- Repeat n times

More efficient to shift the remainder right

n shifts

n subtractions

$n/2$ restorations

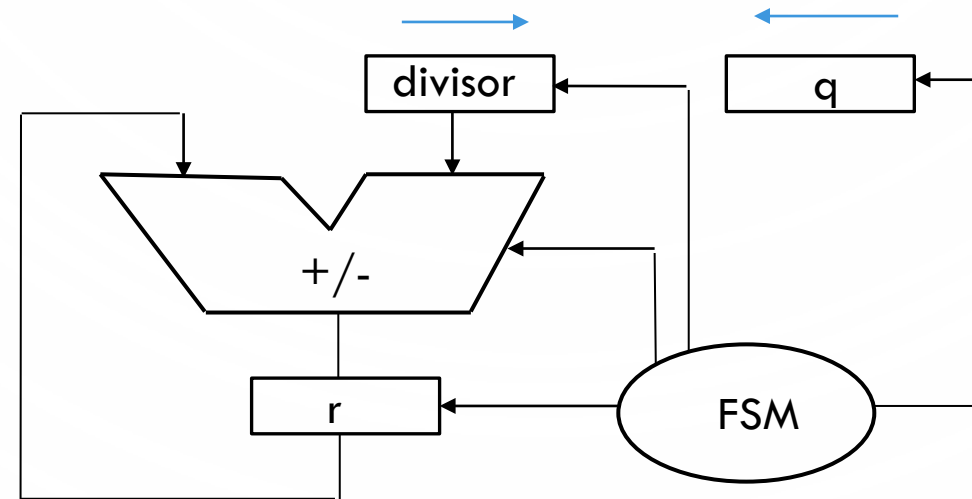

Non-Restoring Divider

- Doesn't restore if $r(i) < 0$
- Instead, adds the divisor in the next iteration
 - n shifts
 - n additions/subtractions


Faster Dividers

- Divide in a higher radix than 2 (typically 4, i.e. guess $q_i q_{i+1}$)
- Keep the partial remainders in redundant form
- Sweeney-Robertson-Tocher (SRT) algorithm
 - Used in many processors




Timing

Synchronous Timing: Review

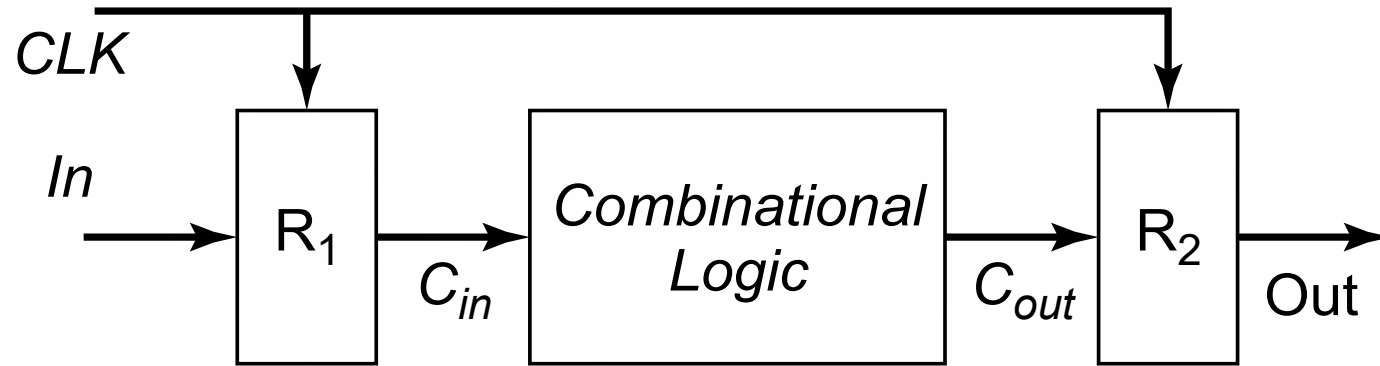


Latch Parameters

- Latch is transparent high or low

 

```
module latch
(
    input clk,
    input d,
    output reg q
);

 
always @(clk or d)
begin
    if ( clk )
        q <= d;
    end
endmodule
```



Delays can be different for rising and falling data transitions


Flip-Flop Parameters

- Flip-flop is edge-triggered

 

```
module flipflop
(
    input clk,
    input d,
    output reg q
);

 
    always @(posedge clk)
    begin
        q <= d;
    end
endmodule
```



Delays can be different for rising and falling data transitions

Clock Uncertainties

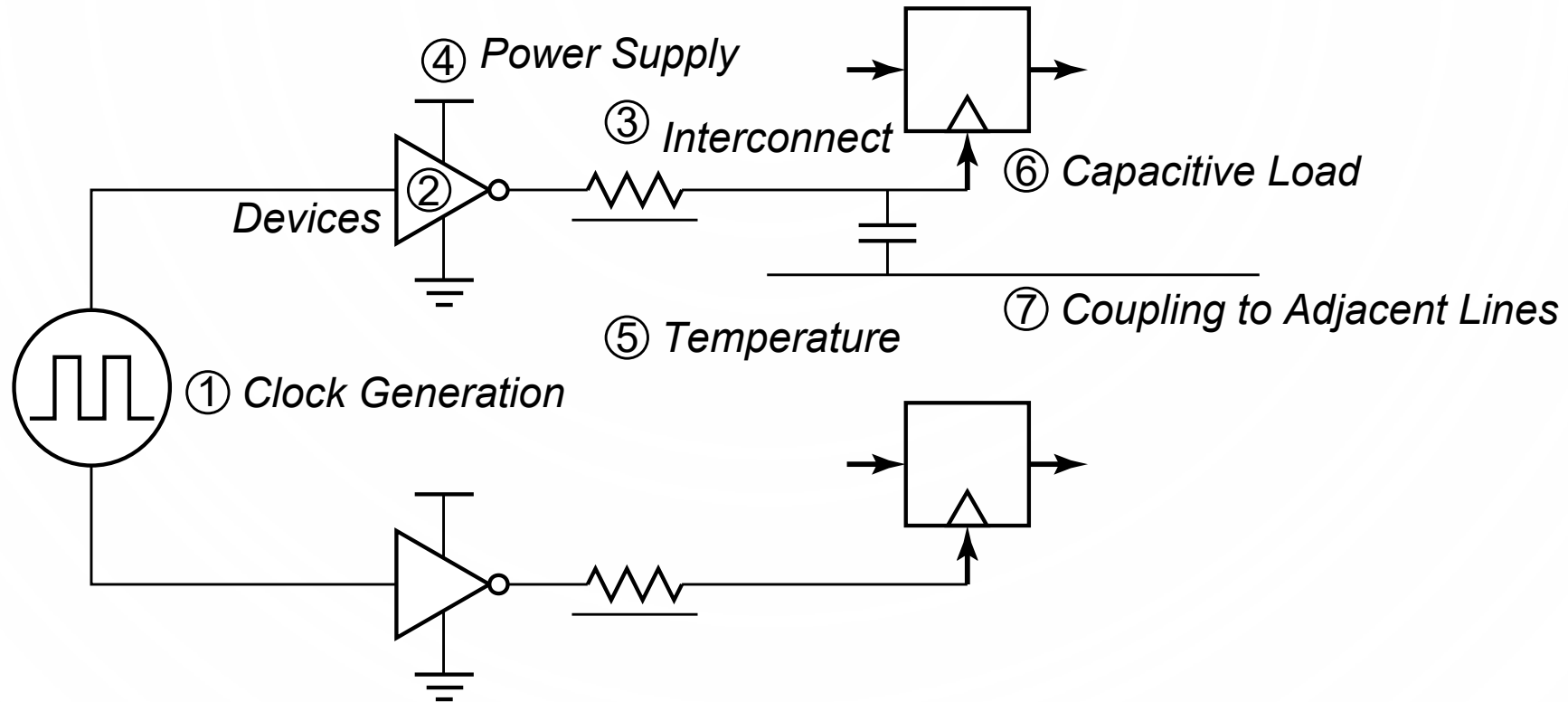- Clock arrival time varies in space and time




Sources of clock uncertainty

Clock Nonidealities

- Clock skew
 - Spatial variation in temporally equivalent clock edges; deterministic + random, t_{SK}
- Clock jitter
 - Temporal variations in consecutive edges of the clock signal; modulation + random noise
 - Cycle-to-cycle (short-term) t_{JS}
 - (there also exists long-term jitter t_{JL})
- Variation of the pulse width
 - Important for level sensitive clocking with latches


Clock Skew and Jitter

 - Both skew and jitter affect the effective cycle time
- Only clock distribution skew affects the race margin



Timing Constraints

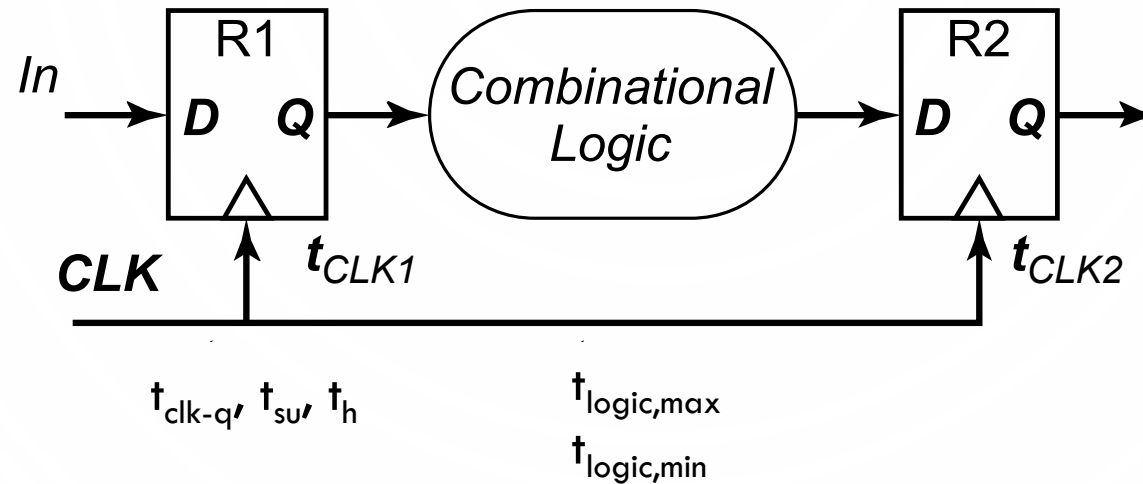- First flip-flop launches data on the first clock edge, the second one captures on the second clock edge




Minimum cycle time is set by the longest logic path:

$$T - t_{sk} - t_i = t_{c-q} + t_{su} + t_{logic,max}$$

Worst case is when receiving edge arrives early

Timing Constraints

 - Launching flip-flop shouldn't contaminate its own data



$t_{\text{clk-q}}, t_{\text{su}}, t_{\text{h}}$

$t_{\text{logic,max}}$

$t_{\text{logic,min}}$


Hold time constraint:

$$t_{\text{c-q}} + t_{\text{logic, min}} > t_{\text{hold}} + t_{\text{sk}}$$

Worst case is when receiving edge arrives late
Race between data and clock

Slack

- Visualizing arrival times

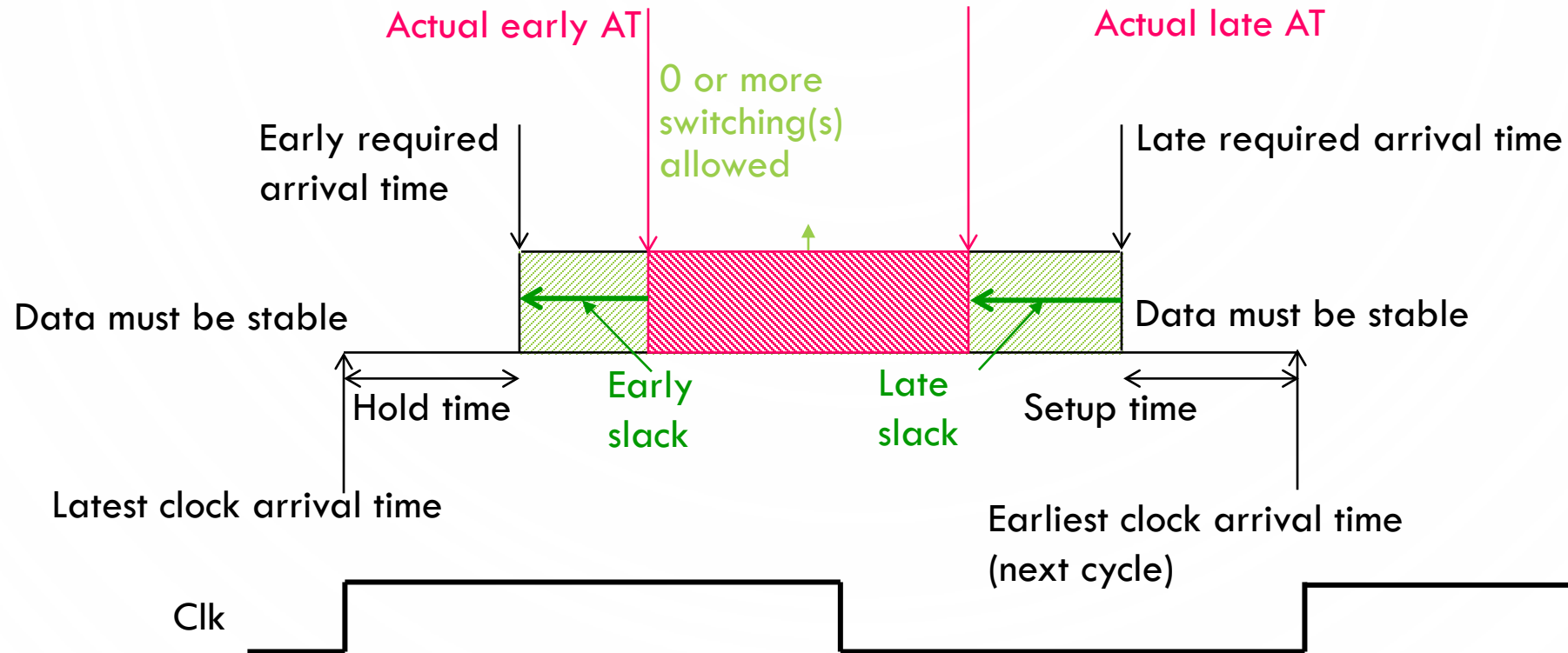

Timing Analysis

- Report timing

Startpoint: dig_agc_0/int_term_reg_0_
(rising edge-triggered flip-flop clocked by clk_agc)
Endpoint: dig_agc_0/int_term_reg_0_
(rising edge-triggered flip-flop clocked by clk_agc)

Point	Fanout	Derate	Incr	Path	Voltage

clock clk_agc (rise edge)		0.00	0.00		
clock source latency		3.13	3.13	r	
timing_control_0/C1276/Y (AND2X3)		0.00	3.13	r	3.00
timing_control_0/o_clk_agc (net)	2	0.00	3.13	r	
dig_agc_0/BUFX8_G6B1I2/A (BUFX8)		0.00	&	3.13	r 3.00
dig_agc_0/o_clk_agc_G6B1I2 (net)	15	0.00		3.91	r
dig_agc_0/int_term_reg_0_/CP (SDFFCQX2)		0.01	&	3.92	r 3.00
...					
clock reconvergence pessimism		0.00	3.92		
clock uncertainty			0.10	4.02	
dig_agc_0/int_term_reg_0_/CP (SDFFCQX2)		0.00	4.02	r	
library hold time		-0.48	3.54		
data required time			3.54		

data required time			3.54		
data arrival time			-5.57		



slack (MET)			2.03		

Administrivia

- Midterm 2 scores released
 - Final can clobber either midterm!
- Homework 9 posted on Friday, due 11/15
 - One more homework before Thanksgiving
- Project checkpoints #2 this week
- Thursday is a holiday (Veterans' Day)

Midterm 2

 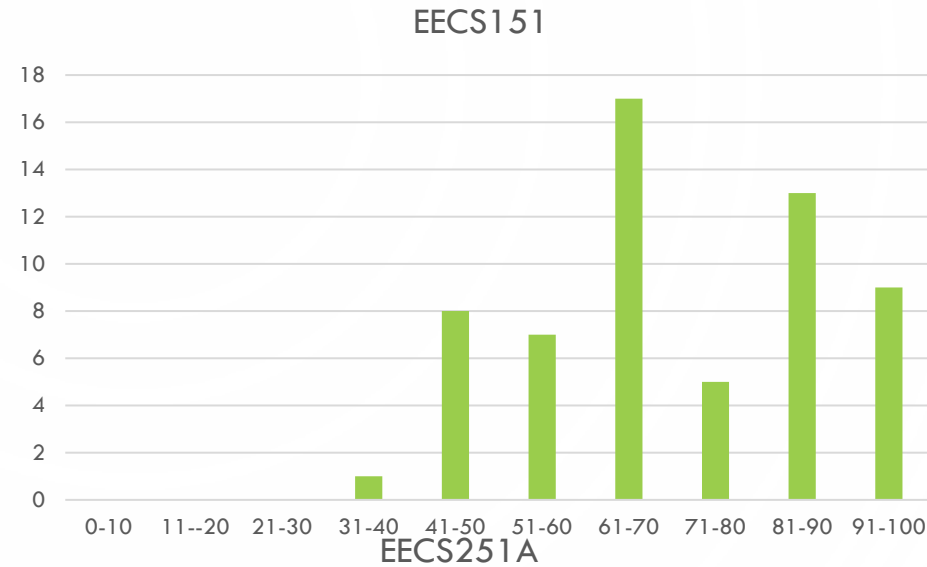- EECS151
 - Max: 60.5/61
 - Average: 42.7/61 (70%)
- EECS251A
 - Max: 71/71
 - Average: 59.2/71 (83%)






Latch-Based Timing



Latch-Based Timing

 - Is there a possible timing problem in this path?



Latch-Based Timing


- Two clock phases

 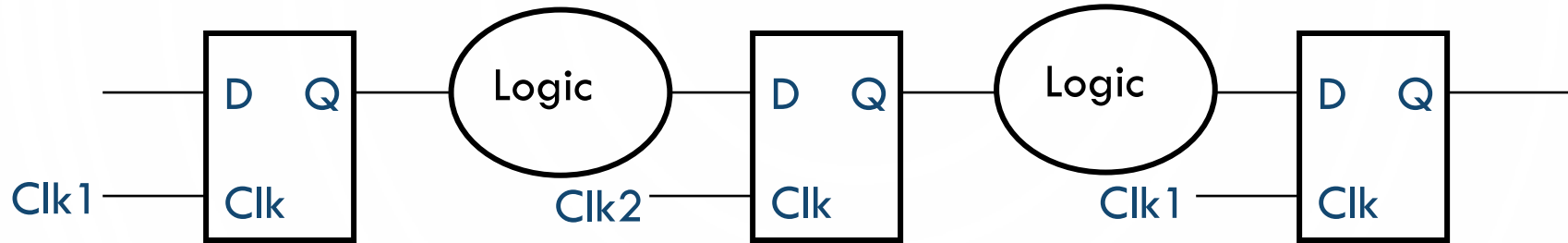

- Two consecutive latches are never transparent at the same time
 - Conservative

Latch-Based Timing

- Single clock phase

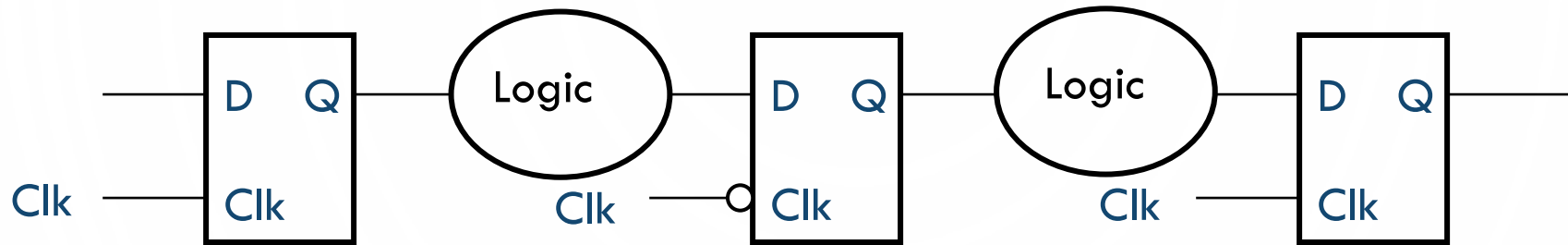



- Possibility of a race condition
 - Needs timing analysis (EE241B/EECS251B)



Latches


Cross-Coupled Inverter

- Positive feedback stores the data

  


Writing into a Static Latch

 Use the clock as a control signal (to break the positive feedback), that distinguishes between the transparent and opaque states



Converting into a MUX

 


Forcing the state (functionality depends on sizing)


Tri-State Inverter

- Out is Z when Clk=0


- Latch

 


Clk-Q Delay

 

Setup and Hold Times

 


(a)

 

(b)


Setup-Hold Time Illustrations

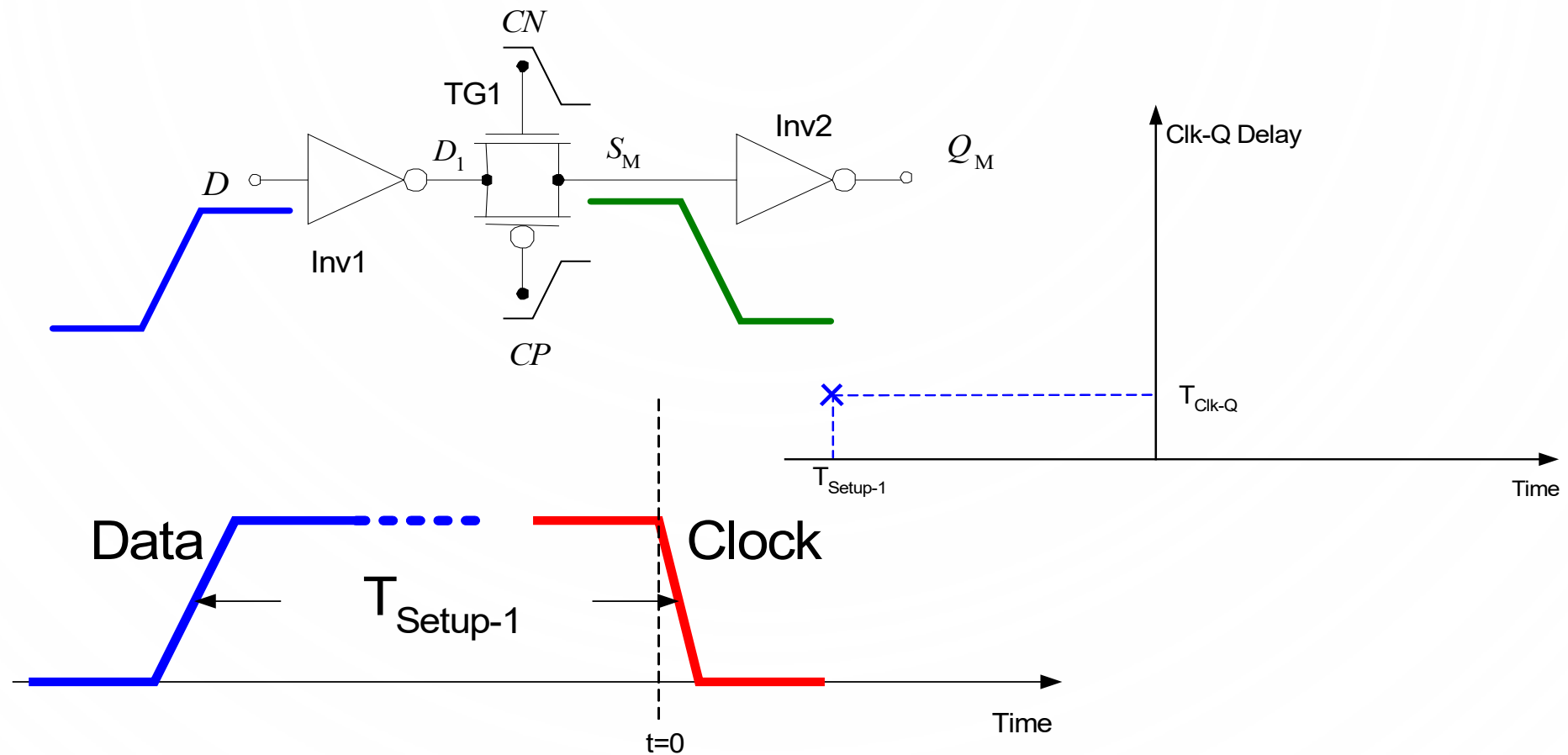Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

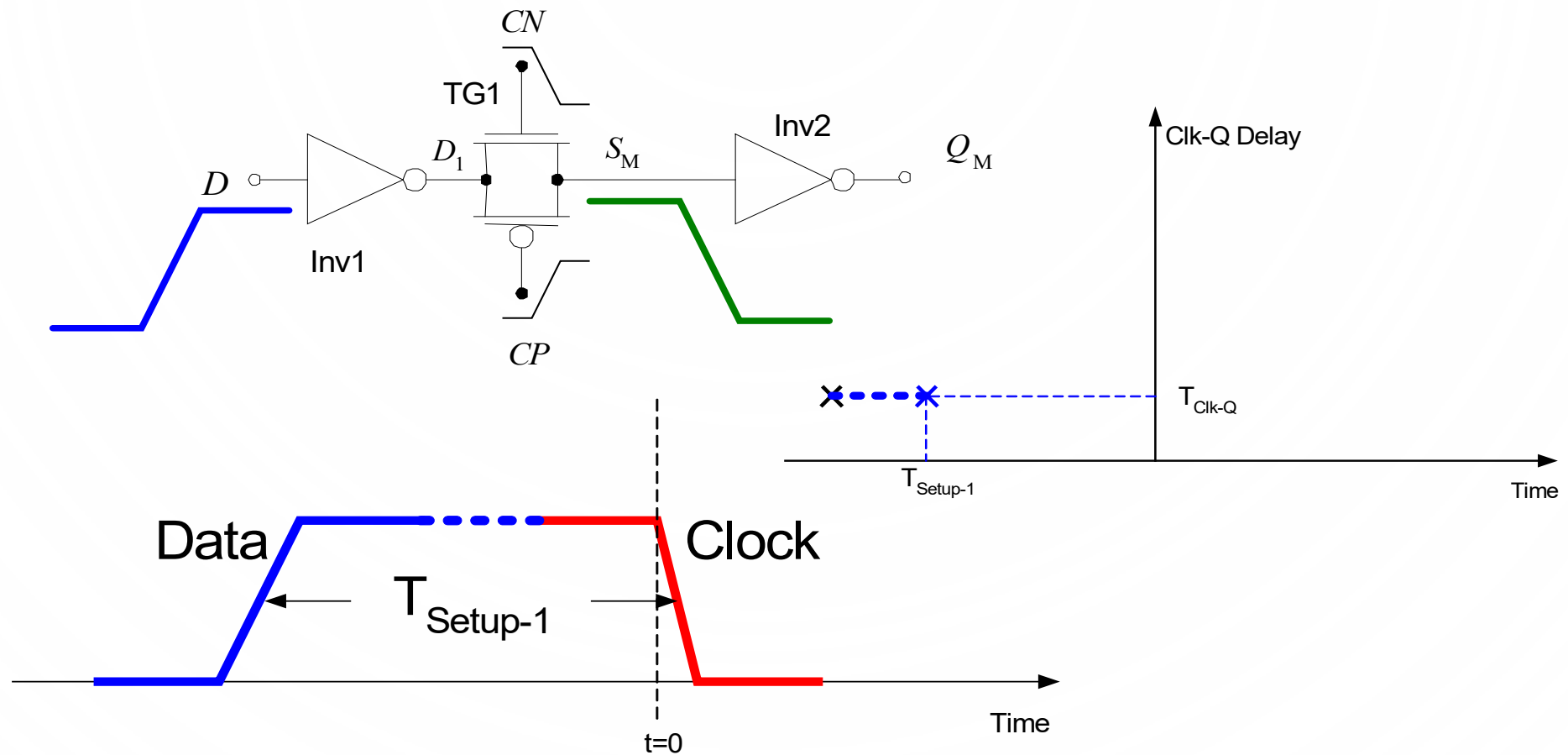Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

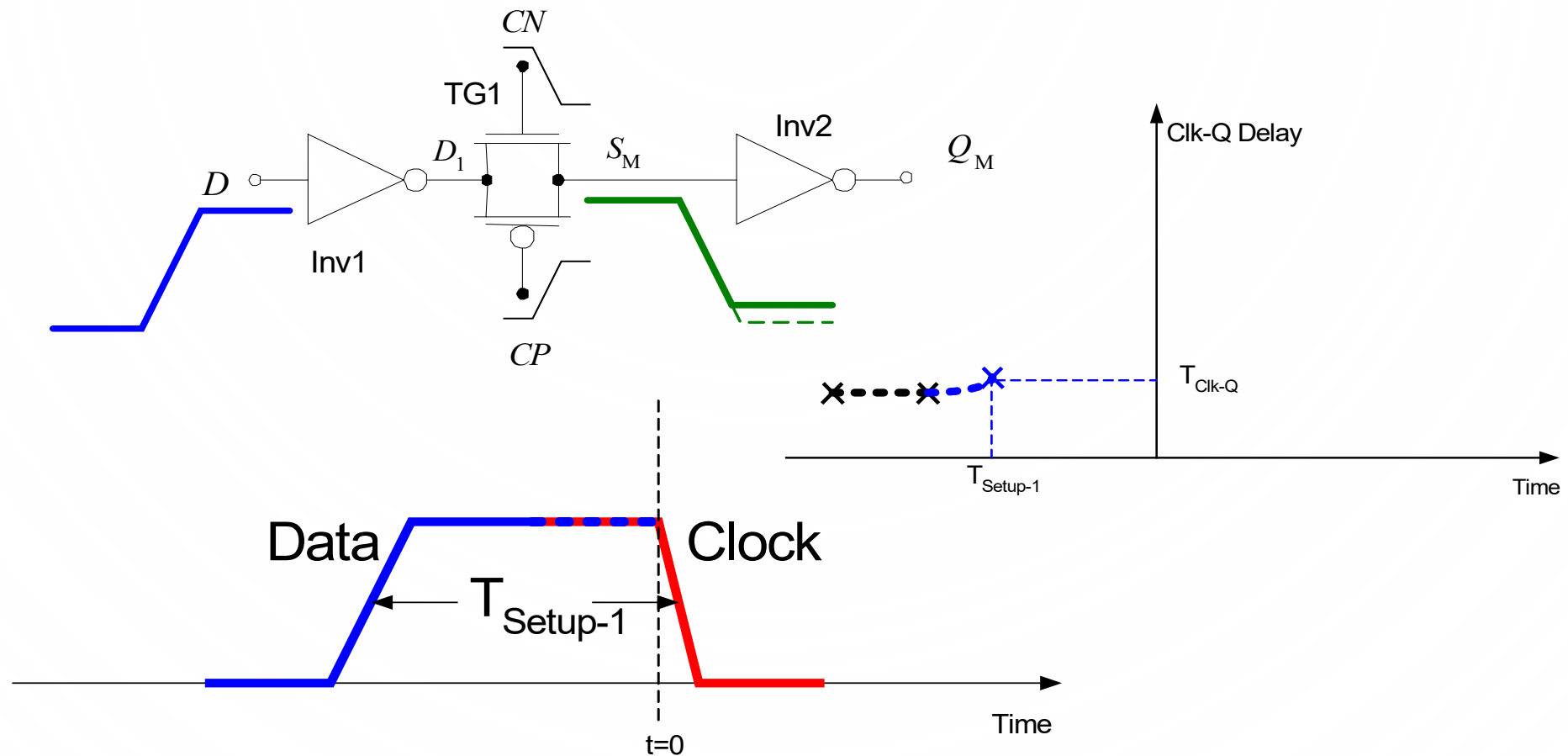Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

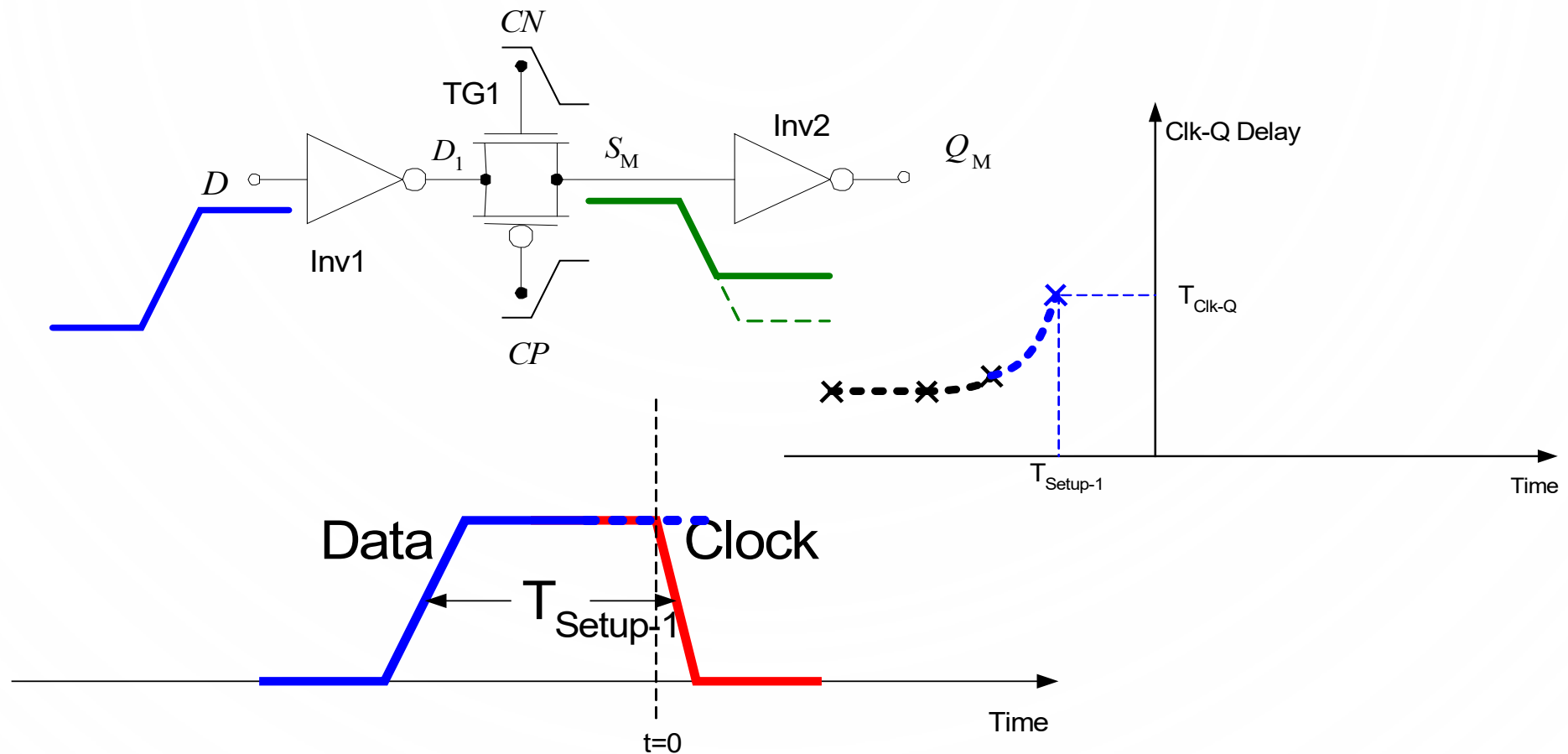Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

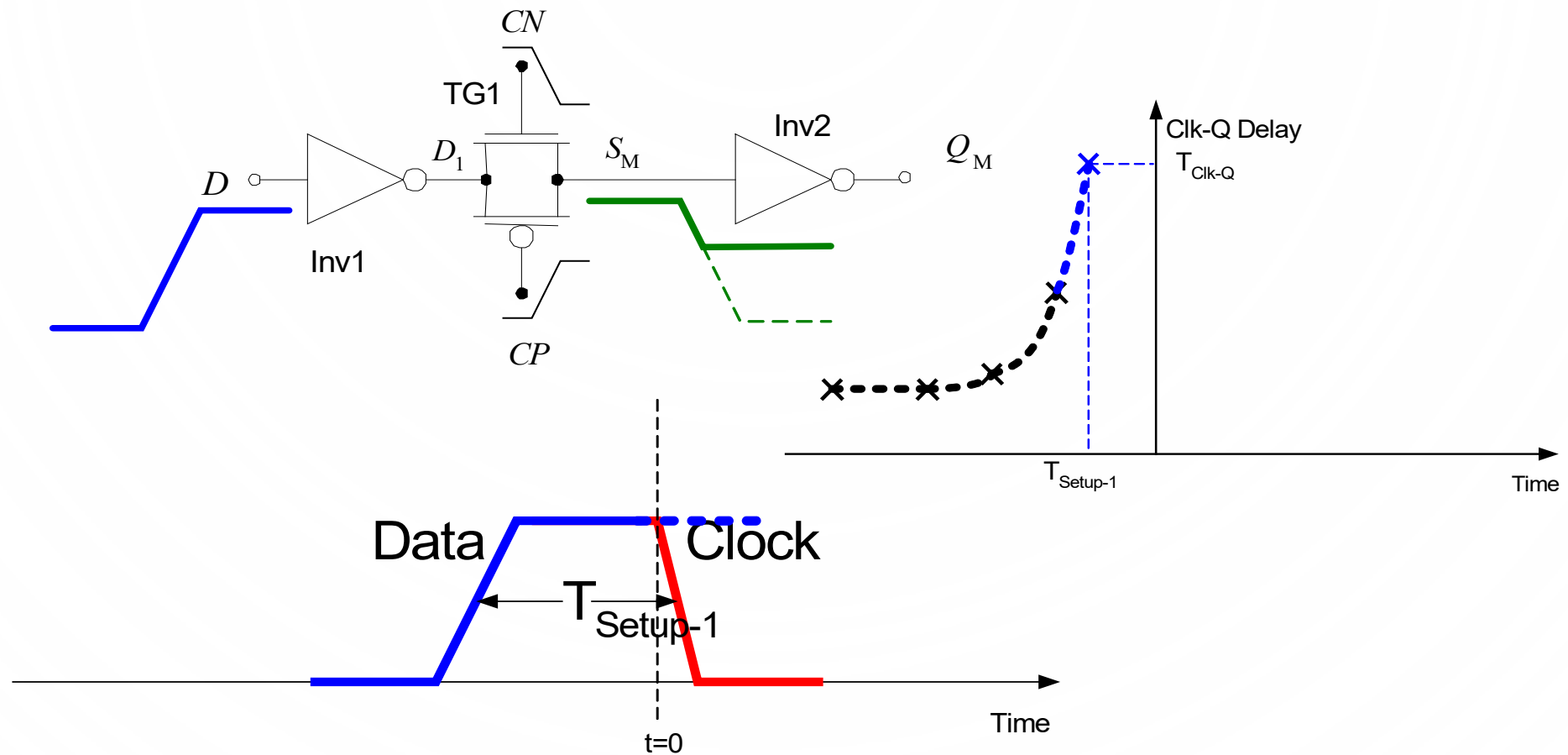Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

Hold-1 case

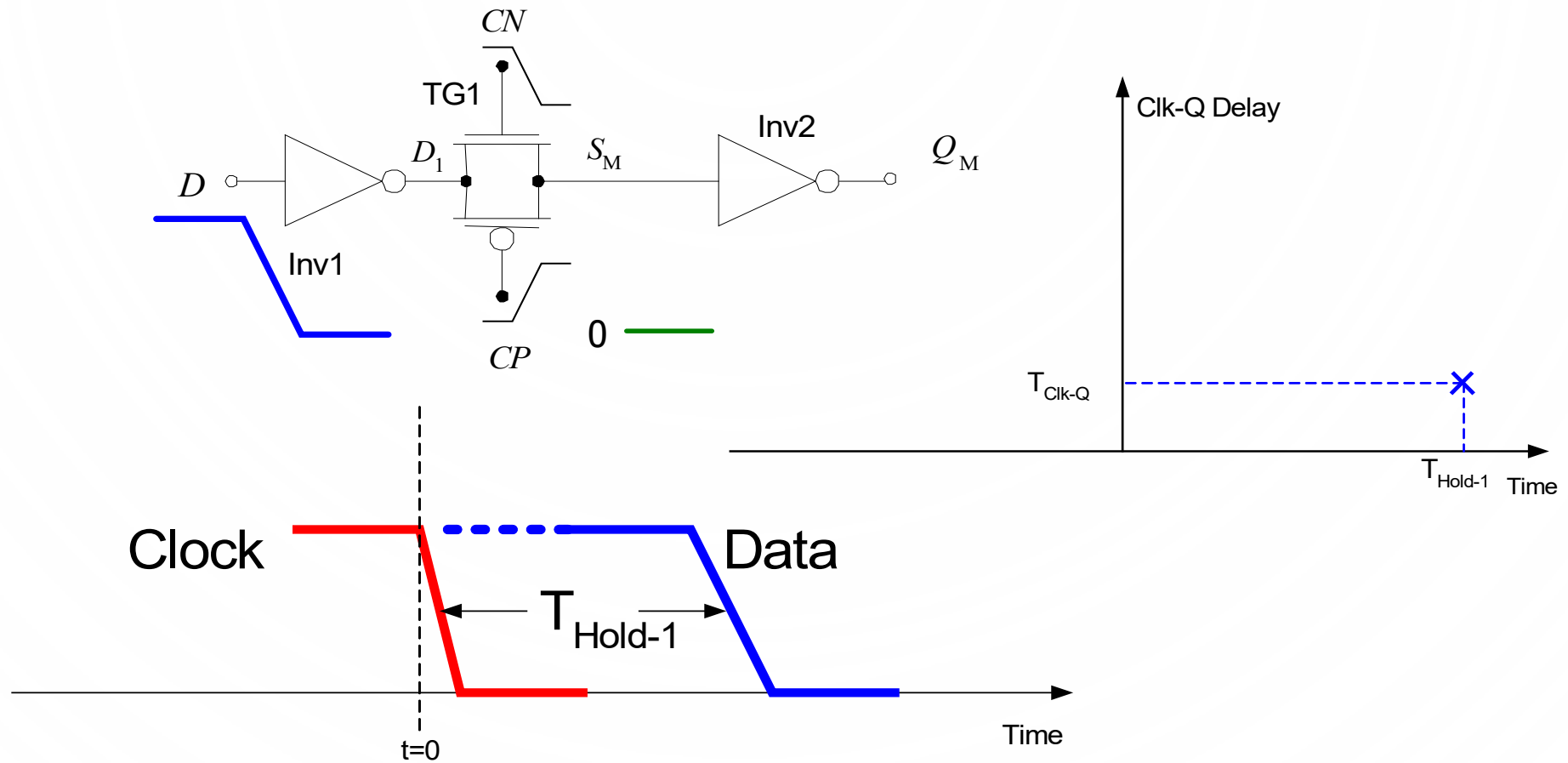


Setup-Hold Time Illustrations

Hold-1 case

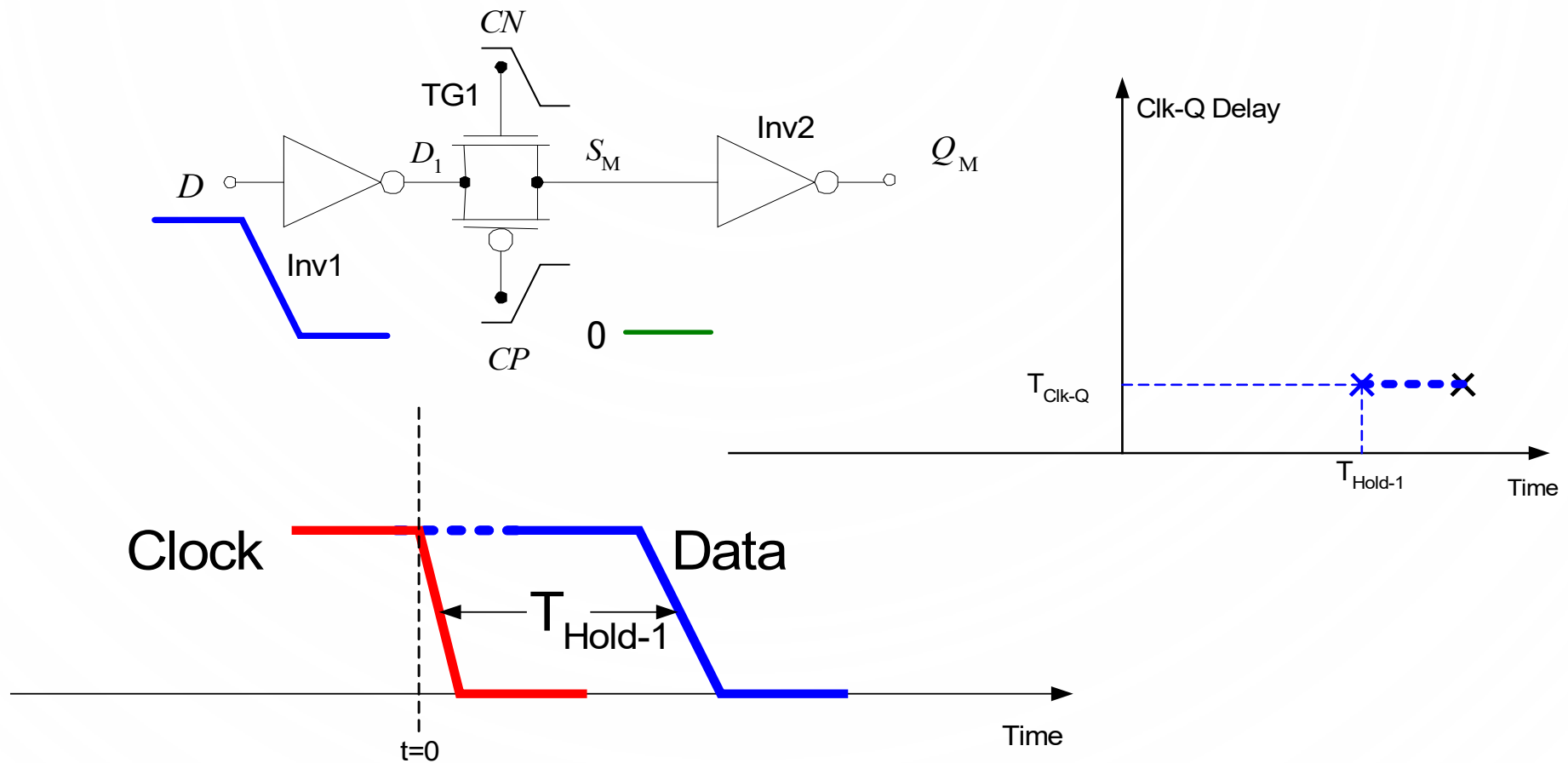


Setup-Hold Time Illustrations

Hold-1 case

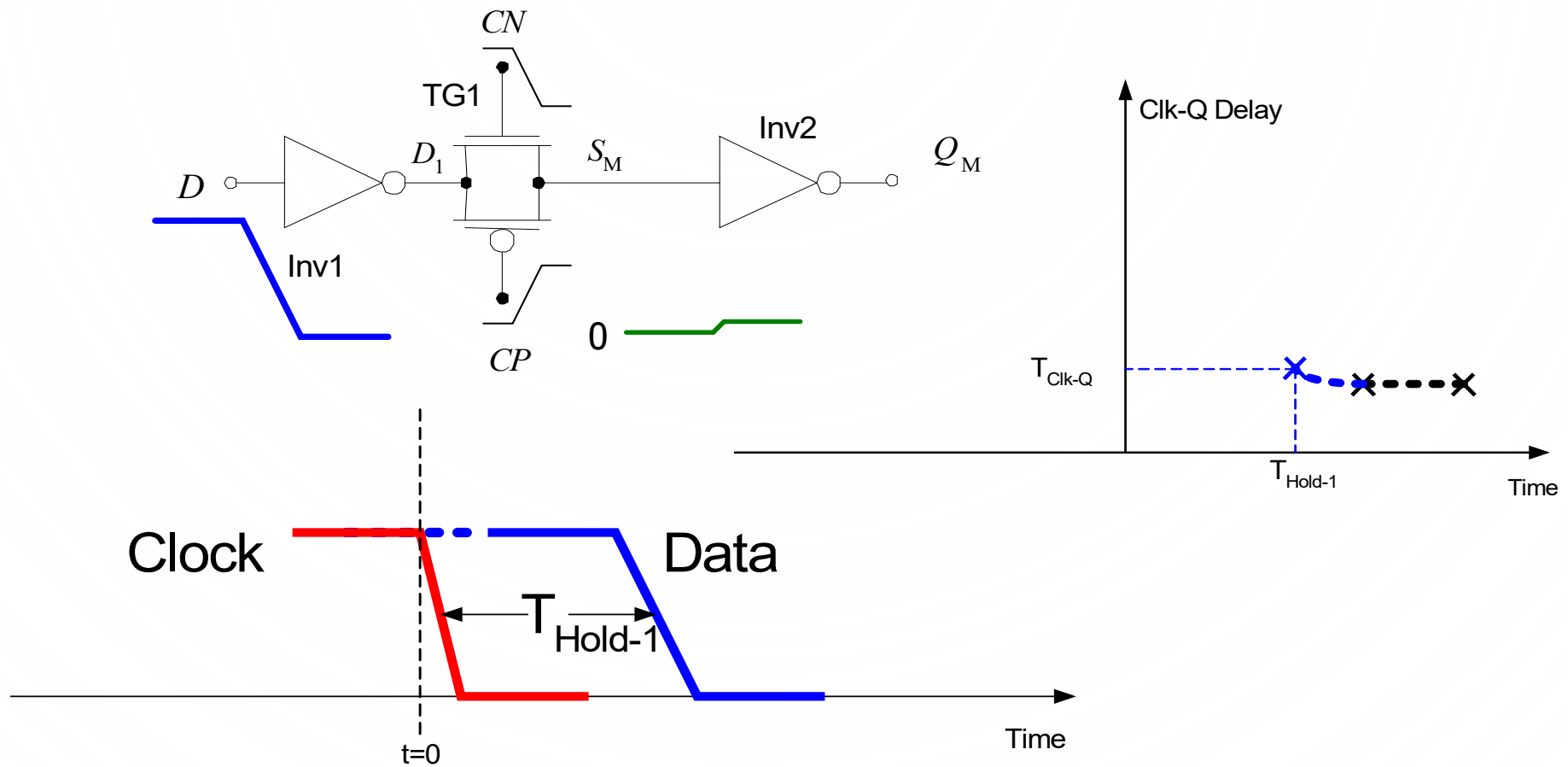


Setup-Hold Time Illustrations

Hold-1 case

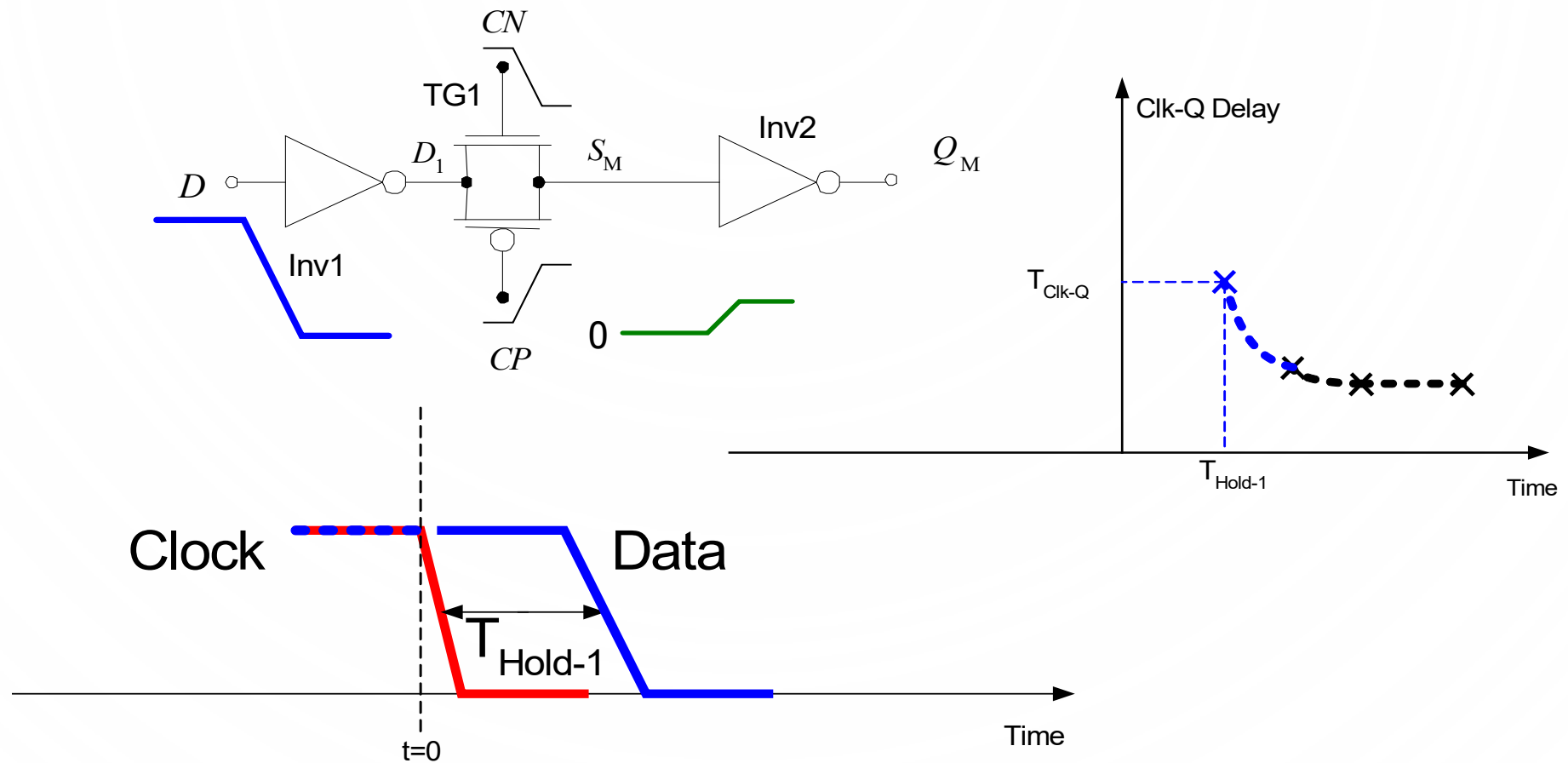

Setup-Hold Time Illustrations

Hold-1 case

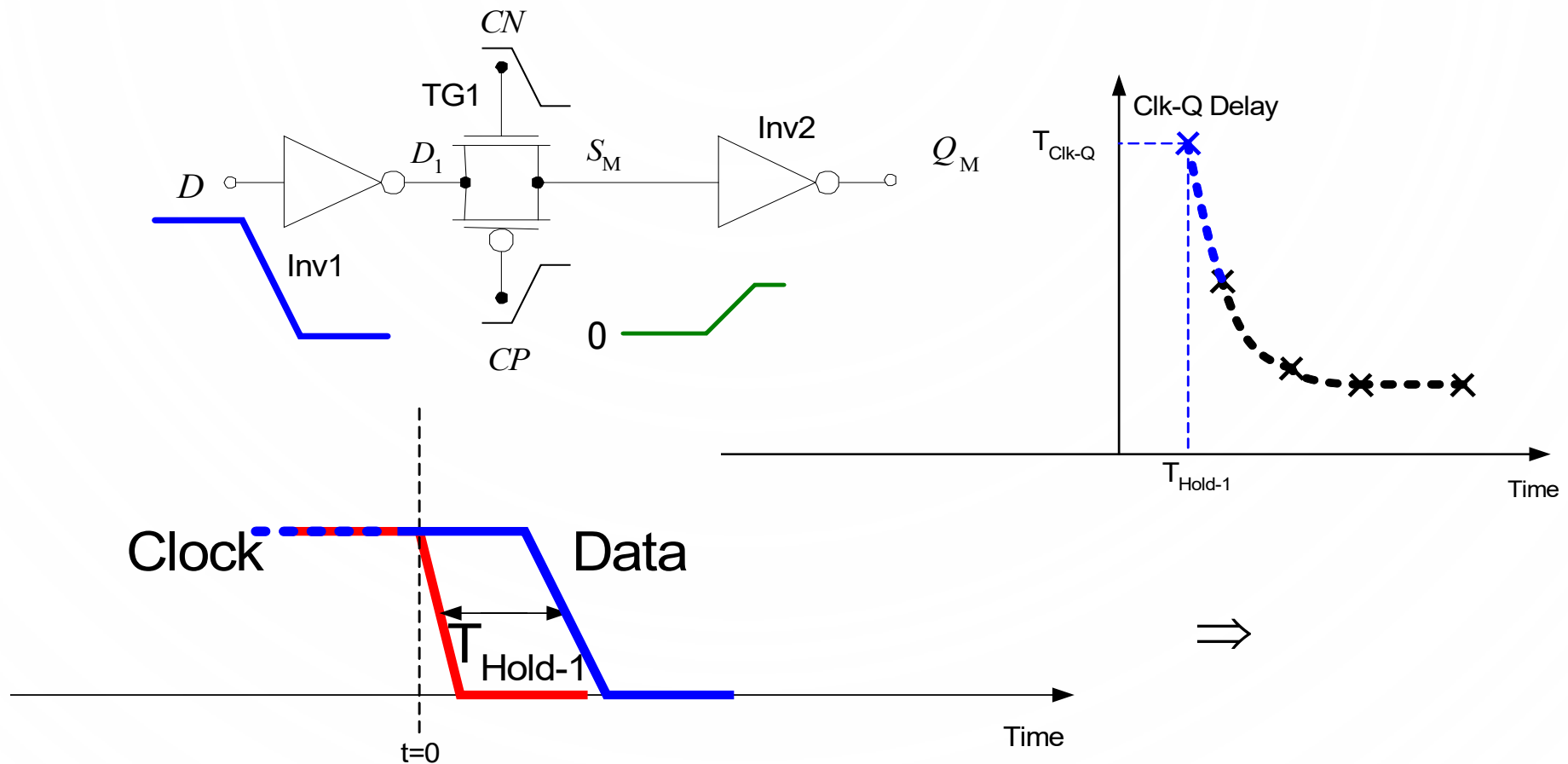





Flip-Flops

Types of Flip-Flops

Latch Pair (Master-Slave)

 


Pulse-Triggered Latch

 


Transmission Gate Flip-Flop

- Two back-to-back latches

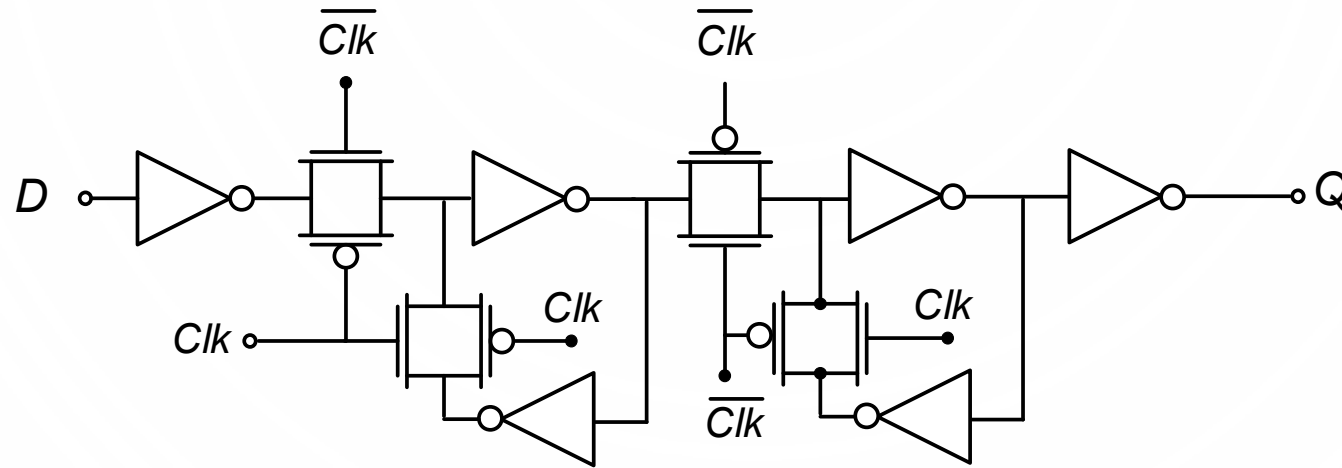


Aside: Inverter Fork

 - Often found in flip-flops: equalize C_k , C_{kb} delays
 - Logical effort = ?



Clk-Q, Setup and Hold Times

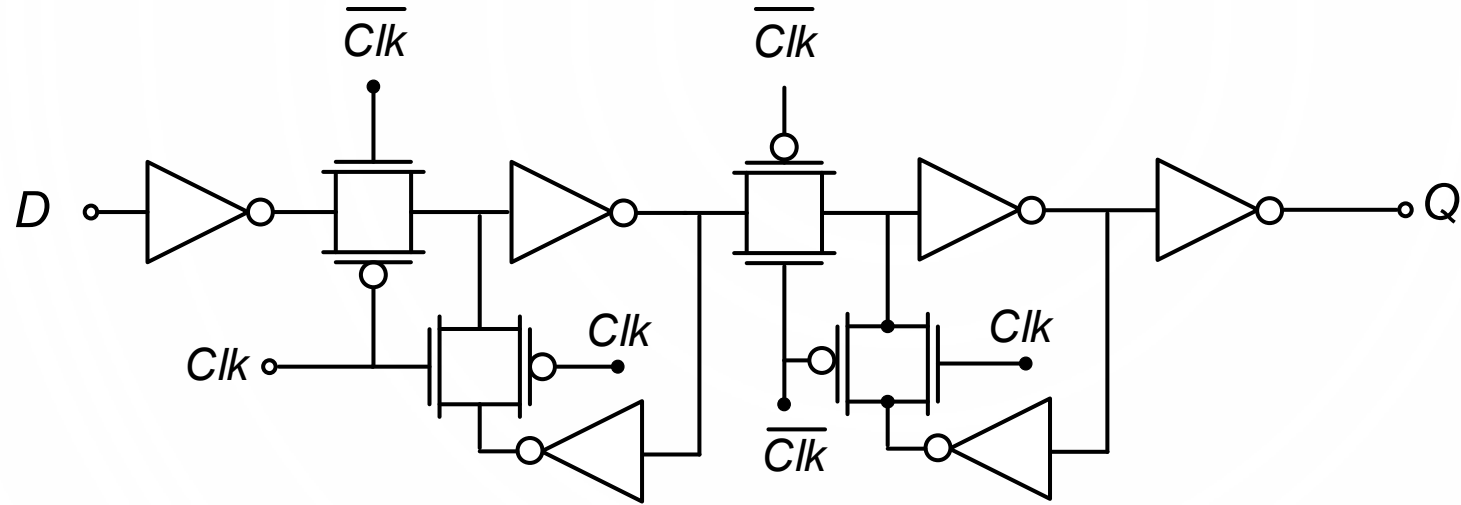

Review

- Binary division is a slow, iterative process
- Non-restoring division speeds it up
- SRT divider, higher radix, redundant number representation
- Timing analysis for early and late signal arrivals
- Flip-flop-based pipelines are a lot easier to analyze than latch-based ones
- Latches are based on positive feedback
- Clk-Q delay calculated similarly to combinational logic
- Setup, hold defined as D-Clk times that correspond to Clk-Q delay increases
- Flip-flop is typically a latch pair