

# EECS 151/251A

## Discussion 8

Daniel Grubb 10/19, 10/20, 10/25

# Administrivia

- Lab 6 due Friday 10/22
  - Cutoff for checkoffs and submissions is the end of next week's lab sessions
- Project starts this week
  - Do your best to finish up labs and don't procrastinate!
- Homework 6 due Friday 10/22
- Midterm 1 grades release
  - Regrades due Friday 10/22
- Midterm 2 on the horizon (tentatively November 4th)
- What are you having trouble with? Feedback?

# Agenda



- Topics
  - Inverter delay and sizing
  - Logical effort
  - Path effort
  - Elmore delay
- How familiar/comfortable are you with:
  - transistor switch model?
  - inverter delay?
  - inverter delay optimization?
  - logical effort?
  - parasitic delay?
  - path effort/optimization?

# A Note on Notation and Values

- PMOS / NMOS ratios
  - Old technologies/textbooks give 2:1, this class generally uses 1:1
- Ratio of  $C_d$  to  $C_g = \gamma$  (gamma) = 1
  - Set by process technology
  - $\sim 1.2$  in recent processes, but still keep it 1
- Logical effort
  - **LE** or **g** both used
- Fanout or electrical effort
  - **F** for total fanout
  - **f** for stage fanout
  - **h** also used

# Inverter RC Delay Model


High-to-low

  


$$t_{p,HL} = (\ln 2)\tau = 0.7 R_{eq,n}(C_p + C_L)$$

$$\tau = R_{eq,n}(C_p + C_L)$$


# Inverter Delay

 

NMOS with size W

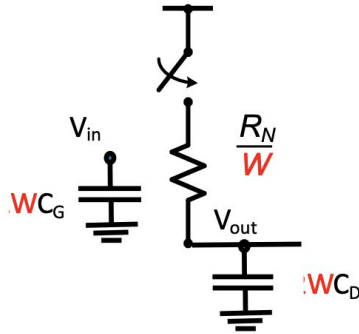

PMOS with same R as NMOS

 

$$t_p = 0.69 \left( \frac{R_N}{W} \right) (3W\gamma C_G) = 0.69(3\gamma)R_N C_G$$



Intrinsic inverter delay

What if we make the inverter bigger?
  
# Inverter Delay

- Add a load capacitance now
- Two components
  - Intrinsic delay
  - Fanout,  $f = C_L / C_{in}$
- FO4 delay: how many unit delays?
  - Why is this a useful quantity?

$$\begin{aligned}
 t_p &= 0.69 \left( \frac{R_N}{W} \right) (C_{int} + C_L) \\
 &= 0.69 \left( \frac{R_N}{W} \right) (3W\gamma C_G + C_L) \\
 &= 0.69 (3C_G R_N) \left( \gamma + \frac{C_L}{C_{in}} \right) \\
 &= t_{inv} \left( \gamma + \frac{C_L}{C_{in}} \right) = t_0 (\gamma + f)
 \end{aligned}$$




# Inverter Delay Scratch Area


 
# Inverter Sizing Thought Experiment

- Say we just have 1 inverter driving a load capacitance
  - We want to minimize delay
  - We can size it anyway we want
  - How should we size it?
- Be careful with this solution!



$C_L = C_{in}$  (next gate)



$$= t_{inv} \left( \gamma + \frac{C_L}{C_{in}} \right) = t_0 (\gamma + f)$$

# Inverter Chain Sizing

$$\frac{C_{in,j}}{C_{in,j-1}} = \frac{C_{in,j+1}}{C_{in,j}}$$


- Goal: minimize the delay of the path
  - Constrain the size of the first inverter + load capacitance in each case
  - What's a first pass solution?
- (1) Size a chain given N inverters
  - Key result: size stages to have identical fanout (minimize the total chain delay expression)
    - What does this say about each stage's delay?
  - Find f:  $f^N N = F = C_L / C_{in,1}$
  - Start from beginning or end of chain
- (2) Determine optimal N and size the chain
  - Assume fanout, f=4 (from graph)
  - Find number of stages, N (integer): ?
  - Same steps as (1)
  
$$t_p = N t_{inv} \left( \gamma + \sqrt[N]{F} \right), \quad F = C_L / C_{in}$$


 
# Inverter Chain Sizing Examples

- Chain of 3 with load cap of 64:
  - What if we add a capacitance in the middle?



- Load cap. of 1024, give N and sizings:
  - What if non-integer?

# Logical Effort and Parasitic Delay


- How much worse is a gate at driving a load capacitance than an inverter with the same input capacitance? (other ways to look at it)
  - Looks like an inverter, but the fanout seems larger
  - Easy way: size gate to deliver same as inverter current, take cap. Ratio
- $LE = (R_{eq,gate} C_{in,gate}) / (R_{eq,inv} C_{in,inv})$
- Parasitic delay: delay of gate driving no load (set by internal cap.)
  - Find gate RC delay, then extract  $t_{inv}$  term; ratio of internal cap to inverter

Effective Fanout (EF)

$$t_{pgate} = t_{inv} (p_{gate} + LE \cdot f)$$



Diagram illustrating the components of the gate delay equation:

 - $t_{pgate}$ : parasitic delay  $\neq f(W)$
- $t_{inv}$ : inverter delay
- $p_{gate}$ : logical effort  $\neq f(W)$
- $LE \cdot f$ : electrical fanout


  
# Logical Effort/Parasitic Delay Examples

- Also, consider if the PMOS/NMOS resistances are different than nominal?



# Path Delay

- How do we minimize delay more generally?

- Delay =  $t_{inv} \sum (p_i + LE_i \cdot f_i)$

- Path fanout:  $F = C_L / C_{in}$

- Path LE:  $G = g_1 g_2 \dots g_N$

$$b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}$$

- Branching effort

- Use similar result to inverter chain

- Best EF is still around 4

- Design process:


- Calculate Path Effort:  $PE = GFB$
  - Estimate best number of stages:  $N = \log_4 F$
  - Calculate Effective Fanout per stage:  $EF = PE^{(1/N)}$
  - Size the gates from beginning or end of chain

- Can always add inverters to the end of the chain

$$G = \prod g_i$$

$$F = \prod f_i = \prod g_i h_i$$


$$B = \prod b_i$$

 

# Path Delay Scratch Area
 
# Path Delay Example



- Remember,  $EF_i = LE_i \cdot f_i = LE_i \cdot C_{L,i} / C_{in,i}$




  
# Elmore Delay

- Approximate RC time constant of a tree network
- R's and C's include both transistors/parasitics and wires
  - Wire  $\pi$  model (where does the R and C come from?)
- Can think of it as:
  - $\sum [C_i \times (\text{sum of R's charging } C_i)]$
  - $\sum [R_i \times (\text{sum of C's that } R_i \text{ charges})]$



$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$

# Elmore Delay Examples

- What information do we need?
- Draw the equivalent model
- Calculate delay to outputs

