



EECS151 : Introduction to Digital Design and ICs

Lecture 24 – Decoders


Bora Nikolić

Happy 50th birthday Intel 4004!

The Intel 4004 is a 4-bit central processing unit (CPU) released by Intel Corporation in 1971. Sold for US\$60, it was the first commercially produced microprocessor, and the first in a long line of Intel CPUs. Launched November 15, 1971.

www.wikipedia.org
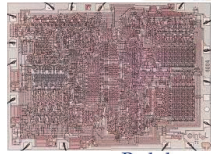
<https://www.intel.com/content/www/us/en/history/museum-story-of-intel-4004.html>



Nikolić Fall 2021



Review

- Dense memories are built as arrays of memory elements
 - SRAM is a static memory
- SRAM has unique combination of density, speed, power
- SRAM cells sized for stability and writeability
- SRAM and regfile cells can have multiple R/W ports

EECS151/251A L24 DECODERS

Nikolić Fall 2021




Memory Decoders




Decoder Design Example

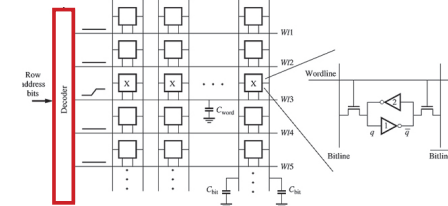- Look at decoder for 256x256 memory block (8KBytes)




Possible Decoder

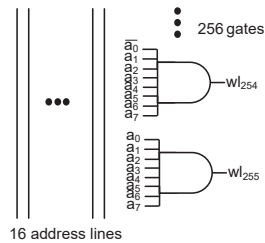- 256 8-input AND gates
 - Each built out of a tree of NAND gates and inverters
- Need to drive a lot of capacitance (SRAM cells and wordline wire)
 - What's the best way to do this?




Possible AND8

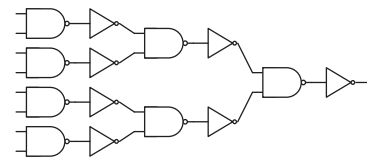- Build 8-input NAND gate using 2-input gates and inverters
- Is this the best we can do?
- Is this better than using fewer NAND4 gates?



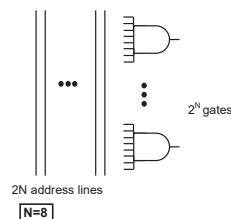Problem Setup

- Goal: Build fastest possible decoder with static CMOS logic
- What we know
 - Basically need 256 AND gates, each one of them drives one word line



Problem Setup (1)

- Each wordline has 256 cells connected to it
- $C_{WL} = 256 \cdot C_{cell} + C_{wire}$
 - Ignore wire for now
- Assume that decoder input capacitance is $C_{address} = 4 \cdot C_{cell}$

EECS151/251A L24 DECODERS

Nikolić Fall 2021



EECS151/251A L24 DECODERS

Nikolić Fall 2021



Problem Setup (2)


- Each address bit drives $2^8/2$ AND gates
 - A0 drives 1/2 of the gates, A0_b the other 1/2 of the gates
- Total fanout on each address wire is:

$$F = \Pi B \frac{C_{load}}{C_{in}} = 128 \frac{(256 C_{cell})}{4 C_{cell}} = 2^7 \frac{(2^8 C_{cell})}{2^2 C_{cell}} = 2^{13}$$

Decoder Fan-Out


- F of 2^{13} means that we will want to use more than $\log_4(2^{13}) = 6.5$ stages to implement the AND8
- Need many stages anyway
 - So what is the best way to implement the AND gate?
 - Will see next that it's the one with the most stages and least complicated gates

8-Input AND

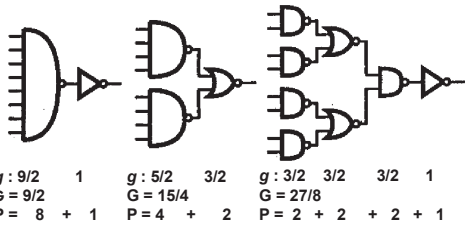

8-Input AND

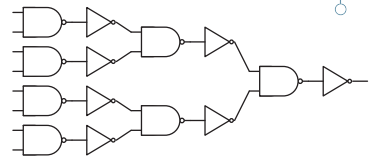- Using 2-input NAND gates
 - 8-input gate takes 6 stages
- Total G is $(3/2)^3 \approx 3.4$
- So H is $3.4 * 2^{13}$ – optimal N of ~ 7.4




Decoder So Far

- 256 8-input AND gates
 - Each built out of tree of NAND gates and inverters
- Issue:
 - Every address line has to drive 128 gates (and wire) right away
 - Forces us to add buffers just to drive address inputs




Look Inside Each AND8 Gate

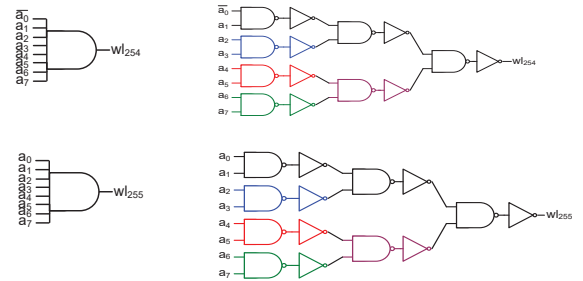

Predecoders


- Use a single gate for each of the shared terms
 - E.g., from $A_0, \bar{A}_0, A_1, \bar{A}_1$, generate four signals: $A_0 A_1, \bar{A}_0 A_1, A_0 \bar{A}_1, \bar{A}_0 \bar{A}_1$
- In other words, we are decoding smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding

Predecoder and Decoder

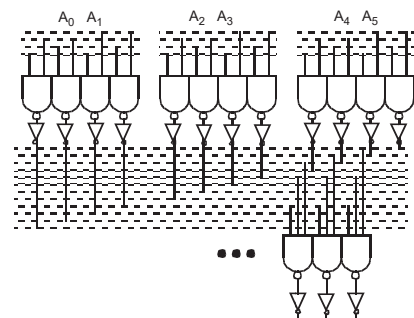

Predecode Options

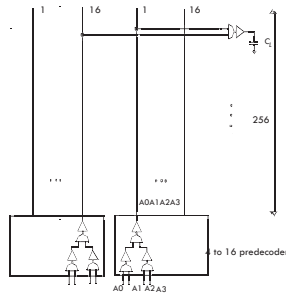- Larger predecode usually better:
- More stages before the long wires
 - Decreases their effect on the circuit
- Fewer number of long wires switches
 - Lower power
- Easier to fit 2-input gate into cell pitch



Administrivia

- Homework 10 posted on Friday, due 11/22
 - No homework during Thanksgiving
- Project checkpoints #2/#3 this week
- Next week:
 - Class lab and discussion on Monday
 - No classes/labs/discussions Tu and We

EECS151/251A L24 DECODERS

Nikolić Fall 2021

17 Berkeley

EECS151/251A L24 DECODERS

Nikolić Fall 2021

18 Berkeley

Building Larger Arrays



Building Larger Custom Arrays

4kB	Dec	4kB	4kB	Dec	4kB
Col, I/O	Pre-Dec	Col, I/O	Col, I/O	Pre-Dec	Col, I/O
4kB	Dec	4kB	4kB	Dec	4kB
4kB	Dec	4kB	4kB	Dec	4kB
Col, I/O	Pre-Dec	Col, I/O	Col, I/O	Pre-Dec	Col, I/O
4kB	Dec	4kB	4kB	Dec	4kB

- Each subarray is 2-8kB
- Hierarchical decoding
- Peripheral overhead is 30-50%
- Delay is wire dominated
- Scratchpads, caches, TLBs

EECS151/251A L24 DECODERS

Nikolić Fall 2021

19 Berkeley


EECS151/251A L24 DECODERS

Nikolić Fall 2021

20 Berkeley


Cascading Memory-Blocks

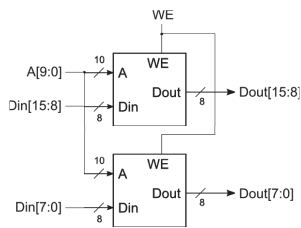How to make larger memory blocks out of smaller ones.
Increasing the width. Example: given 1Kx8, want 1Kx16




Cascading Memory-Blocks

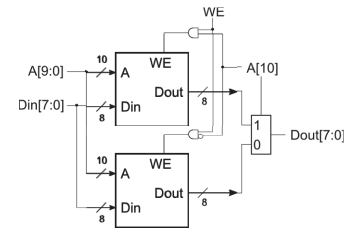How to make larger memory blocks out of smaller ones.
Increasing the depth. Example: given 1Kx8, want 2Kx8




Adding Ports to Primitive Memory Blocks

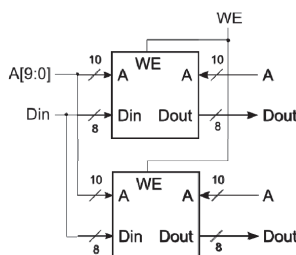Adding a read port to a simple dual port (SDP) memory.
Example: given 1Kx8 SDP, want 1 write & 2 read ports.



Adding Ports to Primitive Memory Blocks

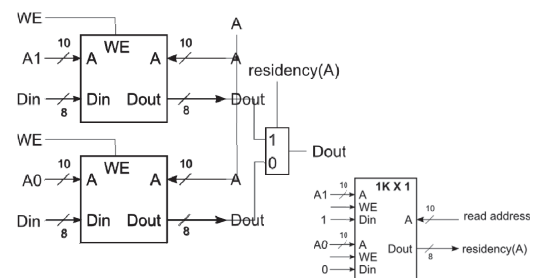How to add a write port to a simple dual-port memory.
Example: given 1Kx8 SDP, want 1 read & 2 write ports.



EECS151/251A L24 DECODERS

Nikolić Fall 2021

23 Berkeley

EECS151/251A L24 DECODERS

Nikolić Fall 2021

24 Berkeley

Caches



Caches (Review from 61C)

Two Different Types of Locality:

- **Temporal locality** (Locality in time): If an item is referenced, it tends to be referenced again soon.
- **Spatial locality** (Locality in space): If an item is referenced, items whose addresses are close by tend to be referenced soon.


By taking advantage of the principle of locality:

- Present the user with as much memory as is available in the cheapest technology.
- Provide access at the speed offered by the fastest technology.
- **DRAM is slow but cheap and dense:**
 - Good choice for presenting the user with a BIG memory system
- **SRAM is fast but expensive and not as dense:**
 - Good choice for providing the user FAST access time.

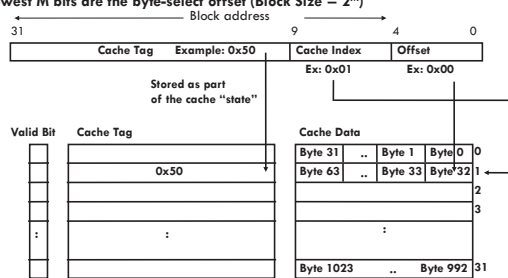Example: 1 KB Direct Mapped Cache with 32-B Blocks

For a 2^N -byte cache:

- The uppermost $(32 - N)$ bits are always the Cache Tag
- The lowest N bits are the byte-select offset (Block Size = 2^N)




Fully Associative Cache

Fully Associative Cache

- Ignore cache Index for now
- Compare the Cache Tags of all cache entries in parallel (expensive...)
- Example: Block Size = 32 B blocks, we need N 27-bit comparators

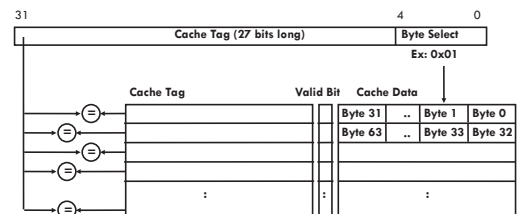By definition: Conflict Miss = 0 for a fully associative cache




Set Associative Cache

N-way set associative: N entries for each Cache Index

- N direct mapped caches operate in parallel

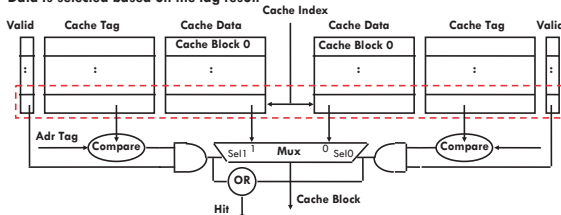Example: Two-way set associative cache


- Cache Index selects a "set" from the cache
- The two tags in the set are compared to the input in parallel
- Data is selected based on the tag result



Disadvantage of Set Associative Cache

N-way Set Associative Cache versus Direct Mapped Cache:

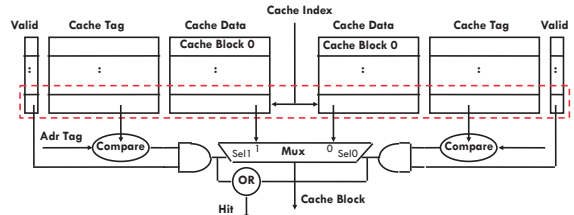- N comparators vs. 1
 - Extra MUX delay for the data
 - Data comes **AFTER** Hit/Miss decision and set selection
- In a direct mapped cache, Cache Block is available **BEFORE** Hit/Miss:
- Possible to assume a hit and continue. Recover later if miss.



Block Replacement Policy

Direct-Mapped Cache

- index completely specifies position which position a block can go in on a miss

N-Way Set Assoc

- index specifies a set, but block can occupy any position within the set on a miss

Fully Associative

- block can be written into any position

Question: if we have the choice, where should we write an incoming block?

- If there's a valid bit off, write new block into first invalid.
- If all are valid, pick a **replacement policy**
 - rule for which block gets "cached out" on a miss.

Block Replacement Policy: LRU

LRU (Least Recently Used)

- Idea: cache out block which has been accessed (read or write) least recently
- Pro: **temporal locality** \Rightarrow recent past use implies likely future use: in fact, this is a very effective policy
- Con: with 2-way set assoc, easy to keep track (one LRU bit); with 4-way or greater, requires more complicated hardware and more time to keep track of this



Summary

- Memory decoding is done hierarchically
 - Wire-limited in large arrays
 - Multiple cache levels make memory appear both fast and big
 - Direct mapped and set-associative cache
- 