

# EECS 151/251A

## Discussion 10/worksheet

Alisha Menon

# Administrativa

- Midterm 2 on Thursday 11/4
- Midterm review session Tuesday 11/2 (problems 4-7)
- How is the project?

# Agenda

- Midterm worksheet/problem examples

# Midterm 2 Topics!

Including:

- CMOS
- Delay optimization and logical effort
- Power and energy
- Wires and RC models
- Arithmetic

# Problem 1 – CMOS Gate (Fa20 m2)

In this problem, use the process that has  $W_n = W_p = 1$  in a reference inverter, and  $\gamma = 1$ .

- (a) Design a complex CMOS gate:  $Y = \overline{(A + B) \cdot C + D}$ . Size the transistors so that the gate has the same pull-up and pull-down strength as a reference inverter.

**251A only:** Also make sure the parasitic delay ( $P$ ) is minimized in your design.

# Problem 1 – CMOS Gate (Fa20 m2)

(b) Calculate the logic effort for each input ( $LE_A, LE_B, LE_C, LE_D$ ).


# Problem 1 – CMOS Gate (Fa20 m2)

(c) **251A only:** Calculate the optimized parasitic delay  $P$ .

# Problem 2 – Logical effort (Fa18 m2)

Reference inverter:  $W_p = 2W_n = W$ ,  $t_{p,inv} = 32\text{ps}$ ,  $\gamma = 2$

 a) Determine path effort and optimal stage effort



b) Find optimal a and b for minimum delay


c) Is this the optimal number of stages for delay? If not, what is?



# Problem 2 – Logical effort (Fa18 m2)

Reference inverter:  $W_p = 2W_n = W$ ,  $t_{p,inv} = 32\text{ps}$ ,  $\gamma = 2$

 
- d) If we could add a single inverter anywhere along the critical path, where would be the best for the minimum total area?



# Problem 2 – Logical effort (Fa18 m2)

Reference inverter:  $W_p = 2W_n = W$ ,  $t_{p,inv} = 32\text{ps}$ ,  $\gamma = 2$

e) “Better” NAND gate logical effort?

 


# Problem 2 – Logical effort (Fa18 m2)

Reference inverter:  $W_p = 2W_n = W$ ,  $t_{p,inv} = 32\text{ps}$ ,  $\gamma = 2$

 f) “Better” NAND gate intrinsic delay parameter (p)?

$$t_{p,inv} = \ln(2) R_{eq,inv} C_{in,inv}$$



g) How does this affect the delay of our original chain?

# Problem 3 (Fa19 m2)

## **4) Delays and Adders (18 points, 22 minutes)**


You are designing a datapath in a brand-new CMOS FinFET technology, where NMOS and PMOS devices have equal strength. In particular, it has only four CMOS gates: 2- input NAND, 2-input NOR, 2-input XOR, and an OAI21 gate ( $Y = \overline{(A+B)C}$ ). Gate capacitance equals drain capacitance per unit area ( $\gamma = 1$ ), and the four gates come in with only one size each, i.e., you do not need to size gates in this problem.

- a) If both the 2-input NAND gate and the 2-input NOR gate have a delay dependence on a fanout,  $f$ , given as  $t_{\text{NAND2}} = t_{\text{NOR2}} = 2\text{ns}(4 + 3f)$ , what is the delay dependence on the fanout of the input C of the OAI21 gate (C is in the critical path)?

$t_{\text{AOI21}} =$  \_\_\_\_\_.

# Problem 3 (Fa19 m2)

 - b) Draw a fast full-adder using the four types of gates and calculate the  $c_i \rightarrow \text{sum}$  and  $c_i \rightarrow c_{out}$  delay. Note that using an OAI21 gate could potentially simplify the logic for  $C_{out}$ . Assume the capacitance driven by the sum and the carry bits is equal to the capacitance of inputs  $a_i$ ,  $b_i$  and  $t_{XOR2} = 2\text{ns} (8 + 8f)$ .




$t_{FA, C_i \rightarrow C_o} =$  \_\_\_\_\_.

$t_{FA, C_i \rightarrow S} =$  \_\_\_\_\_.

# Problem 3 (Fa19 m2)

 - c) Complete the drawing and label all inputs and outputs for an 4-bit ripple-carry adder in figure below by using full-adder (FA) cells from part b). Inputs are  $a[3:0]$  and  $b[3:0]$  and there is no carry-in to the least-significant bit.




# Problem 3 (Fa19 m2)

- d) Find the critical path delay for the circuit in part c), if the capacitance driven by the sum and the carry bits is equal to the input  $a_i$ ,  $b_i$  capacitance. If you are not confident in your answer in part b), you can express the delay in terms of  $t_{FA,Ci \rightarrow Co}$ , and  $t_{FA,Ci \rightarrow S}$

Critical path = \_\_\_\_\_.

# Problem 4 Logical effort (Sp13)


Logical effort and  
intrinsic delay?

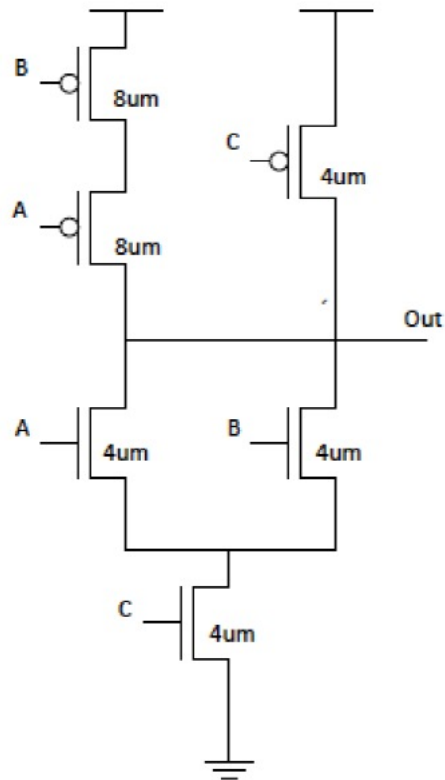



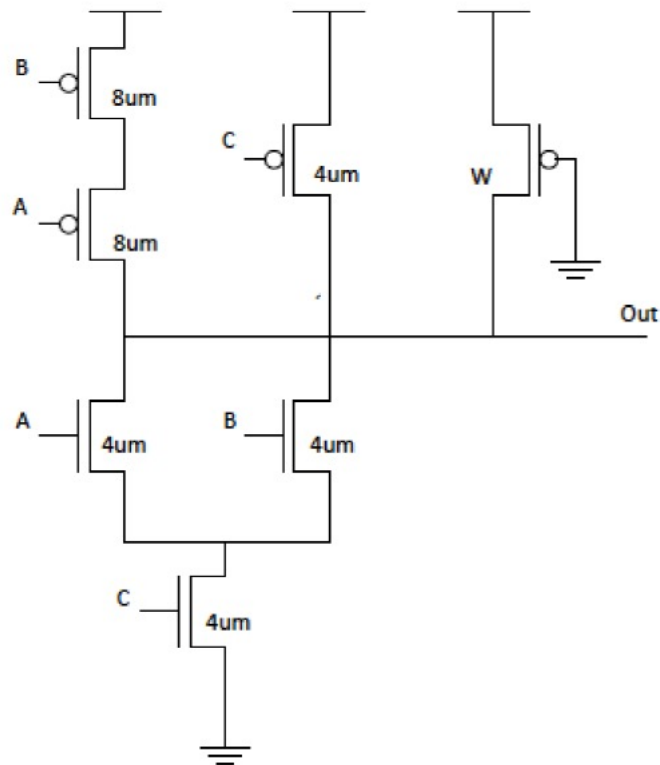
# Problem 4 Logical effort (Sp13)

- Made a mistake in layout! What is the effect on L-H transition? H-L transition?


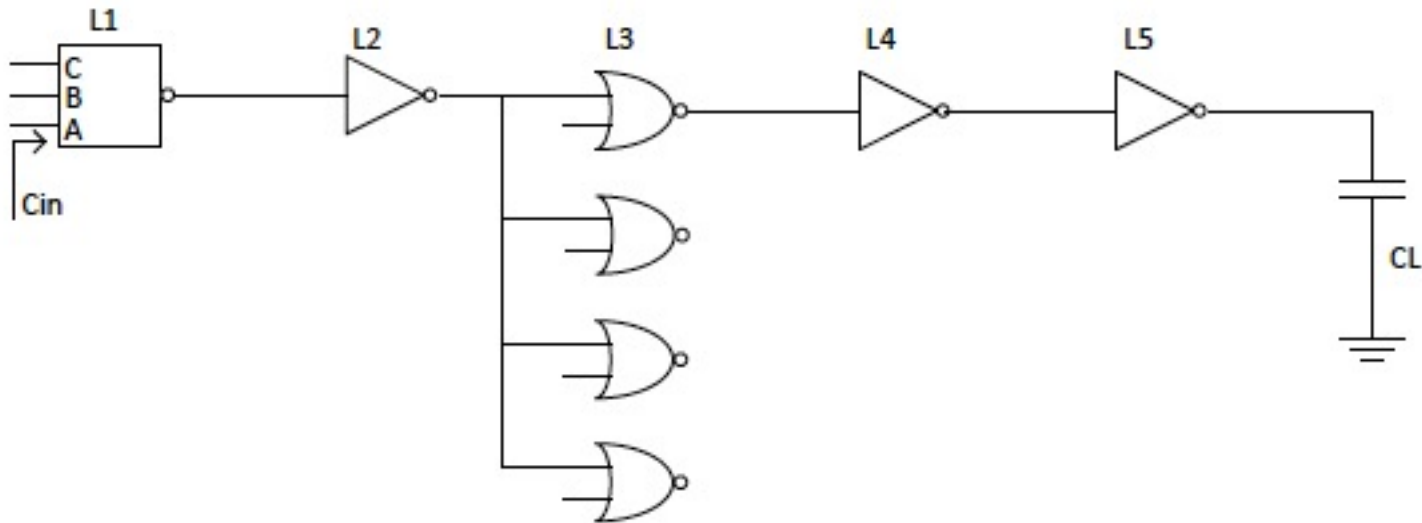
# Problem 4 Logical effort (Sp13)

- Delay optimization with **fixed gate**
- Using A input with  $C_{in} = 24 \text{ fF}$ ,  $C_L = 75C_{in}$




# Problem 5 – Wires and repeaters (fa18 m2)

Min. inverter: drive resistance  $R_d$ , input cap  $C_{in}$ , intrinsic cap  $C_{int}$

Wire:  $r_w$ ,  $c_w$  (per unit length)

 a + b) Propagation delay from *in* to *out* (using distributed model for wires)




# Problem 5 – Wires and repeaters (fa18 m2)

Min. inverter: drive resistance  $R_d$ , input cap  $C_{in}$ , intrinsic cap  $C_{int}$

Wire:  $r_w$ ,  $c_w$  (per unit length)

 c) Derive reduction in delay by increasing the first inverter as much as possible:




# Problem 5 – Wires and repeaters (fa18 m2)

Min. inverter: drive resistance  $R_d$ , input cap  $C_{in}$ , intrinsic cap  $C_{int}$

Wire:  $r_w$ ,  $c_w$  (per unit length)

d) Propagation delay with repeater:

 


# Problem 5 – Wires and repeaters (fa18 m2)

Min. inverter: drive resistance  $R_d$ , input cap  $C_{in}$ , intrinsic cap  $C_{int}$


Wire:  $r_w$ ,  $c_w$  (per unit length)

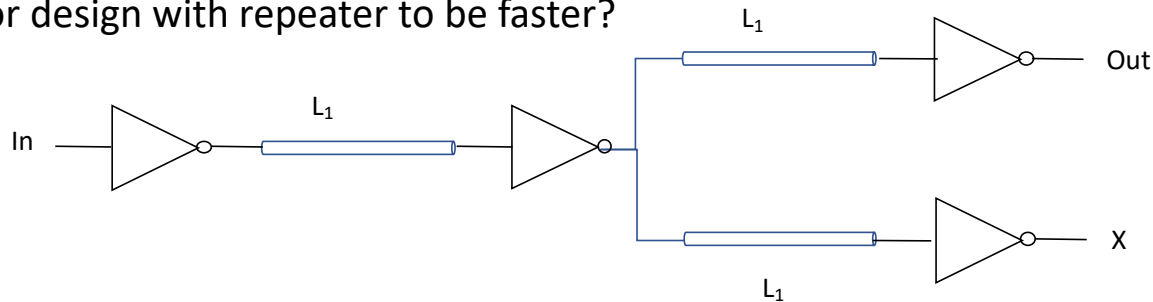e) Conditions for design with repeater to be faster?


 
# Problem 6 - Wires and Energy (Sp16)


A NOR gate (G1) with input capacitance  $C_1$  is driving a wire with total resistance  $R_W$  and total capacitance  $C_W$ , and an inverter with input capacitance  $C_2$ . Inverter G2 is driving an external load of  $C_L$ . The on-resistance of G1 and G2 are  $R_1$  and  $R_2$ , respectively. Assume  $\gamma = 1$  and  $2R_N = R_P$ . The power supply has a voltage of  $V_{DD}$ .



a) Determine the delay between input A to Out
 
# Problem 6 - Wires and Energy (Sp16)

A NOR gate (G1) with input capacitance  $C_1$  is driving a wire with total resistance  $R_W$  and total capacitance  $C_W$ , and an inverter with input capacitance  $C_2$ . Inverter G2 is driving an external load of  $C_L$ . The on-resistance of G1 and G2 are  $R_1$  and  $R_2$ , respectively. Assume  $\gamma = 1$  and  $2R_N = R_P$ . The power supply has a voltage of  $V_{DD}$ .



b) Assume input A is driven by a square-wave signal of frequency  $f_{clk}$  and input B is driven by a square wave signal of frequency  $\frac{1}{3}f_{clk}$ . Derive an expression for total dynamic power consumption of the circuit.



# Problem 7 - adder (Sp19 final)

22. Adder Design [5pts]: The carry-select technique presented in lecture can be applied hierarchically. Imagine applying the technique in a binary way—a larger adder is divided in half using the carry-select and then the same technique is applied to the sub-adders, etc. The process would stop at 4-bit ripple adders.

(a) Assuming a FA and a MUX both have unit delay (delay = 1), what would be the delay (from data in to carry out) of a 32-bit adder?

(b) How would the delay scale with the size of the adder?

# Problem 7 - adders (Sp19 final)

23. Adder Design [6pts]: A carry-lookahead adder used to add  $A$  to  $B$  is organized into groups of 4-bits. A group has carry into the group,  $c_{i-1}$  and carry out of the group,  $c_{i+3}$ .
- (a) In terms of the propagate and generate signals,  $p_i$  and  $g_i$ , of the individual bit stages, write an expression for the *group propagate signal*,  $P$  and *group generate signal*,  $G$ .
  - (b) Write an expression for  $c_{i+3}$  based on the group  $P$  and  $G$ .
  - (c) Write an expression for the bit stage sum output,  $s_i$ .