



EECS151 : Introduction to Digital Design and ICs

Lecture 21 – Dividers, Latches

Bora Nikolić



Pentium FDIV Bug (from Wikipedia)

The Pentium FDIV bug is a hardware bug affecting the floating-point unit (FPU) of the early Intel Pentium processors. Because of the bug, the processor would return incorrect binary floating point results when dividing certain pairs of high-precision numbers. The bug was discovered in 1994 by Thomas R. Nicely, a professor of mathematics at Lynchburg College. Missing values in a lookup table used by the FPU's floating-point division algorithm led to calculations acquiring small errors. While these errors would in most use-cases only occur rarely and result in small deviations from the correct output values, in certain circumstances the errors can occur frequently and lead to more significant deviations.



EECS151 L21 DIVIDERS, LATCHES

Nikolić Fall 2021



Review

- Binary multipliers have three blocks:
 - Partial-product generation (NAND or Booth)
 - Partial-product compression (ripple-carry array, CSA or Wallace)
 - Final adder
- Multipliers are often pipelined
- Constant multipliers can be optimized for size/speed
- Shifters and crossbars are common building blocks in digital systems
 - Often require customization

EECS151 L21 DIVIDERS, LATCHES

Nikolić Fall 2021



Dividers

Pencil-And-Paper Division

	1512	quotient
3	4537	dividend
divisor	3000	divisor * $q_1 * 10^i$
	1537	partial remainder
	1500	
	0037	
	0030	
	0007	
	0006	
	0001	remainder

Division is an iterative process:

$$r(i) = r(i+1) - q_i * D * 10^i$$

We usually 'guess' q_i

EECS151 L21 DIVIDERS, LATCHES

Nikolić Fall 2021




Restoring Divider

- Assume $q_i = 1$
- Subtract divisor from r ; check if $r(i) \geq 0$
 - if $r(i) > 0$, guess was good ($q_i = 1$)
 - if $r(i) < 0$, restore the value by adding divisor, $q_i = 0$
- Shift divisor to right
- Repeat n times

More efficient to shift the remainder right

 n shifts
 n subtractions
 $n/2$ restorations



Non-Restoring Divider

- Doesn't restore if $r(i) < 0$
- Instead, adds the divisor in the next iteration
 - n shifts
 - n additions/subtractions

Faster Dividers

- Divide in a higher radix than 2 (typically 4, i.e. guess q_i, q_{i+1})
- Keep the partial remainders in redundant form
- Sweeney-Robertson-Tocher (SRT) algorithm
 - Used in many processors




Timing

EECS151 L21 DIVIDERS, LATCHES

Nikolić Fall 2021




Synchronous Timing: Review

 


Latch Parameters

- Latch is transparent high or low

 

 
```
module latch
(
    input clk,
    input d,
    output reg q
);
always @(clk or d)
begin
    if ( clk )
        q <= d;
    end
endmodule
```




Delays can be different for rising and falling data transitions

Flip-Flop Parameters

- Flip-flop is edge-triggered

 

 
```
module flipflop
(
    input clk,
    input d,
    output reg q
);
always @(posedge clk)
begin
    q <= d;
end
endmodule
```



Delays can be different for rising and falling data transitions

Clock Uncertainties

 - Clock arrival time varies in space and time




Sources of clock uncertainty

Clock Nonidealities

- Clock skew
 - Spatial variation in temporally equivalent clock edges; deterministic + random, t_{sk}
- Clock jitter
 - Temporal variations in consecutive edges of the clock signal; modulation + random noise
 - Cycle-to-cycle (short-term) t_{js}
 - (there also exists long-term jitter t_{jl})
- Variation of the pulse width
 - Important for level sensitive clocking with latches


Clock Skew and Jitter

 - Both skew and jitter affect the effective cycle time
- Only clock distribution skew affects the race margin



Timing Constraints

 - First flip-flop launches data on the first clock edge, the second one captures on the second clock edge




Minimum cycle time is set by the longest logic path:

$$T - t_{sk} - t_j = t_{c-q} + t_{su} + t_{logic,max}$$

Worst case is when receiving edge arrives early

Timing Constraints

 - Launching flip-flop shouldn't contaminate its own data




Hold time constraint:

$$t_{c-q} + t_{logic,min} > t_{hold} + t_{sk}$$

Worst case is when receiving edge arrives late
Race between data and clock

Slack

- Visualizing arrival times

 

EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Timing Analysis

- Report timing

Startpoint: dig_agc_0/int_term_reg_0
(rising edge-triggered flip-flop clocked by clk_agc)
Endpoint: dig_agc_0/int_term_reg_0
(rising edge-triggered flip-flop clocked by clk_agc)

Point	Fanout	Derate	Incr	Path	Voltage
clock clk_agc (rise edge)	0.00	0.00			
clock source latency	3.13	3.13 r			
timing_control_0/C1276/Y (AND2X3)	0.00	3.13 r	3.00		
timing_control_0/o_clk_agc (net)	2	0.00	3.13 r		
dig_agc_0/BUF28_G6B112/A (BUF28)	0.00	0.00	3.13 r	3.00	
dig_agc_0/o_clk_agc_G6B112 (net)	15	0.00	3.91 r		
dig_agc_0/int_term_reg_0/CP (SDFFCQX2)	0.01	0.01	3.92 r	3.00	
clock reconvergence pessimism	0.00	3.92			
clock uncertainty	0.10	4.02 r	4.02		
dig_agc_0/int_term_reg_0/CP (SDFFCQX2)	0.00	4.02 r			
library hold time	-0.48	3.54			
data required time		3.54			
data arrival time		-5.57			
slack (MET)		2.03			

EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Administrivia

- Midterm 2 scores released
 - Final can clobber either midterm!
- Homework 9 posted on Friday, due 11/15
 - One more homework before Thanksgiving
- Project checkpoints #2 this week
- Thursday is a holiday (Veterans' Day)


EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Midterm 2

 - EECS151
 - Max: 60.5/61
 - Average: 42.7/61 (70%)
- EECS251A
 - Max: 71/71
 - Average: 59.2/71 (83%)




EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Latch-Based Timing

 - Is there a possible timing problem in this path?



Latch-Based Timing




EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Latch-Based Timing

- Single clock phase

 

- Possibility of a race condition
 - Needs timing analysis (EE241B/EECS251B)


EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021



Latch-Based Timing

- Two clock phases

 

- Two consecutive latches are never transparent at the same time
 - Conservative

EECS151 L21 DIVIDERS, LATCHES

Hkaidi Fall 2021







Latches


Cross-Coupled Inverter

- Positive feedback stores the data

  

Writing into a Static Latch

 Use the clock as a control signal (to break the positive feedback), that distinguishes between the transparent and opaque states




Converting into a MUX

Forcing the state (functionality depends on sizing)


Tri-State Inverter

- Out is Z when Clk=0



- Latch

 

Clk-Q Delay

 


Setup and Hold Times

  


Setup-Hold Time Illustrations

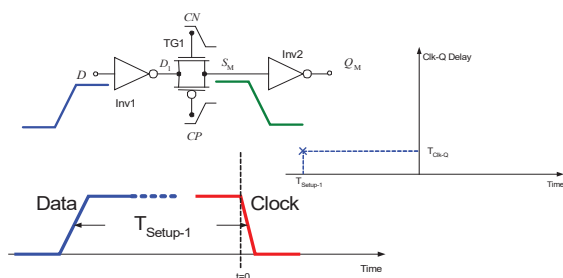Circuit before clock arrival (Setup-1 case)



Setup-Hold Time Illustrations

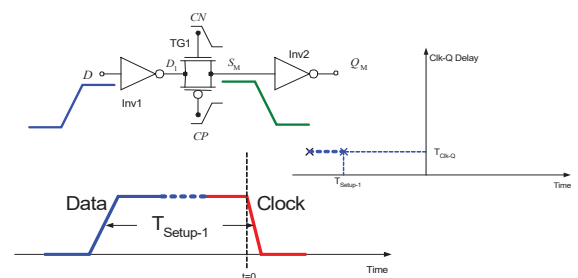Circuit before clock arrival (Setup-1 case)





Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021



Nikolić Fall 2021




Flip-Flops



Types of Flip-Flops


Latch Pair
(Master-Slave)

Pulse-Triggered Latch

 


Transmission Gate Flip-Flop

- Two back-to-back latches

 


Aside: Inverter Fork

 - Often found in flip-flops: equalize Ck, Ckb delays
- Logical effort = ?



Clk-Q, Setup and Hold Times

 

Review

- Binary division is a slow, iterative process
- Non-restoring division speeds it up
- SRT divider, higher radix, redundant number representation
- Timing analysis for early and late signal arrivals
- Flip-flop-based pipelines are a lot easier to analyze than latch-based ones
- Latches are based on positive feedback
- Clk-Q delay calculated similarly to combinational logic
- Setup, hold defined as D-Clk times that correspond to Clk-Q delay increases
- Flip-flop is typically a latch pair