




EECS151 : Introduction to Digital Design and ICs

Lecture 5 – Verilog III

Bora Nikolić



Mojo Lens - AR Contact Lenses for Real People
Michael Wiemer and Renaldi Winoto, Mojo Vision

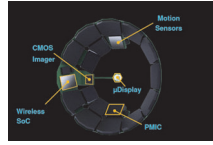

HotChips 33

EECS151/251A L05 VERILOG III



Review

- Verilog is the most-commonly used HDL
- We have seen combinatorial constructs
 - Assign statement
 - Always blocks
- Practice is the best way to learn a new language...



Sequential Logic, Take 2

EECS151/251A L05 VERILOG III


Latches and Flip-Flops

- Flip-flop is edge-triggered, latch is level-sensitive

- D Flip-flop

- Rising edge


Signifies 'edge triggered'

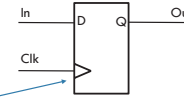


- D Latch

- Transparent HIGH

Level sensitive if there is no 'edge'

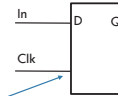

- Transparent LOW



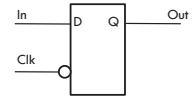


EECS151/251A L05 VERILOG III



Timing

- Combinational logic timing

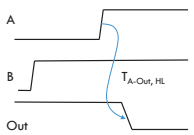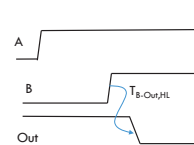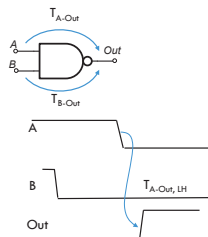
A is arriving late
(is in the critical path)B is arriving late
(is in the critical path)

HL and LH transition differ
 t_{A-Out} and t_{B-Out} differ
In CMOS, propagation delay depends on:
- Gate type, size (output resistance)
- Capacitive loading
- Input slope

EECS151/251A L05 VERILOG III


Timing

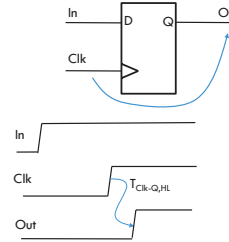- Flip-flop timing
(latch timing will be covered later)



- Setup and hold times

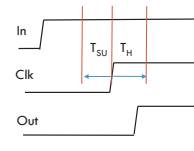- Data cannot change in the interval of setup time **before** the clock edge to hold time **after** the clock edge




EECS151/251A L05 VERILOG III




Register

- 4-bit register

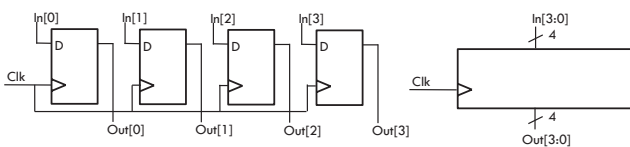

- Accumulator

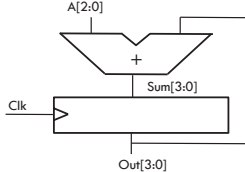

EECS151/251A L05 VERILOG III

Administrivia

- Homework 2 is due this Friday
 - Homework 3 will be posted this week
- Lab 3 this week



EECS151/251A L05 VERILOG III



Sequential Logic in Verilog

State Elements in Verilog

Always blocks are the only way to specify the "behavior" of state elements. Synthesis tools will turn state element behaviors into state element instances.

D-flip-flop with synchronous set and reset example:

```
module dff(q, d, clk, set, rst);
    input d, clk, set, rst;
    output q;
    reg q;


    always @(posedge clk)
        if (rst)
            q <= 1'b0;
        else if (set)
            q <= 1'b1;
        else
            q <= d;
endmodule
```

keyword

"always @(posedge clk)" is key to flip-flop inference.

This gives priority to reset over set and set over d.

On FPGAs, maps to native flip-flop.

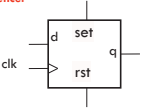


Unlike logic gates, there are no primitive flip-flops in Verilog. Although, it is possible to instantiate FPGA or standard-cell specific flip-flops.

The Sequential always Block


Combinational
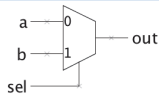
```
module comb(input a, b, sel,
            output reg out);
    always (*) begin
        if (sel) out = b;
        else out = a;
    end
endmodule
```



Sequential

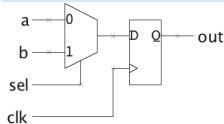
```
module seq(input a, b, sel, clk,
            output reg out);
    always @(posedge clk) begin
        if (sel) out <= b;
        else out <= a;
    end
endmodule
```



Latches vs. Flip-Flops


Flip-Flop
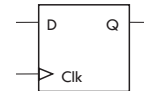
```
module flipflop(
    input clk,
    input d,
    output reg q
);
    always @(posedge clk)
        q <= d;
endmodule
```



Latch
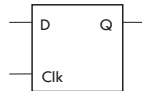
```
module latch(
    input clk,
    input d,
    output reg q
);
    always @(clk or d)
        begin
            if (clk)
                q <= d;
        end
endmodule
```



Importance of the Sensitivity List

- The use of `posedge` and `negedge` makes an `always` block sequential (edge-triggered)

D-Register with **synchronous** clear

```
module dff_sync_clear(
    input d, clearb, clock,
    output reg q);
    always @(posedge clock)
        begin
            if (!clearb) q <= 1'b0;
            else q <= d;
        end
endmodule
```

always block entered only at each positive clock edge

D-Register with **asynchronous** clear

```
module dff_async_clear(
    input d, clearb, clock,
    output reg q);
    always @(negedge clearb or posedge clock)
        begin
            if (!clearb) q <= 1'b0;
            else q <= d;
        end
endmodule
```

always block entered immediately when (active-low) clearb is asserted

Note: The following is incorrect syntax: `always @(clear or negedge clock)`
If one signal in the sensitivity list uses `posedge/negedge`, then all signals must.

- Assign any signal or variable from only one `always` block.
- Be wary of race conditions: `always` blocks with same trigger execute concurrently...

Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.

- Blocking assignment (`=`): evaluation and assignment are immediate

```
always (*) begin
    x = a | b; // 1. evaluate a|b, assign result to x
    y = a ^ b ^ c; // 2. evaluate a^b^c, assign result to y
    z = b & ~c; // 3. evaluate b^~c, assign result to z
end
```


- Nonblocking assignment (`<=`): all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (even those in other active `always` blocks)

```
always (*) begin
    x <= a | b; // 1. evaluate a|b, but defer assignment to x
    y <= a ^ b ^ c; // 2. evaluate a^b^c, but defer assignment to y
    z <= b & ~c; // 3. evaluate b^~c, but defer assignment to z
    // 4. end of time step: assign new values to x, y and z
end
```

Sometimes, as above, both produce the same result. Sometimes, not!

Assignment Styles for Sequential Logic

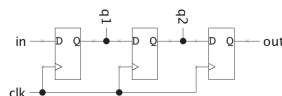What we want:
Register-based digital delay line
(a.k.a. shift-register)




Use Nonblocking for Sequential Logic

```
always @(posedge clk) begin
    q1 <= in; // uses old q1
    q2 <= q1; // uses old q2
    out <= q2;
end
```

```
always @(posedge clk) begin
    q1 = in; // uses new q1
    q2 = q1; // uses new q2
    out = q2;
end
```

("old" means value before clock edge, "new" means the value after most recent assignment)

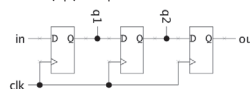"At each rising clock edge, q1, q2, and out simultaneously receive the old values of in, q1, and q2."



"At each rising clock edge, q1 = in. After that, q2 = q1. After that, out = q2. Therefore out = in."




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- Guideline: use nonblocking assignments for sequential `always` blocks

```
module nonblocking(
    input in, clk,
    output reg out
);
    reg q1, q2;
    always @(posedge clk) begin
        q1 <= in;
        q2 <= q1;
        out <= q2;
    end
endmodule
```

```
module blocking(
    input in, clk,
    output reg out
);
    reg q1, q2;
    always @(posedge clk) begin
        q1 = in;
        q2 = q1;
        out = q2;
    end
endmodule
```

Example: A Simple Counter

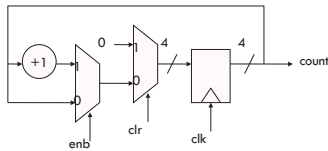


```
// 4-bit counter with enable and synchronous clear
module counter(input clk,enb,clr,
               output reg [3:0] count);
    always @(posedge clk) begin
        count <= clr ? 4'b0 : (enb ? count+1 : count);
    end
endmodule
```

EECS151/251A, L05 VERILOG III

Berkeley

Example - Parallel to Serial Converter

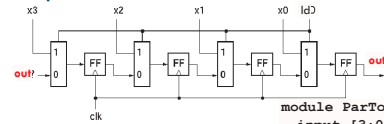

```
module ParToSer(ld, X, out, clk);
    input [3:0] X;
    input ld, clk;
    output out;

    reg [3:0] Q;
    wire [3:0] NS;

    assign NS =
        (ld) ? X : {Q[0], Q[3:1]};

    always @ (posedge clk)
        Q <= NS;

    assign out = Q[0];
endmodule
```

Specifies the muxing with "rotation"

forces Q register (flip-flops) to be rewritten every cycle

connect output

EECS151/251A, L05 VERILOG III

Berkeley

Simplified Verilog Guidelines

• Combinational logic:

- Continuous Assignment:


```
assign a = b & c;
```
- Always block with @(*)


```
always @(*) begin
    a = b & c; // blocking statement
end
```

assign statement → wire

always statement → reg

• Sequential logic:

- Always block with @(posedge clk)

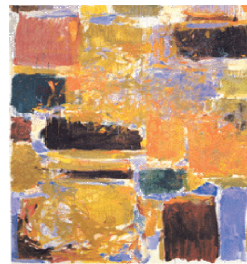

```
always @(posedge clk) begin
    a <= b & c; // nonblocking statement
end
```

Verilog in EECS 151/251A

- We use behavioral modeling at the bottom of the hierarchy
- Use instantiation to 1) build hierarchy and, 2) map to FPGA and ASIC resources not supported by synthesis.
- Favor continuous assign and avoid always blocks unless:
 - No other alternative: ex: state elements, case
 - Helps readability and clarity of code: ex: large nested if else
- Use named ports.
- Verilog is a big language. This is only an introduction.
 - Harris & Harris book chapter 4 is a good source.
 - Be careful of what you read on the web. Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!

Verilog vs. SystemVerilog

- always** statements in Verilog can be used to infer flip-flops, latches or logic
 - Depends on the sensitivity list and the statement
 - Easy to create confusion
- System Verilog adds disambiguation:
 - always_ff** for flip-flops
 - always_latch** for latches
 - always_comb** for combinational logic



Verilog Testbenches

Simulating the Circuit

- Once you have a circuit in Verilog (device under test, or DUT), you would like to test it
- Instantiate the DUT and supply its inputs via a testbench
 - Simple
 - Comprehensive
 - Random
- initial** statement supplies the stimuli

Testbench basics

• Example clock

```
reg clk;

initial clk = 0;
always #('CLOCK_PERIOD/2) clk <= ~clk;
```

• Example inputs

```
initial begin
    in <= 4'h0;
    @(negedge clk) in<= 4'h1;
    ...
    (sets up inputs on the negedge, so they are ready at the posedge)
```

Only small DUTs can be tested exhaustively

EECS151/251A, L05 VERILOG III

Berkeley

EECS151/251A, L05 VERILOG III

Berkeley

SystemVerilog

- SystemVerilog adds many more verification features
 - We will touch on assertions and covers
(relates to CS70)

Final Thoughts on Verilog Examples

Verilog looks like C, but it describes hardware:

Entirely different semantics: multiple physical elements with parallel activities and temporal relationships.

A large part of digital design is knowing how to write Verilog that gets you the desired circuit. First understand the circuit you want then figure out how to code it in Verilog. If you try to write Verilog without a clear idea of the desired circuit, you will struggle.

As you get more practice, you will know how to best write Verilog for a desired result.

Be suspicious of the synthesis tools! Check the output of the tools to make sure you get what you want.

Clicker Question


- How many stimuli to exhaustively test a 32-b adder?
 - 32
 - 64
 - 65,536
 - 4,294,967,296
 - 18,446,744,073,709,551,616

www.yellkey.com/perform


Combinational Logic

Combinational Logic

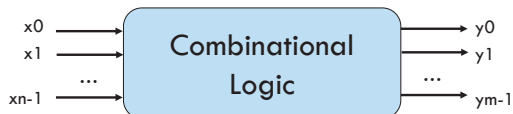- The outputs depend **only** on the current values of the inputs.
 - Memoryless: compute the output values using the current inputs.



Combinational Logic Example

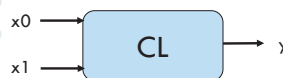

Boolean Equations:

$$y = x0 \text{ OR } x1 \\ = x0 + x1$$


Truth Table Description:

x0	x1	y
0	0	0
0	1	1
1	0	1
1	1	1

Gate Representations:



Relationship Among Representations

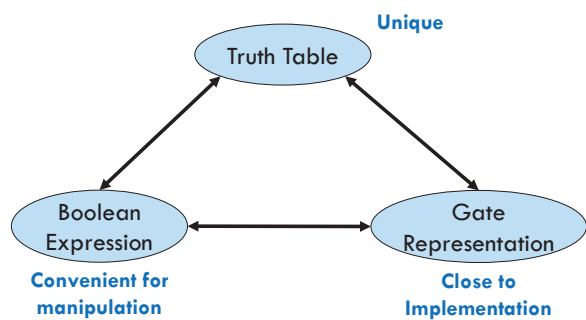

Boolean Algebra


Boolean Algebra Background

- Logic: The study of the principles of reasoning.
- The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
 - His variables took on TRUE, FALSE.
- Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits.




Boolean Algebra Fundamentals

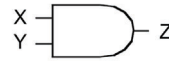
- Two elements $\{0, 1\}$
- Two binary operators: AND (\cdot) OR ($+$)
- One unary operator: NOT ($'$, \neg)



X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

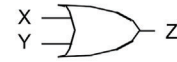

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

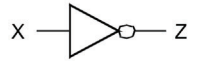

X	Z
0	1
1	0

Boolean Operations

- Given two variables (x, y), 16 logic functions

X	Y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Laws of Boolean Algebra

- Identities, null elements:**
 - $X+0=X, X \cdot 1=X$
 - $X+1=1, X \cdot 0=0$
- Idempotency:**
 - $X+X=X, X \cdot X=X$
- Complements:**
 - $X+X'=1, X \cdot X'=0$
- Commutativity:**
 - $X+Y=Y+X, X \cdot Y=Y \cdot X$
- Associativity:**
 - $(X+Y)+Z=X+(Y+Z)=X+Y+Z$
 - $(X \cdot Y) \cdot Z=X \cdot (Y \cdot Z)=X \cdot Y \cdot Z$
- Distributivity:**
 - $X \cdot (Y+Z) = (X \cdot Y) + (X \cdot Z)$
 - $X + (Y \cdot Z) = (X+Y) \cdot (X+Z)$
- Duality:**
 - AND \leftrightarrow OR and vice versa
 - $0 \leftrightarrow 1$ and vice versa
 - Leave literals unchanged

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \cdot)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \cdot, +)\}$$

Literals are variables or their complements

Proving Distributive Law

- $X \cdot (Y+Z) = (X \cdot Y) + (X \cdot Z)$

X	Y	Z	$(Y+Z)$	$X \cdot (Y+Z)$	$(X \cdot Y)$	$(X \cdot Z)$	$(X \cdot Y) + (X \cdot Z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Proving Distributive Law


- $X \cdot (Y+Z) = (X \cdot Y) + (X \cdot Z)$

X	Y	Z	$(Y+Z)$	$X \cdot (Y+Z)$	$(X \cdot Y)$	$(X \cdot Z)$	$(X \cdot Y) + (X \cdot Z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

DeMorgan's Law


- Theorem for complementing a complex function.

$$(x + y)' = x' y'$$

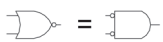

x	y	x'	y'	$(x+y)'$	$x' y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

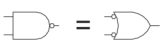


x	y	x'	y'	$(x y)'$	$x' + y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

DeMorgan's Law


- Procedure for complementing a complex function.

$$(x + y)' = x' y'$$

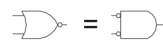

x	y	x'	y'	$(x+y)'$	$x' y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

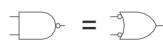

x	y	x'	y'	$(x y)'$	$x' + y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0



Summary

- Sequential logic uses flip-flops and (sometimes) latches
- Flip-flops and latches are inferred in Verilog
 - Always blocks
- Practice is the best way to learn a new language...
- Blocking and non-blocking assignments
- Combinational logic block outputs depend only on its inputs
- Boolean algebra can be used for manipulation and simplification of Boolean equations

