

EECS 151/251A

Discussion 2

Daniel Grubb
9/7, 9/8

About Me (Daniel Grubb)




- EECS graduate student
 - Advised by Bora
 - EECS undergrad at Cal too
- I took EECS151 4.5 years ago... from Vighnesh and Bob!
 - Lots of course staff experience, so learn and ask questions
- I've been in Berkeley (and northern California) for a while now, so ask me about suggestions for things to do/see/eat!

EECS151 General Course Recap

- Stay on top of your work for this class
 - You can get a job straight from this course!
- I recommend looking over both ASIC and FPGA labs - useful info in both
 - FPGA - focus on Verilog, practical circuits, physical demos
 - ASIC - focus on design, tool flow
- Piazza and office hours - use liberally!
- The suggested texts are extremely helpful!
 - Lots of history lessons in courses like this

Textbooks

- **Recommended** [Digital Design and Computer Architecture](#), 2nd ed, David Money Harris & Sarah L. Harris (H & H)
- **Recommended** [Digital Integrated Circuits: A Design Perspective](#), Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolić (RCN)
- **Useful** [Computer Organization and Design RISC-V Edition](#), David Patterson and John Hennessy (P&H)
- **Useful** [CMOS VLSI Design](#), Neil Weste, David Harris (W&H)

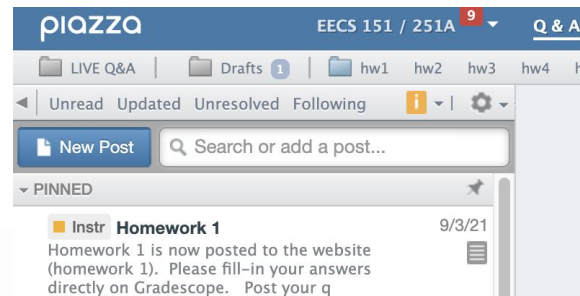

Agenda



- Administrivia
- Lecture recap
- Digital? CMOS Inverter
- Verilog primer

Administrivia

- Reminder that Monday & Wednesday discussions are in-person only
- Homework 1 due on Friday, 9/10
- Monday labs will roll-over to the next week due to the holiday
- Lab 1 due on Friday, 9/10
- Lectures
 - Ironing out the overflow room, wifi
 - Watch the recorded ones - power, performance, cost, robustness
 - The course will explore quantitative optimization of these metrics
- Reminder that labs are individual and projects will be in pairs


What has the course discussed so far?

  - Semiconductor trends
 - Moore's Law? Dennard scaling?
- Design process
 - Abstraction, hierarchy
- Boolean logic
- ASICs and FPGAs
 - Full custom -> standard cells; CAD
 - Gate arrays -> FPGAs
- Lots of background
 - Now starting engineering material




Exclusive OR
XOR

$$\text{Out} = A \oplus B$$




 


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

 



Digital?: CMOS Inverter

    - Complementary Metal Oxide Semiconductor
 - Inverter has 1 NMOS and 1 PMOS
- in: low \rightarrow out: high; in: high \rightarrow out: low
 - Low (0): $V_{in} < V_L$ or $V_{in} < V_{th,n}$
 - High (1): $V_{in} > V_H$ or $V_{in} > V_{DD} - V_{th,p}$
- NMOS and PMOS each have an “on” and “off” resistance
- Voltage Transfer Curve (VTC)
 - Mid/switching-point is a function of PMOS vs NMOS strength





Noise Margins

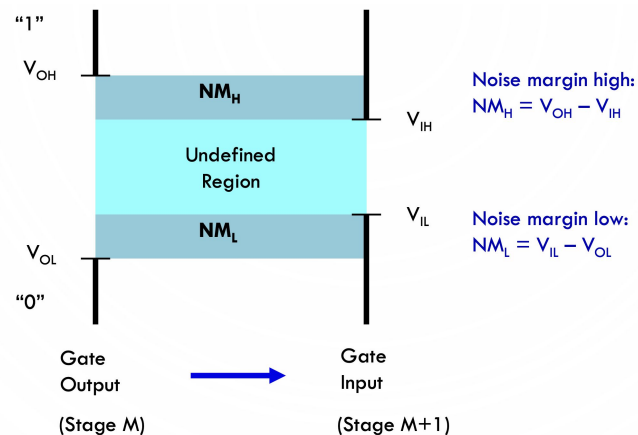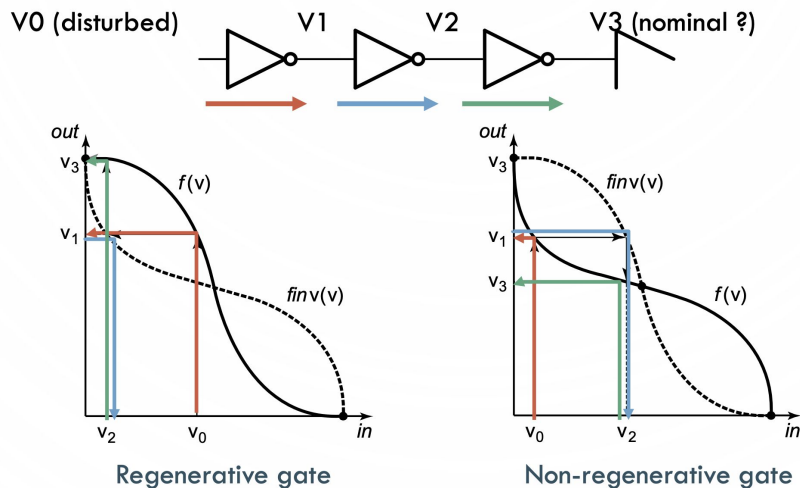- Noisy, but still want 1s and 0s (digital)
 - “Restoration” / “regeneration” property
- Noise margins
 - The amount of noise that can be tolerated such that the signal can be correctly interpreted by the next gate
 - Eg. in a chain of inverters
- VTC is low gain/stable near supplies, high gain regime between



Hardware Description Languages

- Languages that describe hardware
 - Writing hardware, not software! (despite some common syntax)
 - Hardware is running all in parallel at all times
- Examples
 - Verilog, VHDL, SystemVerilog, Chisel, ...
 - Verilog is language of choice for this course and most companies
- What is RTL? -> Register Transfer Level
 - Describe synchronous digital systems with operations on signals flowing between registers
- Not everything you can write is “synthesizable”
- Build up systems in lab from very simple -> complex!

  

```
module mux2 (  
    input [1:0] in,  
    input select,  
    output out);  
  
    assign out = select ? in[1] : in[0];  
  
endmodule
```

Verilog

- Let's go over some of the Verilog Primer Slides and some previous discussion Verilog slides
- The primer slides and some other resources can be found on the course website

Blocking vs Non-Blocking

Blocking

```
reg c, out;  
wire a, b, d;  
always @(*) begin  
    c = a | b;  
    out = c & d;  
end
```

Non-Blocking

```
reg c, out;  
wire a, b, clk;  
always @(posedge clk) begin  
    //use val of 'out' before clk edge  
    c <= out | a;  
    //use val of 'c' before clk edge  
    out <= c & b;  
end
```

- Don't mix blocking and non-blocking

Revisiting Last Discussion Examples

```
module mux2 (  
    input [1:0] in,  
    input select,  
    output out);  
assign out = (select == 1) ? in[1] : in[0]  
endmodule
```

```
module mux2_behav (in,out,out_b)  
    input [0:1] in;  
    input select;  
    output out;  
    output out_b;  
always @ (in)  
    if (select == 1)  
        out = in[1]  
        out_b = ~in[1]  
    else  
        out = in[0]  
        out_b = ~in[0]  
endmodule
```

Corrected Example

```
module mux2 (  
    input [1:0] in,  
    input select,  
    output out);  
assign out = select ? in[1] : in[0];  
endmodule
```

```
module mux2_behav (in,select,out,out_b);  
    input [1:0] in;  
    input select;  
    output reg out;  
    output reg out_b;  
    always @ (*) begin  
        if (select == 1) begin  
            out = in[1];  
            out_b = ~in[1];  
        end else begin  
            out = in[0];  
            out_b = ~in[0];  
        end  
    end  
end  
endmodule
```

What you'll do in lab 2:

- Verilog basics
- Simulation
- Very helpful to draw out diagrams
 - For labs and the project, try to keep a set of digital diagrams that you can edit and add to
 - They will help you design more efficiently and can go straight into your project report!
 - Draw.io, omnigraffle, etc.
- Learn by doing!
 - Writing Verilog
 - Simulating and writing testbenches
 - Debugging
 - Check your logs for warnings -> the tools can sometimes obscure errors

