

EECS151 : Introduction to Digital Design and ICs

Lecture 8 – RISC-V ISA

Bora Nikolić



September 21, 2021, EET Asia


RISC-V to Shake Up \$8.6B Semiconductor IP Market

RISC-V is now a rising star in the industry, largely due to its open-source advantage, better power consumption performance promise, reliable security functions and lower political risk impact yet.


Semiconductor IP market size, 2020 vs 2025



 
ARM dominates global pure play IP market with 37% share



RISC-V Penetration Rate by 2025

 

Advantages RISC-V offers

 

<https://www.eetasia.com/risc-v-to-shake-up-8-6b-semiconductor-ip-market/>

Review

- Finite state machines: Common example of sequential logic
 - Moore's machine: Output depends only on the current state
 - Mealy's machine: Output depends on the current state and the input
- Large state machines can be factored
- Common Verilog patterns for FSMs
- Common job interview questions 😊



Building a RISC-V Processor

Berkeley RISC-V ISA


www.riscv.org

- An open, license-free ISA
 - Runs GCC, LLVM, Linux distributions, ...
 - RV32, RV64, and RV128 variants for 32b, 64b, and 128b address spaces
- Originally developed for teaching classes at Berkeley, now widely adopted
- Base ISA only ~40 integer instructions
- Extensions provide full general-purpose ISA, including IEEE-754/2008 floating-point
- Designed for extension, customization
- Developed at UC Berkeley, now maintained by RISC-V Foundation
- Open and commercial implementations
- RISC-V ISA, datapath, and control covered in CS61C; summarized here



RISC-V Processor Design

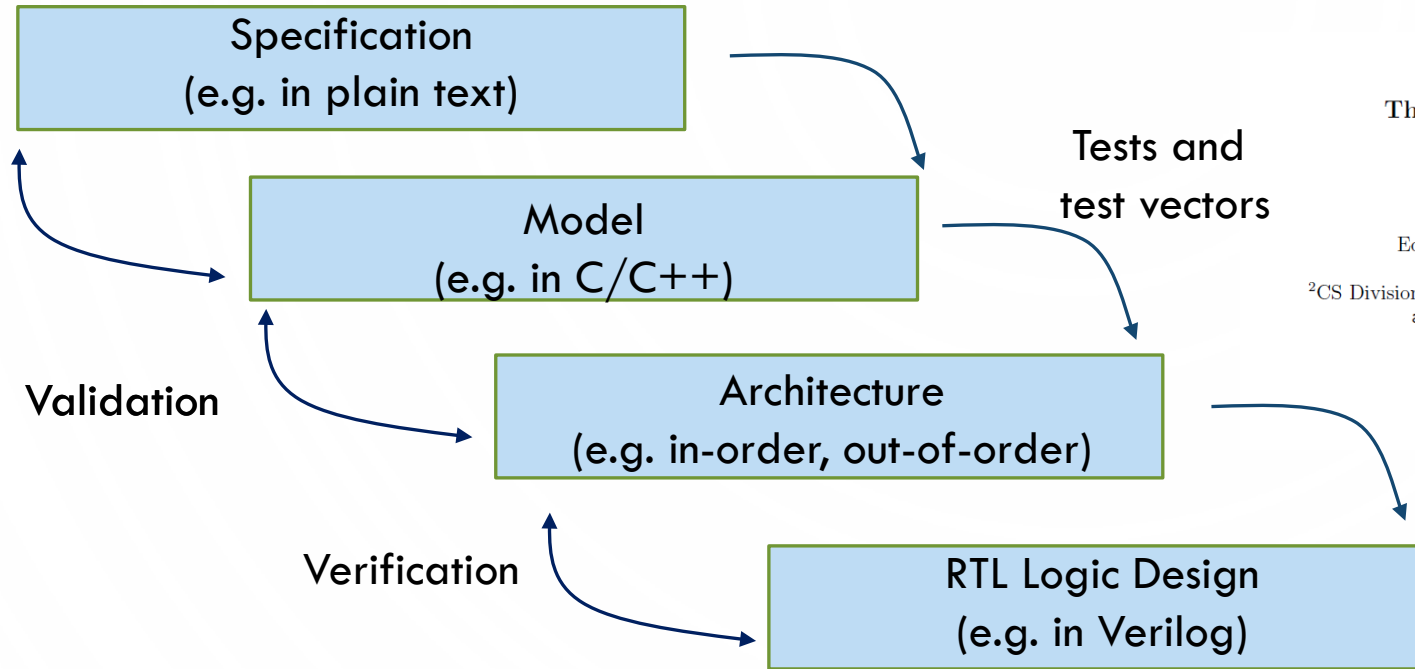- Spec: Unprivileged ISA, RV32I (and a look at RV64I)




The RISC-V Instruction Set Manual
Volume I: Unprivileged ISA
Document Version 20190608-Base-Ratified

Editors: Andrew Waterman¹, Krste Asanović^{1,2}
¹SiFive Inc.,

²CS Division, EECS Department, University of California, Berkeley
andrew@sifive.com, krste@berkeley.edu
June 8, 2019

- Tests provided as a part of the project
- Architecture: Single-cycle and pipelined in-order processor
 - Expanded from CS61C

One-Instruction-Per-Cycle RISC-V Machine

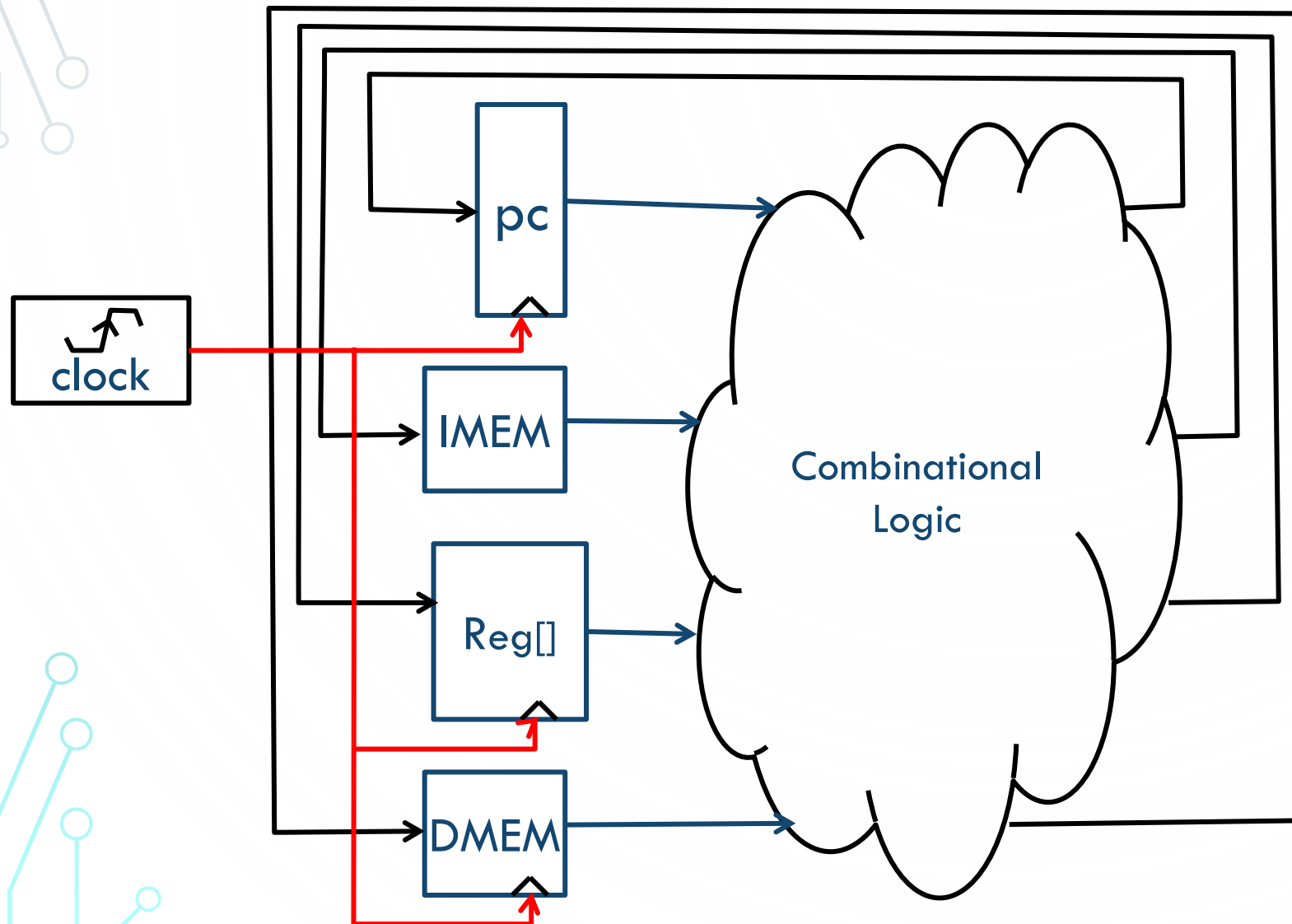

- On every tick of the clock, the computer executes one instruction
- Current state outputs drive the inputs to the combinational logic, whose outputs settle at the values of the state before the next clock edge
- At the rising clock edge, all the state elements are updated with the combinational logic outputs, and execution moves to the next clock cycle

State Required by RV32I ISA

Each instruction reads and updates this state during execution:

- Registers (**x0** . . **x31**)
 - Register file (*regfile*) **Reg** holds 32 registers x 32 bits/register: **Reg[0]** . . **Reg[31]**
 - First register read specified by *rs1* field in instruction
 - Second register read specified by *rs2* field in instruction
 - Write register (destination) specified by *rd* field in instruction
 - **x0** is always 0 (writes to **Reg[0]** are ignored)
 - Program counter (**PC**)
 - Holds address of current instruction
-
- Memory (**MEM**)
 - Holds both instructions & data, in one 32-bit byte-addressed memory space
 - We'll use separate memories for instructions (**IMEM**) and data (**DMEM**)
 - *These are placeholders for instruction and data caches*
 - Instructions are read (*fetch*) from instruction memory
 - Load/store instructions access data memory


Stages of the Datapath : Overview

- Problem: A single, “monolithic” CL block that “executes an instruction” (performs all necessary operations beginning with fetching the instruction and completing with the register access) is be too bulky and inefficient
- Solution: Break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
 - smaller stages are easier to design
 - easy to optimize (change) one stage without touching the others (modularity)

Five Stages of the Datapath


- Stage 1: *Instruction Fetch (IF)*
- Stage 2: *Instruction Decode (ID)*
- Stage 3: *Execute (EX) - ALU (Arithmetic-Logic Unit)*
- Stage 4: *Memory Access (MEM)*
- Stage 5: *Write Back to Register (WB)*

Basic Phases of Instruction Execution

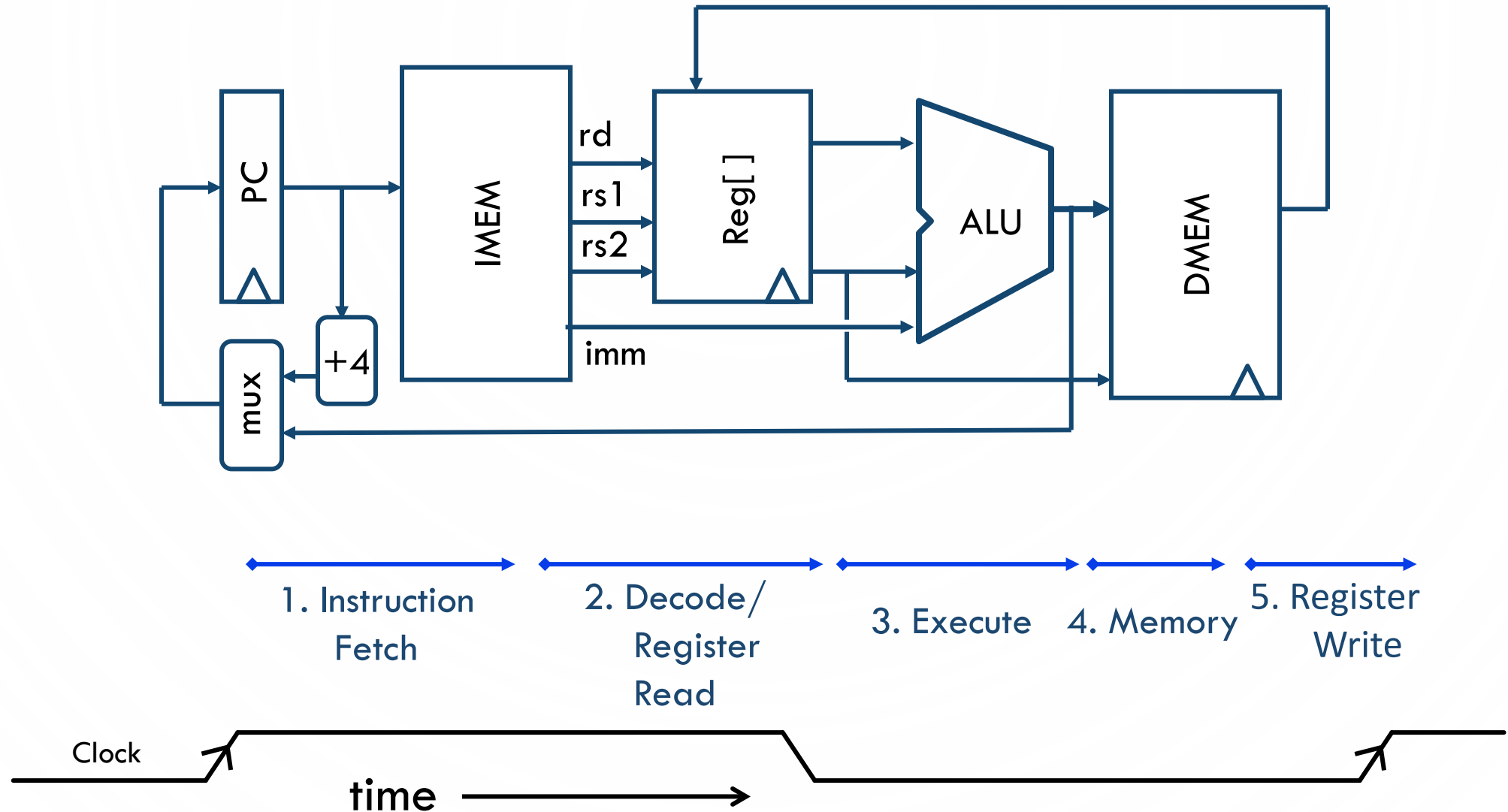

Datapath Components: Combinational


- Combinational Elements

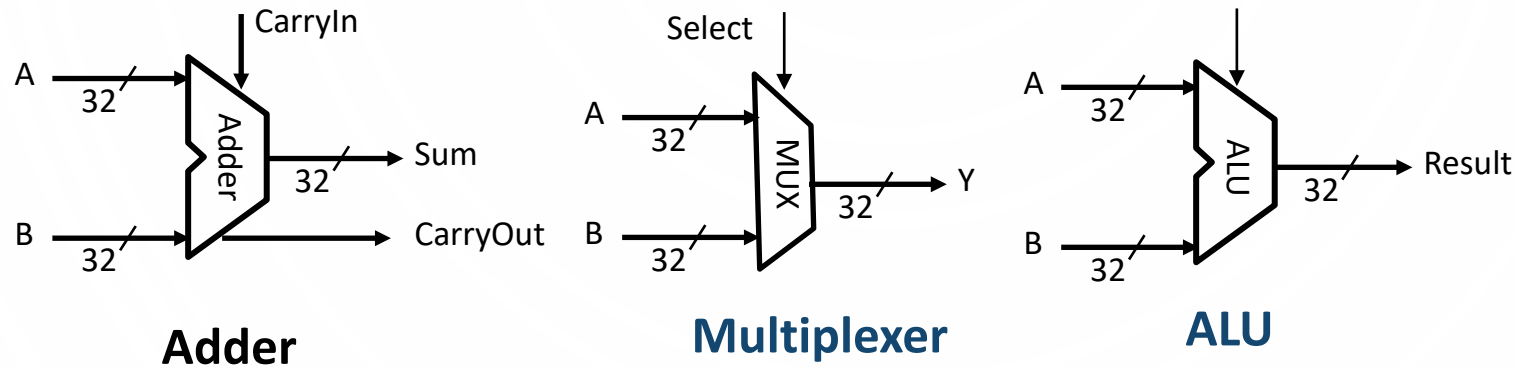

- Storage Elements + Clocking Methodology
- Building Blocks

Datapath Elements: State and Sequencing (1 / 4)

- Register

 

```
always @(posedge clk)
    if (wen) dataout <= datain;
endmodule
```


- Write Enable:

- Negated (or deasserted) (0):
Data Out will not change
- Asserted (1): Data Out will become
Data In on positive edge of clock

Datapath Elements: State and Sequencing (2/4)

- Register file (regfile, RF) consists of 32 registers:

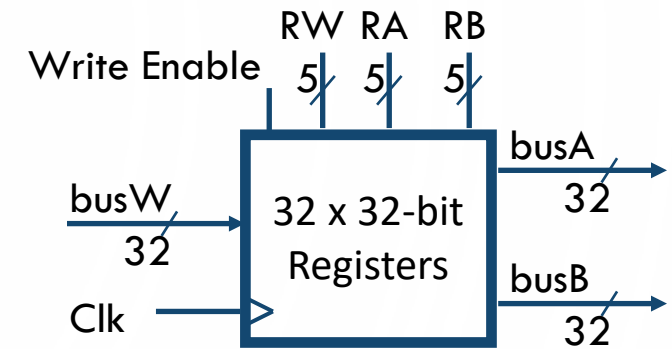- Two 32-bit output busses: busA and busB
- One 32-bit input bus: busW
- x0 is wired to 0




- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
 - Clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”


Datapath Elements: State and Sequencing (3/4)

- Reg file in Verilog

```
module rv32i_regs (  
    input clk, wen,  
    input [4:0] rw,  
    input [4:0] ra,  
    input [4:0] rb,  
    input [31:0] busw,  
    output [31:0] busa,  
    output [31:0] busb  
);  
    reg [31:0] regs [0:30];  
    always @(posedge clk)  
        if (wen) regs[rw] <= busw;  
    assign busa = (ra == 5'd0) ? 32'd0: regs[ra];  
    assign busb = (rb == 5'd0) ? 32'd0: regs[rb];  
endmodule
```

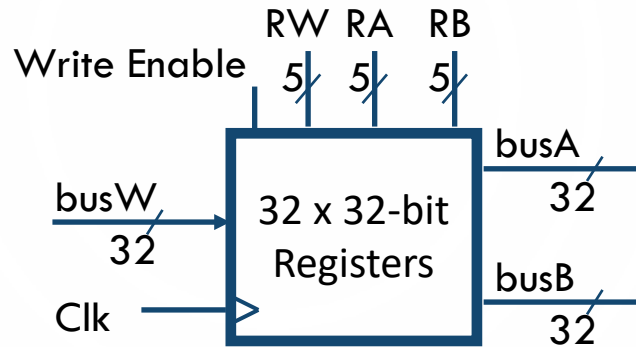


x0 is zero

 

- How does RV64I register file look like?

Datapath Elements: State and Sequencing (4/4)

- “Magic” memory
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - For Read: Address selects the word to put on Data Out
 - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
Address valid \Rightarrow Data Out valid after “access time”
- Real memory later in the class

 

Review: Complete RV32I ISA

Open Reference Card							
Base Integer Instructions: RV32I							
Category	Name	Fmt	RV32I Base	Category	Name	Fmt	RV32I Base
Shifts	Shift Left Logical	R	SLL rd,rs1,rs2	Loads	Load Byte	I	LB rd,rs1,imm
	Shift Left Log. Imm.	I	SLLI rd,rs1,shamt		Load Halfword	I	LH rd,rs1,imm
	Shift Right Logical	R	SRL rd,rs1,rs2		Load Byte Unsigned	I	LBU rd,rs1,imm
	Shift Right Log. Imm.	I	SRLI rd,rs1,shamt		Load Half Unsigned	I	LHU rd,rs1,imm
	Shift Right Arithmetic	R	SRA rd,rs1,rs2		Load Word	I	LW rd,rs1,imm
	Shift Right Arith. Imm.	I	SRAI rd,rs1,shamt	Stores	Store Byte	S	SB rs1,rs2,imm
Arithmetic	ADD	R	ADD rd,rs1,rs2		Store Halfword	S	SH rs1,rs2,imm
	ADD Immediate	I	ADDI rd,rs1,imm		Store Word	S	SW rs1,rs2,imm
	SUBtract	R	SUB rd,rs1,rs2	Branches	Branch =	B	BEQ rs1,rs2,imm
	Load Upper Imm	U	LUI rd,imm		Branch ≠	B	BNE rs1,rs2,imm
	Add Upper Imm to PC	U	AUIPC rd,imm		Branch <	B	BLT rs1,rs2,imm
	XOR	R	XOR rd,rs1,rs2		Branch ≥	B	BGE rs1,rs2,imm
Logical	XOR Immediate	I	XORI rd,rs1,imm		Branch < Unsigned	B	BLTU rs1,rs2,imm
	OR	R	OR rd,rs1,rs2		Branch ≥ Unsigned	B	BGEU rs1,rs2,imm
	OR Immediate	I	ORI rd,rs1,imm	Jump & Link	J&L	J	JAL rd,imm
	AND	R	AND rd,rs1,rs2		Jump & Link Register	I	JALR rd,rs1,imm
	AND Immediate	I	ANDI rd,rs1,imm	Synch	Synch thread	I	FENCE
	Compare Set <	R	SLT rd,rs1,rs2				
Compare	Set < Immediate	I	SLTI rd,rs1,imm	Environment	CALL	I	ECALL
	Set < Unsigned	R	SLTU rd,rs1,rs2		BREAK	I	EBREAK
	Set < Imm Unsigned	I	SLTIU rd,rs1,imm				

- Need datapath and control to implement these instructions

Quiz

- 1) We **should use the main ALU** to compute $PC=PC+4$ in order to save some gates
- 2) The **ALU** is a sequential element
- 3) Program counter is a register

www.yellkey.com/picture

1	2	3
F	F	F
F	F	T
F	T	F
F	T	T
T	F	F
T	F	T
T	T	F
T	T	T




R-Format Instructions: Datapath

Summary of RISC-V Instruction Formats


31	30	25	24	21	20	19	15	14	12	11	8	7	6	0					
funct7					rs2			rs1			funct3			rd			opcode		R-type
imm[11:0]							rs1			funct3			rd			opcode		I-type	
imm[11:5]					rs2			rs1			funct3			imm[4:0]			opcode		S-type
imm[12 10:5]					rs2			rs1			funct3			imm[4:1 11]			opcode		B-type
imm[31:12]										rd			opcode		U-type				
imm[20 10:1 11]]							imm[19:12]					rd			opcode		J-type		

R-Format Instruction Layout

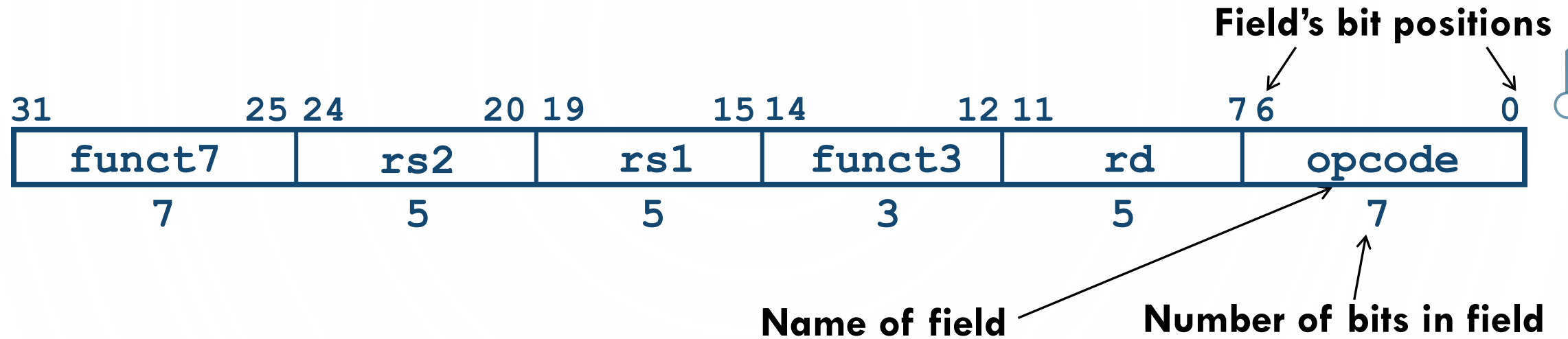


- 32-bit instruction word divided into six fields of varying numbers of bits each: $7+5+5+3+5+7 = 32$
- Examples
 - **opcode** is a 7-bit field that lives in bits 6-0 of the instruction
 - **rs2** is a 5-bit field that lives in bits 24-20 of the instruction

 R-Format Instructions opcode/funct fields



- **opcode**: partially specifies what instruction it is
 - Note: This field is equal to **0110011**_{two} for all R-Format register-register arithmetic instructions
- **funct7+funct3**: combined with **opcode**, these two fields describe what operation to perform
- **Question: You have been professing simplicity, so why aren't opcode and funct7 and funct3 a single 17-bit field?**
 - **Simpler implementation is more important than simpler spec**

 R-Format Instructions register specifiers




- rs1 (**S**ource **R**egister #1): specifies register containing first operand
- rs2 : specifies second register operand
- rd (**D**estination **R**egister): specifies register which will receive result of computation
- Each register field holds a 5-bit unsigned integer (0-31) corresponding to a register number (**x0-x31**)

R-Format Example


- RISC-V Assembly Instruction:

add x18,x19,x10

 

add rs2=10 rs1=19 add rd=18 Reg-Reg OP

Implementing the **add** instruction

 

add rs2 rs1 add rd Reg-Reg OP


add rd, rs1, rs2

- Instruction makes two changes to machine's state:
 - **Reg[rd] = Reg[rs1] + Reg[rs2]**
 - **PC = PC + 4**


Datapath for add

$$PC = PC + 4$$

$$Reg[rd] = Reg[rs1] + Reg[rs2]$$

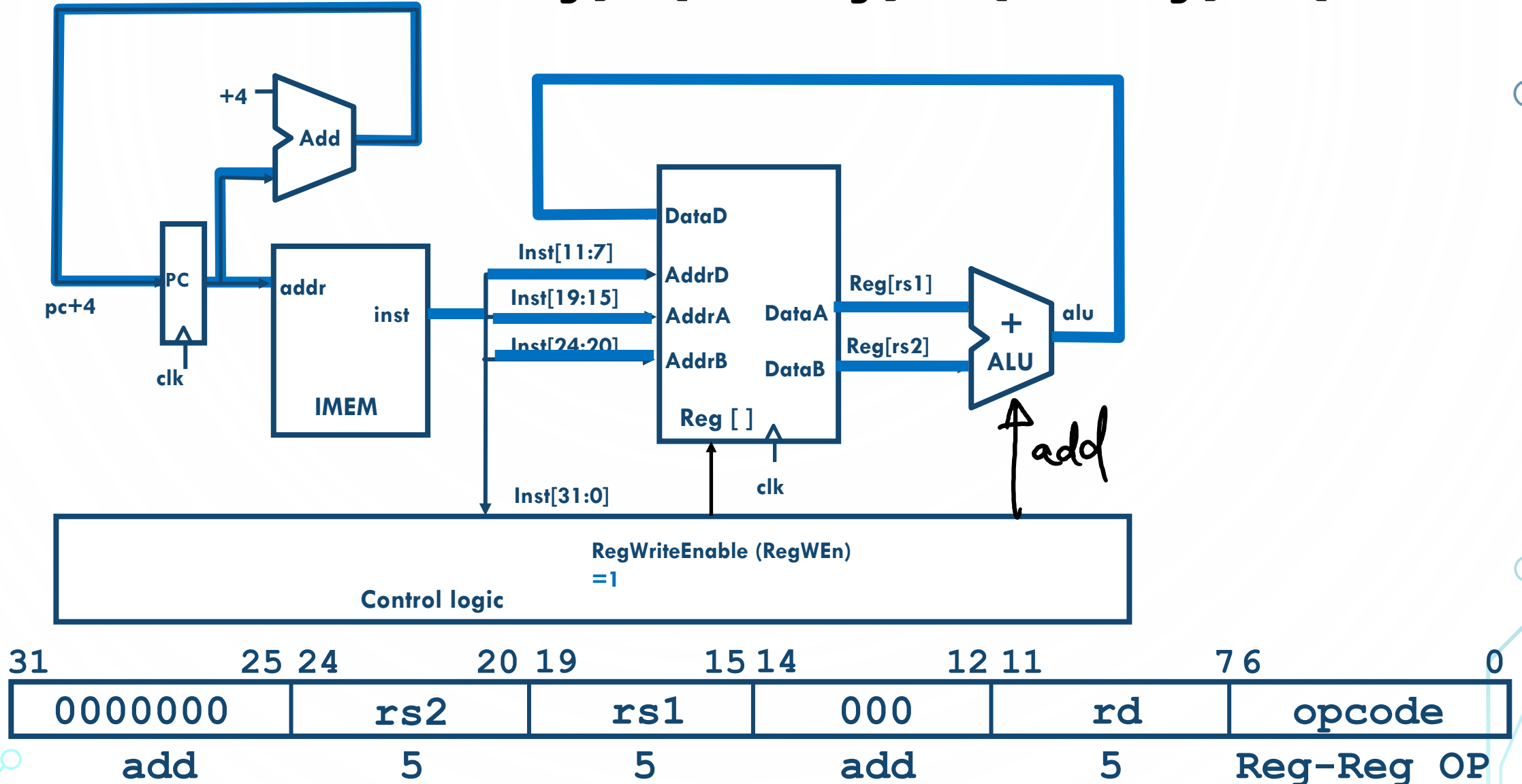

Timing Diagram for add

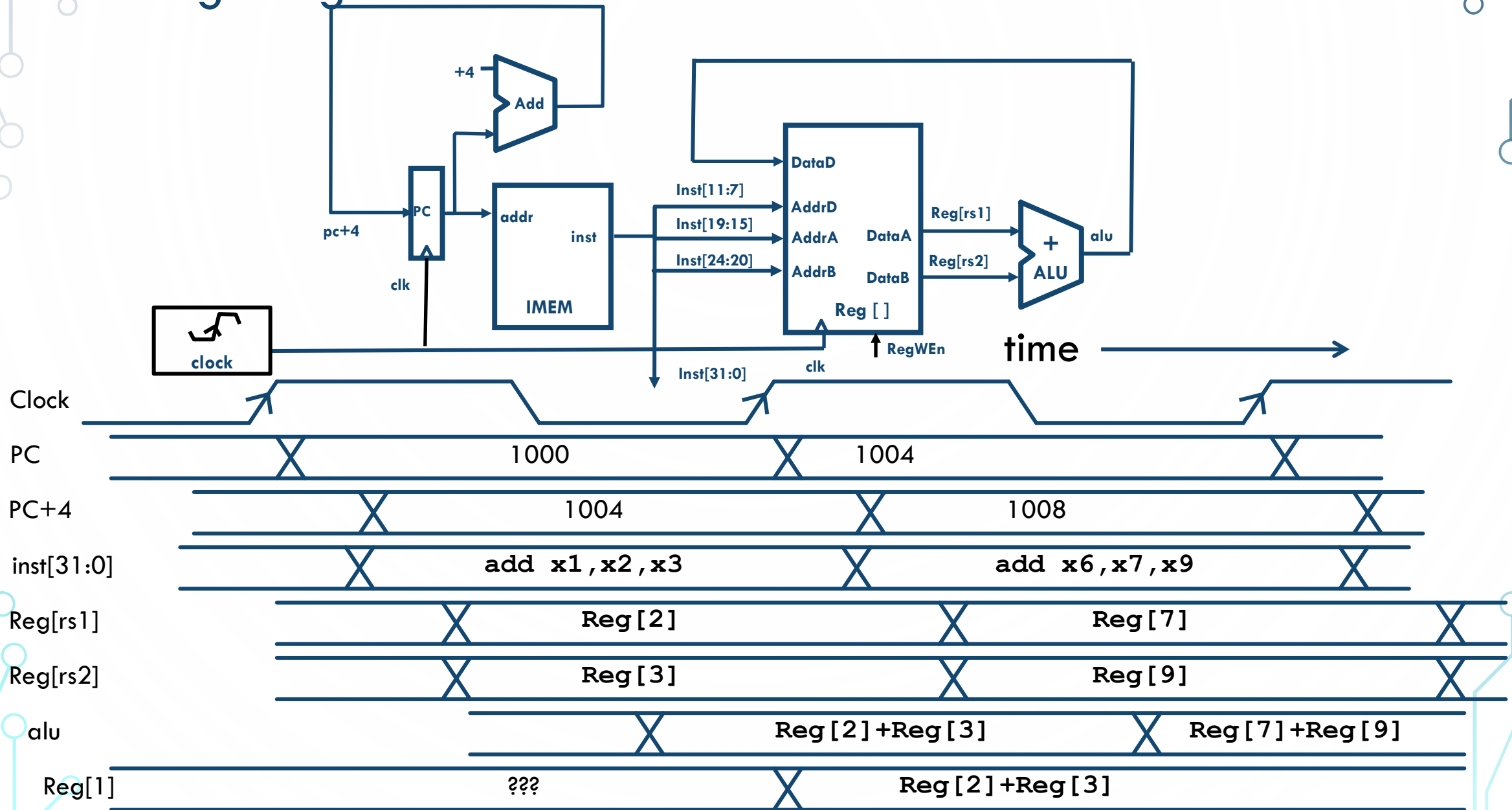


Implementing the **sub** instruction

31	25	24	20	19	15	14	12	11	7	6	0	
0000000	rs2		rs1		000		rd		0110011			add
0100000	rs2		rs1		000		rd		0110011			sub

sub rd, rs1, rs2

- Almost the same as add, except now have to subtract operands instead of adding them
- **inst[30]** selects between add and subtract

Datapath for add/sub

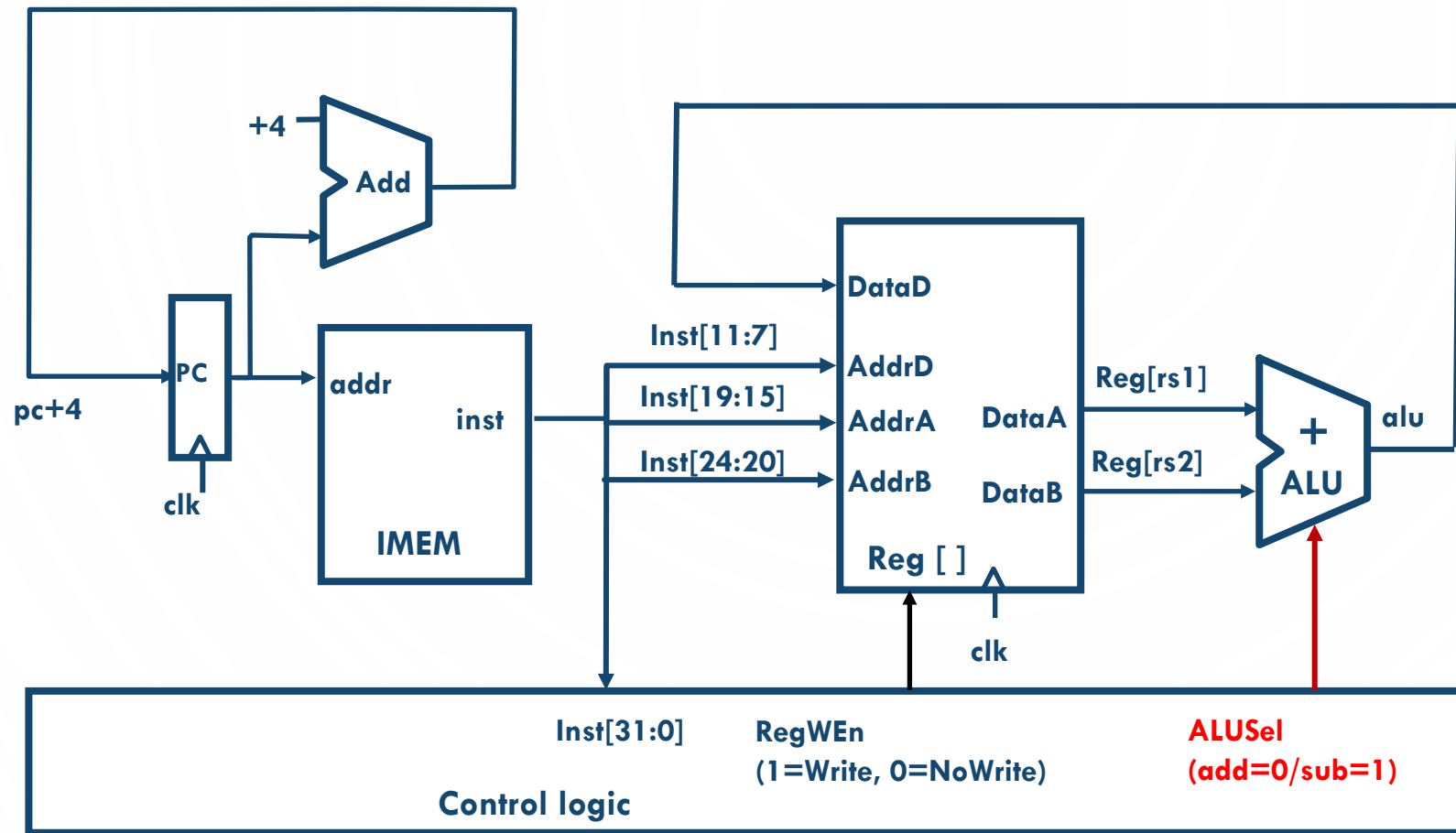

Implementing other R-Format instructions

0000000	rs2	rs1	000	rd	0110011	add
0100000	rs2	rs1	000	rd	0110011	sub
0000000	rs2	rs1	001	rd	0110011	sll
0000000	rs2	rs1	010	rd	0110011	slt
0000000	rs2	rs1	011	rd	0110011	sltu
0000000	rs2	rs1	100	rd	0110011	xor
0000000	rs2	rs1	101	rd	0110011	srl
0100000	rs2	rs1	101	rd	0110011	sra
0000000	rs2	rs1	110	rd	0110011	or
0000000	rs2	rs1	111	rd	0110011	and

- All implemented by decoding funct3 and funct7 fields and selecting appropriate ALU function

Administrivia

- Homework 3 is due next Monday
 - Homework 4 will be posted this week, due before midterm 1
- Lab 4 this week
- Lab 5 next week
- Midterm 1 on October 7, 7-8:30pm



I-Format Instructions: Datapath

Instruction Encoding

- Instructions are encoded to simplify logic
 - **sub** and **sra** differ in Inst[30] from **add** and **srl**
- **RV64I** widens registers (XLEN=64)
- Additional instructions manipulate 32-bit values, identified by a suffix **W**
 - **ADDW, SUBW**
 - RV64I opcode field for 'W' instructions is **0111011** (0110011 for RV32I)

0000000	rs2	rs1	000	rd	0110011
0000000	rs2	rs1	000	rd	0111011


32b

addw

add

64b

I-Format Instruction Layout

 

- Only one field is different from R-format, rs2 and funct7 replaced by 12-bit signed immediate, **imm[11:0]**
- Remaining fields (rs1, funct3, rd, opcode) same as before
- imm[11:0] can hold values in range $[-2048_{\text{ten}}, +2047_{\text{ten}}]$
- Immediate is always sign-extended to 32-bits before use in an arithmetic operation
- Other instructions handle immediates > 12 bits

All RV32 I-format Arithmetic Instructions

imm[11:0]		rs1	000	rd	0010011
imm[11:0]		rs1	010	rd	0010011
imm[11:0]		rs1	011	rd	0010011
imm[11:0]		rs1	100	rd	0010011
imm[11:0]		rs1	110	rd	0010011
imm[11:0]		rs1	111	rd	0010011
0000000	shamt	rs1	001	rd	0010011
0000000	shamt	rs1	101	rd	0010011
0100000	shamt	rs1	101	rd	0010011

addi
slti
sltiu
xori
ori
andi
slli
srli
srai



The same Inst[30] immediate bit is used to distinguish “shift right logical” (SRLI) from “shift right arithmetic” (SRAI)

“Shift-by-immediate” instructions only use lower 5 bits of the immediate value for shift amount (can only shift by 0-31 bit positions)


Implementing I-Format - **addi** instruction

- RISC-V Assembly Instruction – add immediate:


addi x15,x1,-50

  


Datapath for add/sub

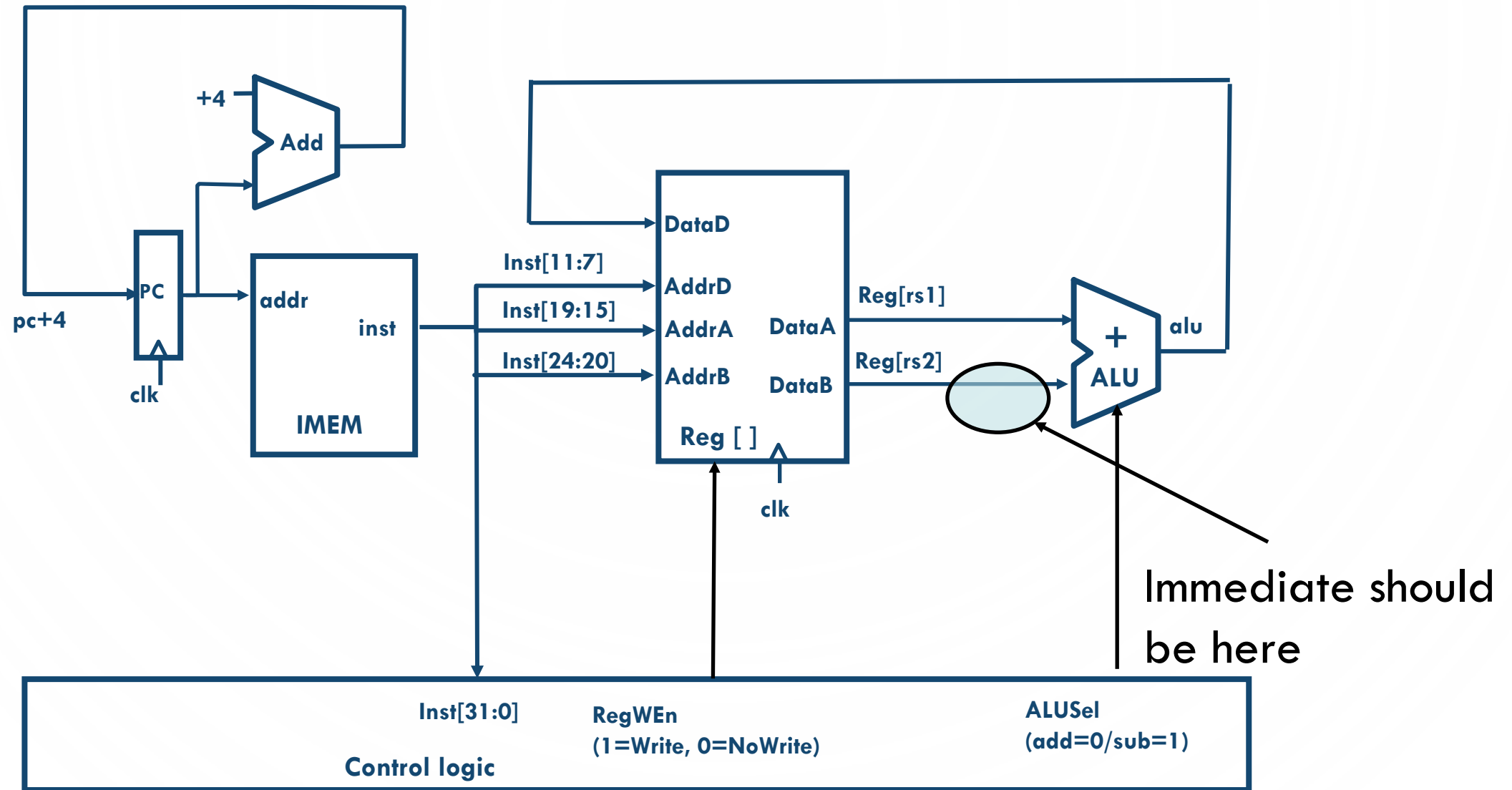



Adding addi to Datapath

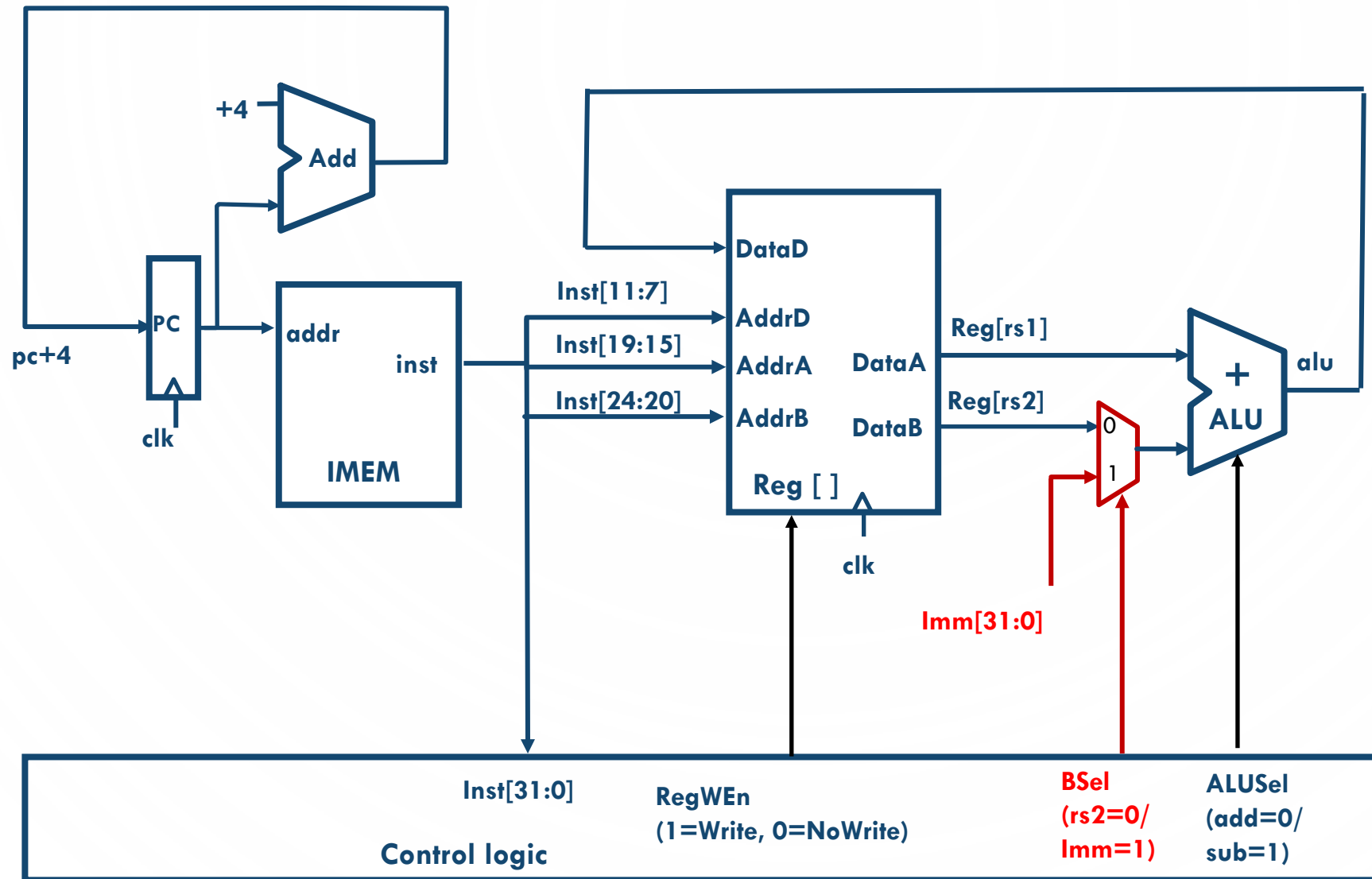

Adding `addi` to Datapath

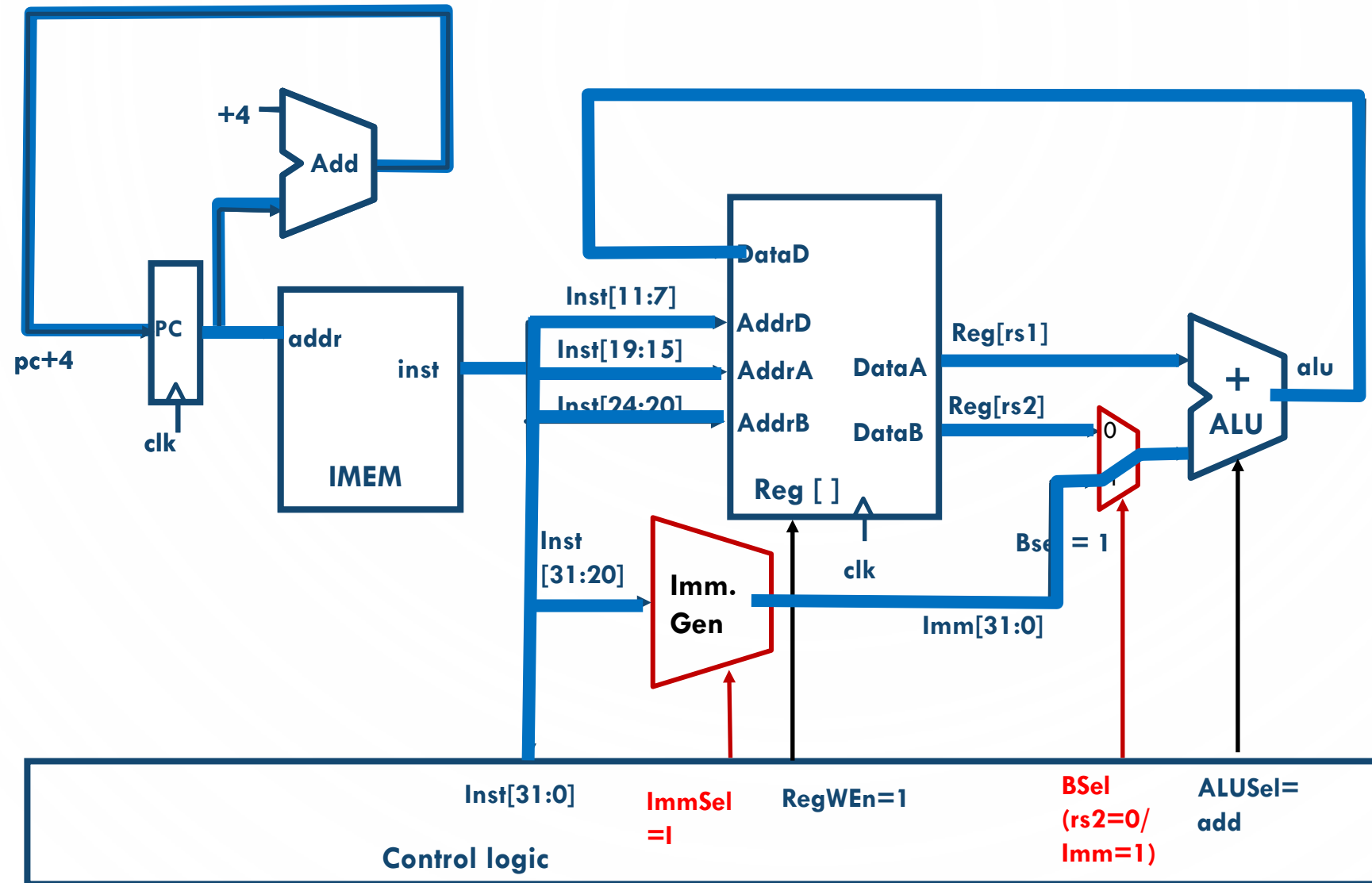


I-Format immediates

 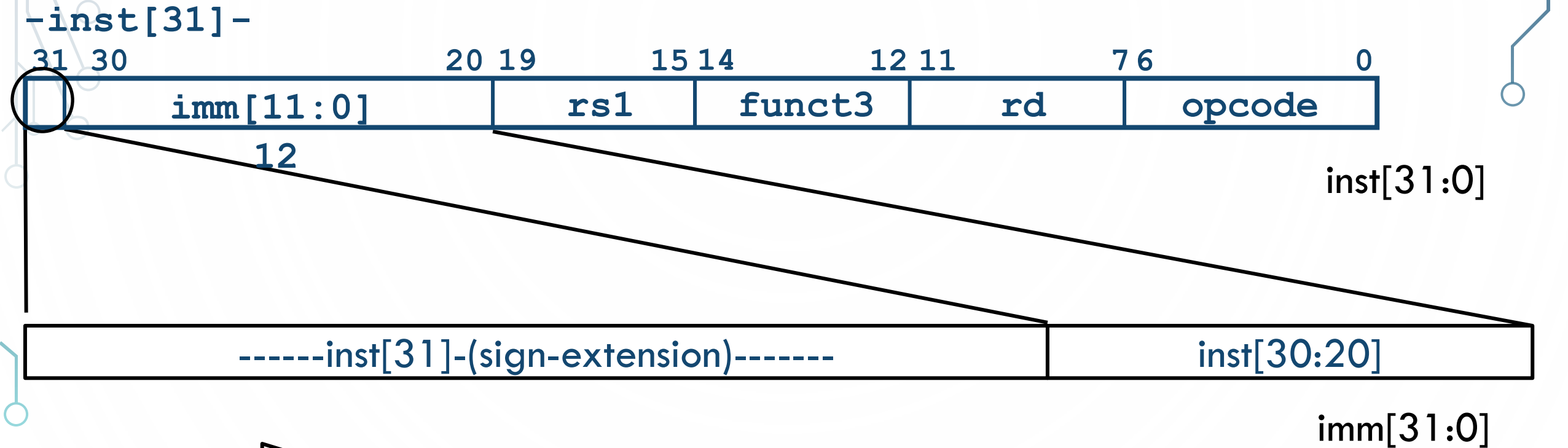

- **High 12 bits of instruction (inst[31:20]) copied to low 12 bits of immediate (imm[11:0])**
- **Immediate is sign-extended by copying value of inst[31] to fill the upper 20 bits of the immediate value (imm[31:12])**
- **Sign extension often in critical path**

R+I Datapath

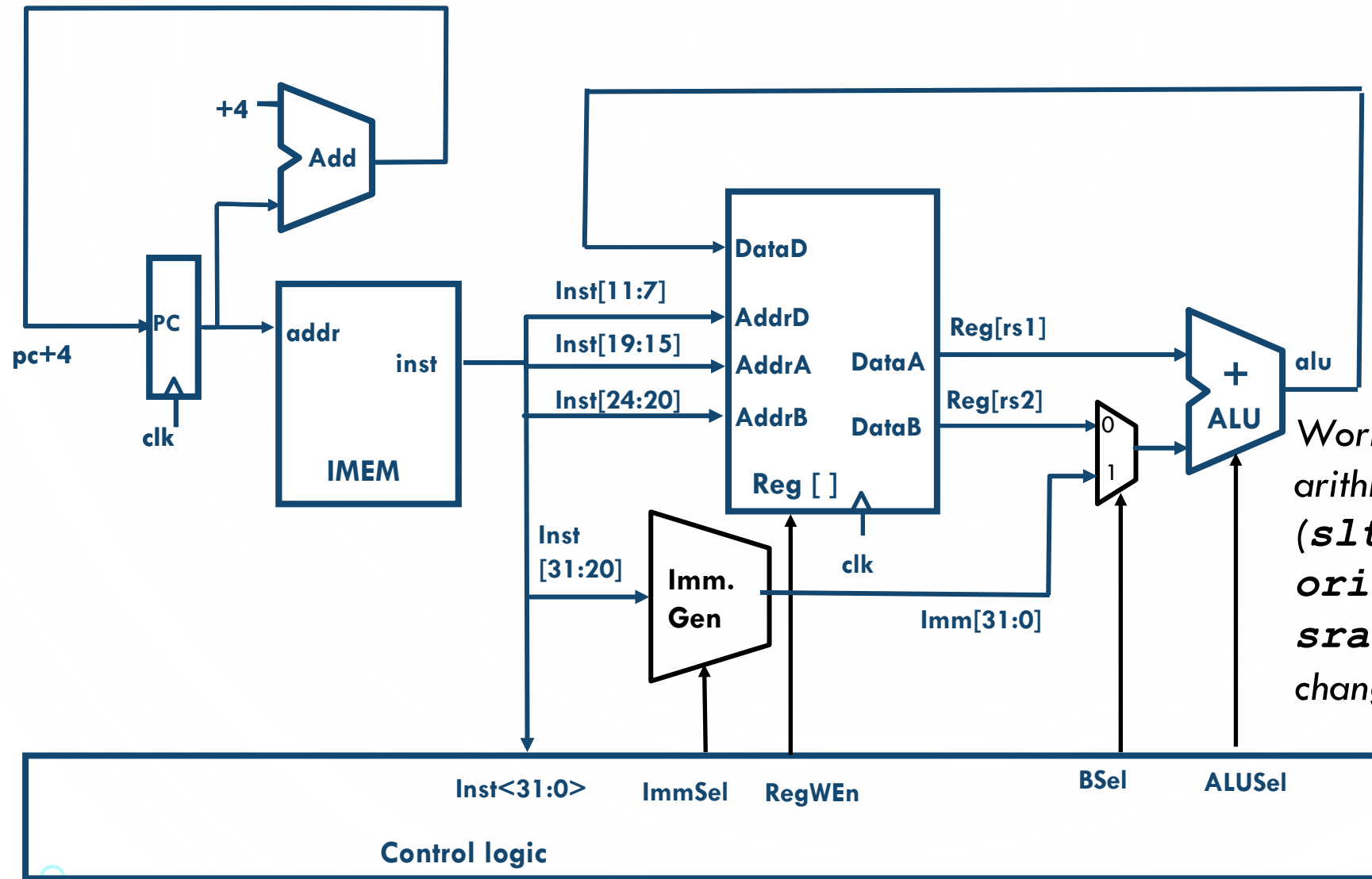


Works for all other I-format arithmetic instructions (*slti*, *sltiu*, *andi*, *ori*, *xori*, *slli*, *srli*, *srai*) just by changing **ALUSel**

Add lw to Datapath


- RISC-V Assembly Instruction (I-type):

lw x14, 8(x2)

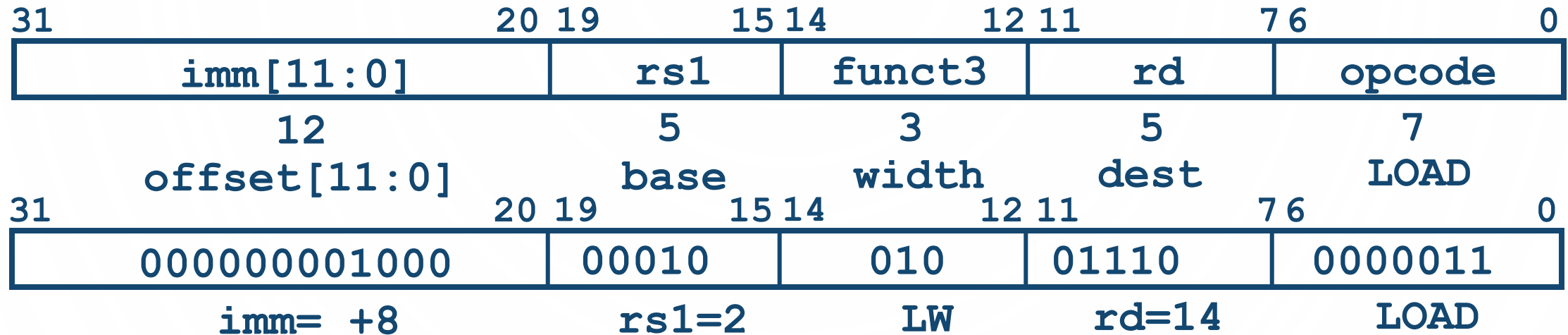

- The 12-bit signed immediate is added to the base address in register **rs1** to form the **memory** address
 - This is very similar to the add-immediate operation but used to create address not to create final result
- The value loaded from **memory** is stored in register **rd**

Adding 1w to Datapath

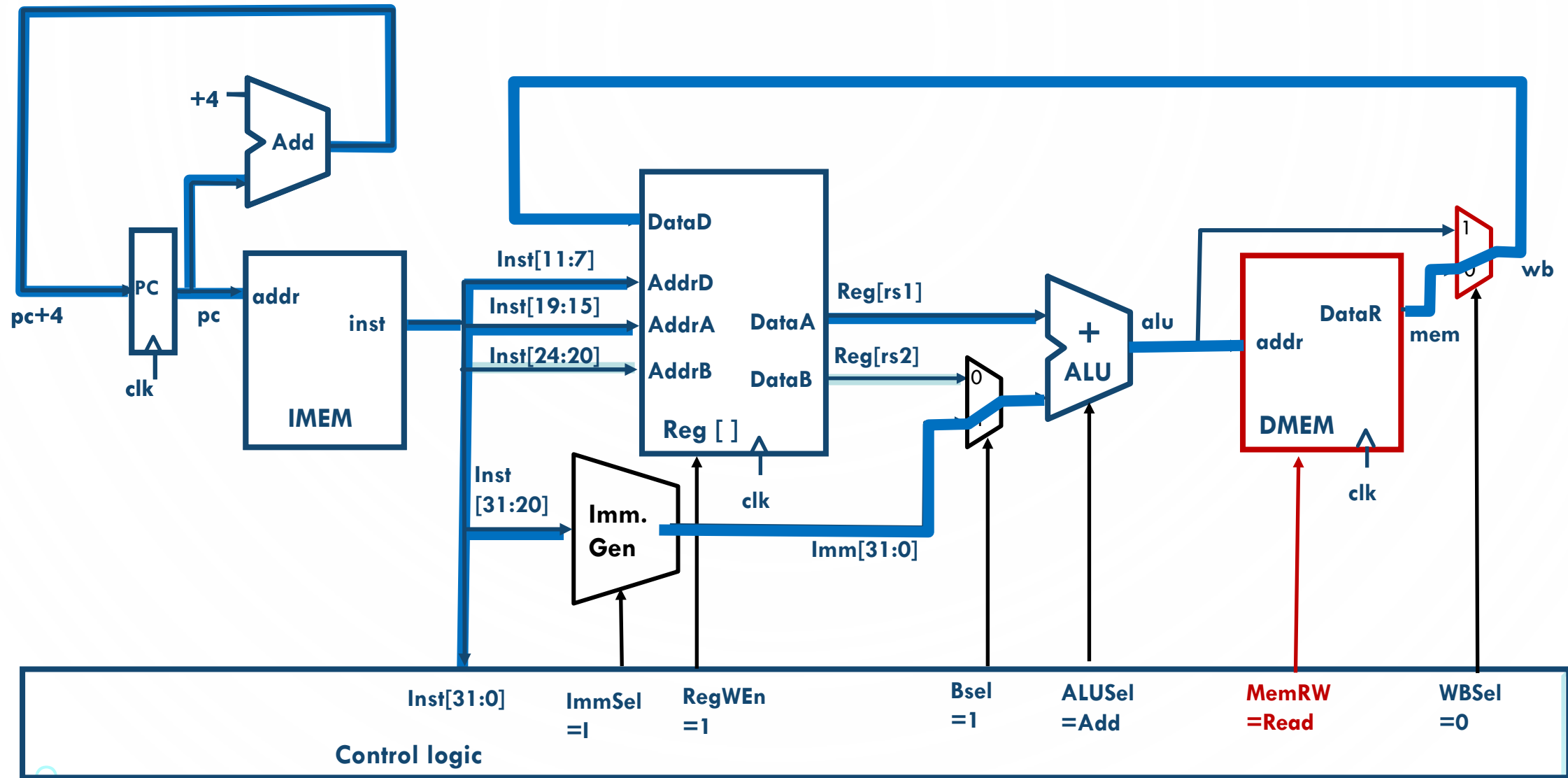

All RV32 Load Instructions

<code>imm[11:0]</code>	<code>rs1</code>	000	<code>rd</code>	0000011	lb
<code>imm[11:0]</code>	<code>rs1</code>	001	<code>rd</code>	0000011	lh
<code>imm[11:0]</code>	<code>rs1</code>	010	<code>rd</code>	0000011	lw
<code>imm[11:0]</code>	<code>rs1</code>	100	<code>rd</code>	0000011	lbu
<code>imm[11:0]</code>	<code>rs1</code>	101	<code>rd</code>	0000011	lhu


funct3 field encodes size and
'signedness' of load data

- Supporting the narrower loads requires additional logic to extract the correct byte/halfword from the value loaded from memory, and sign- or zero-extend the result to 32 bits before writing back to register file.
 - It is just a mux for load extend, similar to sign extension for immediates



S-Format Instructions: Datapath


S-Format Used for Stores

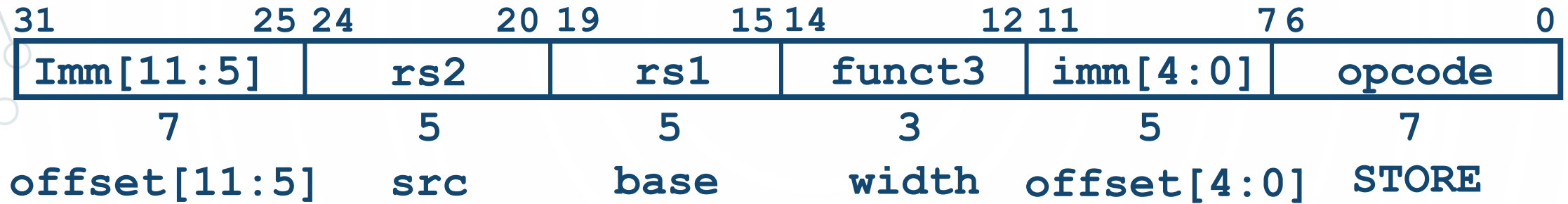

- Store needs to read two registers, rs1 for base memory address, and rs2 for data to be stored, as well immediate offset!
- Can't have both rs2 and immediate in same place as other instructions!
- Note that stores don't write a value to the register file, **no rd!**
- RISC-V design decision is move low 5 bits of immediate to where rd field was in other instructions – keep rs1/rs2 fields in same place
 - register names more critical than immediate bits in hardware design

Adding **sw** Instruction

 
- **sw**: Reads two registers, rs1 for base memory address, and rs2 for data to be stored, as well immediate offset!




offset[11:5] rs2=14 rs1=2 SW offset[4:0] STORE
=0 =8



Datapath with 1w

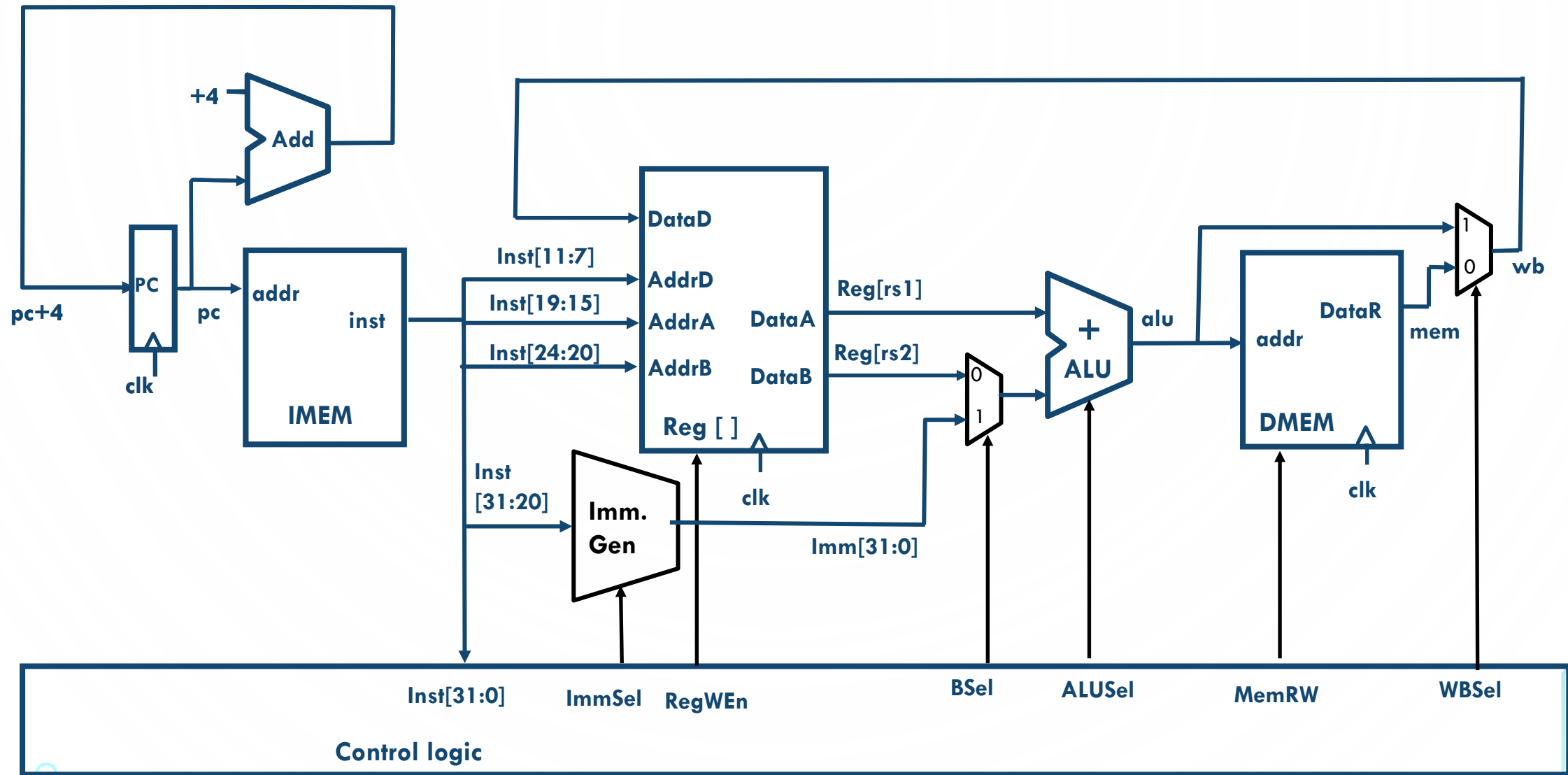

Adding **sw** to Datapath

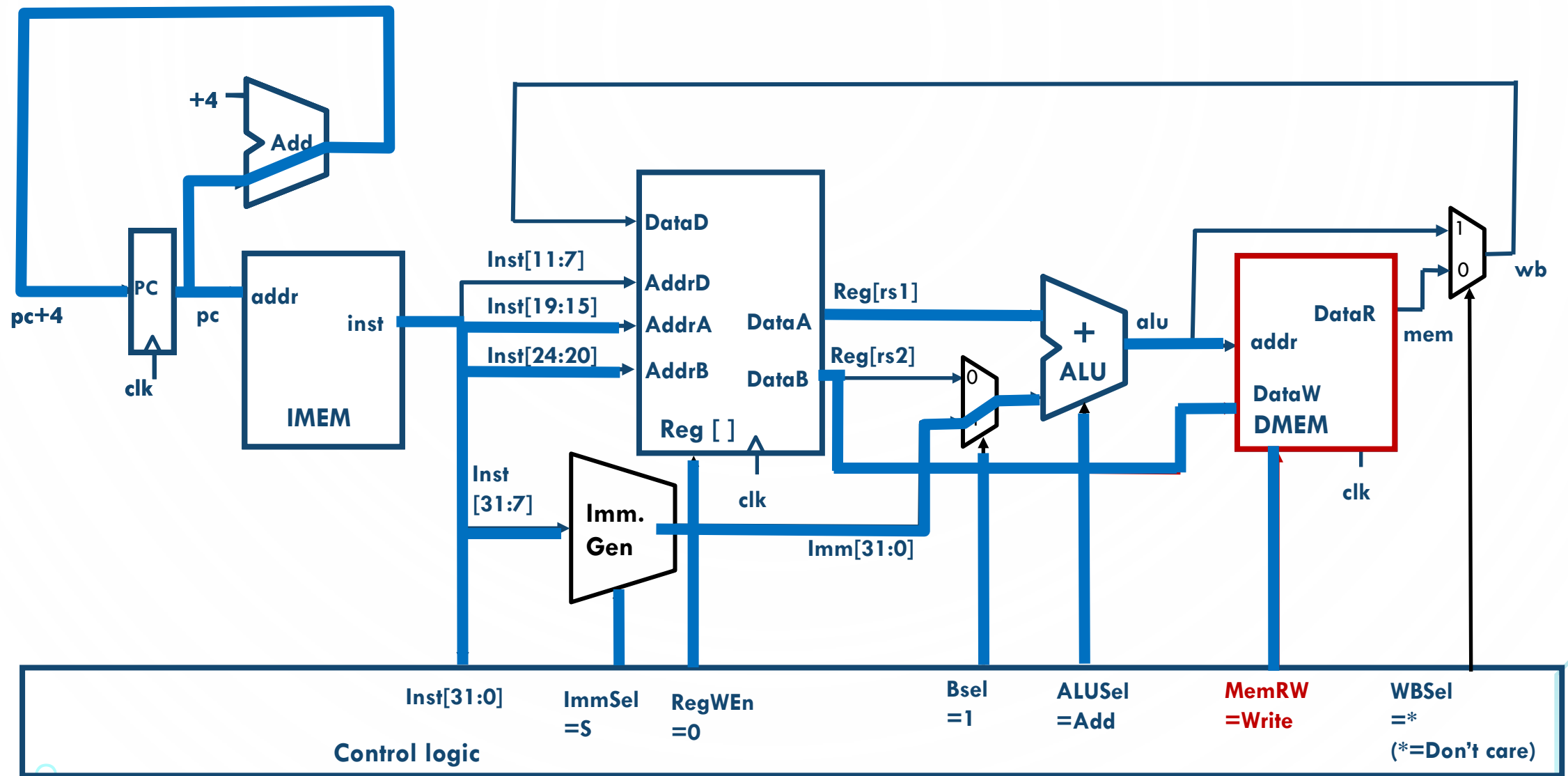


All RV32 Store Instructions

Imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	sb
Imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	sh
Imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	sw

width

- Store byte, halfword, word

I+S Immediate Generation

 

- Just need a 5-bit mux to select between two positions where low five bits of immediate can reside in instruction
- Other bits in immediate are wired to fixed positions in instruction

Summary

- RISC-V ISA
 - Open, with increasing adoption
- RISC-V processor
 - A large state machine
 - Datapath + control
 - Reviewed R-, I-, S-format instructions and corresponding datapath elements