 


EECS 151/251A Homework 6

Due Friday, April 1st, 2022


Problem 1: Not So Much Effort

Consider a NAND3 gate that drives one of the input of a NAND2 gate:



For this problem, assume you have a reference inverter with $W_P = W_N = 1$ and $R_p = R_n = R_{eq}$. This technology has $\gamma \equiv \frac{C_d}{C_g} = 1.5$.

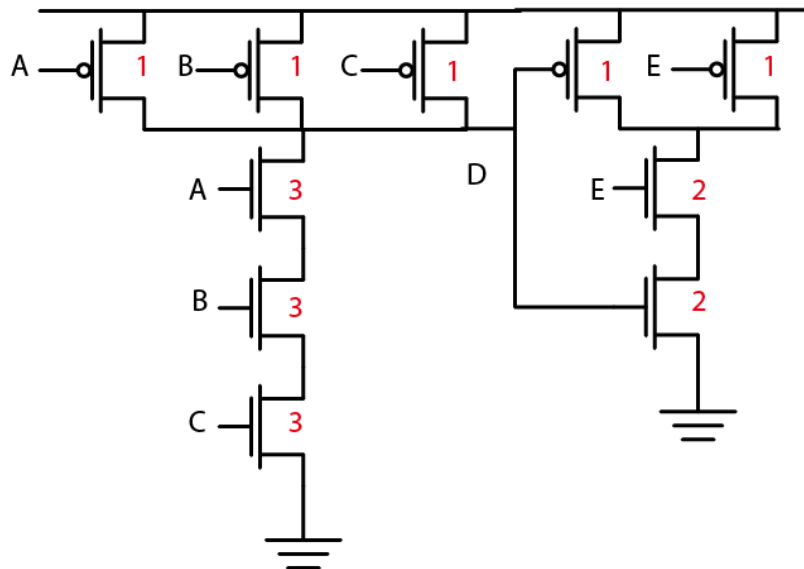- (a) Assume PMOS has unit size (“1”). Draw the transistor-level schematic for the circuit above and size all the NMOS transistors such that the equivalent switching resistances are the same as a reference inverter.



- (b) What is the Logical Effort of each gate? Show your steps.

$$LE_{NAND3} = \frac{C_g + 3C_g}{C_g + C_g} = \frac{4}{2} = 2$$


$$LE_{NAND2} = \frac{C_g + 2C_g}{C_g + C_g} = \frac{3}{2}$$

- (c) Now let the second NAND gate drive a load C_L . Assume the PMOS of the reference inverter has gate capacitance C_g . Write the delay from A to the output driving C_L .

$$\begin{aligned} \text{Total delay} &= \text{Delay of NAND3 driving NAND2} + \text{Delay of NAND2 driving } C_L \\ t_{loaded} &= \ln(2) * R_{eq} * (3\gamma C_g + 3\gamma C_g + 3C_g) + \ln(2) * R_{eq} * (2\gamma C_g + 2\gamma C_g + C_L) \\ &= \ln(2) * R_{eq} * [(6\gamma + 3 + 4\gamma)C_g + C_L] \\ &= \ln(2) * R_{eq} * C_g * \gamma * 2 * \frac{(6 + 4)}{2} + \ln(2) * R_{eq} * C_g * 2 \left(\frac{3}{4} * \frac{4}{2} + \frac{C_L}{3C_g} * \frac{3}{2} \right) \\ &= \ln(2) * R_{eq} * [18C_g + C_L] \end{aligned}$$

 Problem 2: More Effort

Consider the following multi-stage network. The two inverters in the last stage are identical.



Again, assume you have a reference inverter with $W_P = W_N = 1$ and $R_p = R_n = R_{eq}$. This technology has $\gamma \equiv \frac{C_d}{C_g} = 1.5$.

- (a) The input capacitance of A is C_{in} and the load $C_L = 48 * C_{in}$. Determine the path effort from A to the output load C_L .

$$\begin{aligned} G &= \frac{3}{2} * \frac{3}{2} * 1 * 2 * 1 = \frac{9}{2} \\ B &= 1 * 1 * 1 * 1 * 2 = 2 \\ F &= 48 \\ H &= GBF = 432 \end{aligned}$$

- (b) Determine the optimum stage effort (SE) that results in minimum delay.

$$SE_{opt} = \sqrt[5]{432} \cong 3.37$$

- (c) Express the minimum delay in terms of the intrinsic delay of the reference inverter, τ_{inv} .

$$\begin{aligned} \tau_{min} &= \frac{\tau_{inv}}{\gamma} * (5 * SE_{opt}) + \tau_{inv} \Sigma p \\ &= \tau_{inv} * \left(5 * \frac{SE_{opt}}{\gamma} + \Sigma p \right) \end{aligned}$$

$$\begin{aligned}
&= \tau_{inv} * \left(\frac{5 * \sqrt[5]{432}}{\gamma} + \left(\frac{4}{2} + \frac{4}{2} + 1 + \frac{6}{2} + 1 \right) \right) \\
&= \tau_{inv} * \left(5 * \frac{\sqrt[5]{432}}{\gamma} + 9 \right) \\
&\cong 20.2 * \tau_{inv}
\end{aligned}$$

Alternatively, if define $\tau_{inv} = \ln 2 * R_{eq} * C_{in,inv}$, then the answer is

$$\begin{aligned}
\tau_{inv} * (5 * SE_{opt} + \sum p * \gamma) &= \tau_{inv} * \left(5 * \sqrt[5]{432} + \left(\frac{4}{2} + \frac{4}{2} + 1 + \frac{6}{2} + 1 \right) * 1.5 \right) \\
&= 30.32 \tau_{inv}
\end{aligned}$$

- (d) Based on your answers above, find the optimum input capacitance of the gates of each stage on the critical path.

$$\begin{aligned}
E &= 48 C_{in} * 1 * \frac{2}{SE_{opt}} \cong 28.49 C_{in} \\
D &= E * 2 * \frac{1}{SE_{opt}} \cong 16.91 C_{in} \\
C &= D * 1 * \frac{1}{SE_{opt}} \cong 5.01 C_{in} \\
B &= C * \frac{3}{2} * \frac{1}{SE_{opt}} \cong 2.23 C_{in}
\end{aligned}$$

Sanity check:

$$A = B * \frac{3}{2} * \frac{1}{SE_{opt}} \cong 1 C_{in}$$