

EECS151 : Introduction to Digital Design and ICs

Lecture 18 – Adders, Multipliers

Bora Nikolić



TSMC Details The Benefits of Its N3 Node

October 27, 2021, EETimes - TSMC, now chugging along with its N5 process node, said it will have its evolutionary N4 node ramped up to volume production this year. The N3 node, which will provide more of a technological leap than N4, is planned to go into volume production in the second half of 2022. N3 will indeed offer customers the kind of performance improvements they might hope for from a major node jump, though the speed improvement will be at the low-end of TSMC's projected aspirations from last year; the company also just missed its target for density improvement.

TSMC Node Comparisons

Metric	N7 to N5	N5 to N3 (2020 projection)	N5 to N3 (2021 actual)
Logic density improvement	1.87x	1.7x	1.6x
Speed improvement	15%	10-15%	11%
Power draw improvement	-20%	(n/a)	-27%

Source: TSMC, EE Times

EECS151 L18 ADDERS II

Nikolić Fall 2021

1

Berkeley



1

Review

- Binary adders are a common building block of digital systems
- Carry is in the critical path
- Mirror adders cells are commonly found in libraries
- Ripple-carry adder is the least complex, lowest energy

EECS151 L18 ADDERS II

Nikolić Fall 2021

2

Berkeley



2



Ripple-Carry Adders


EECS151 L18 ADDERS II

Nikolić Fall 2021

3 Berkeley

3

Sizing the Mirror Adder

  $g_{Ci} = 2$ 

- Carry is in the critical path
- Optimal effort is 4, logical effort is 2
- Drives one carry and one sum input
 - Conveniently split fanout
- All stages equally sized

EECS151 L18 ADDERS II

Nikolić Fall 2021

4 Berkeley

4

The Mirror Adder

- The NMOS and PMOS chains are **completely symmetrical**.
A maximum of two series transistors in the carry-generation stack.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be smaller.
- The transistors connected to C_i are placed closest to the output.
- Minimize the capacitance at node C_o .


EECS151 L18 ADDERS II

Nikolić Fall 2021



5

Transmission Gate Full Adder

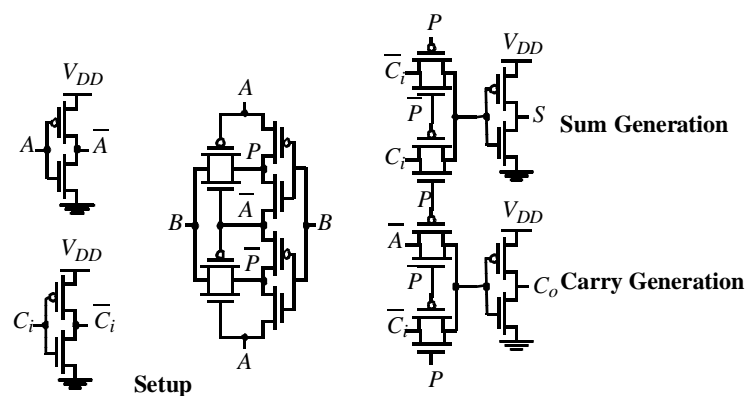

EECS151 L18 ADDERS II

Nikolić Fall 2021



6



Carry Bypass Adders

EECS151 L18 ADDERS II


Nikolić Fall 2021

7 Berkeley

7

Carry-Bypass Adder

- Also called 'carry skip'

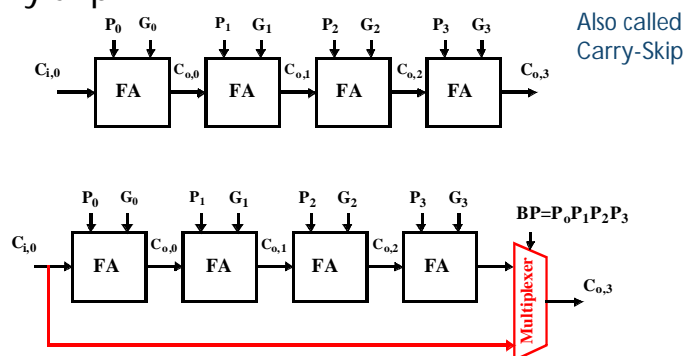

Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{0,3} = C_{0,0}$, else "kill" or "generate".


EECS151 L18 ADDERS II

Nikolić Fall 2021

8 Berkeley

8

Carry-Bypass Adder (cont.)

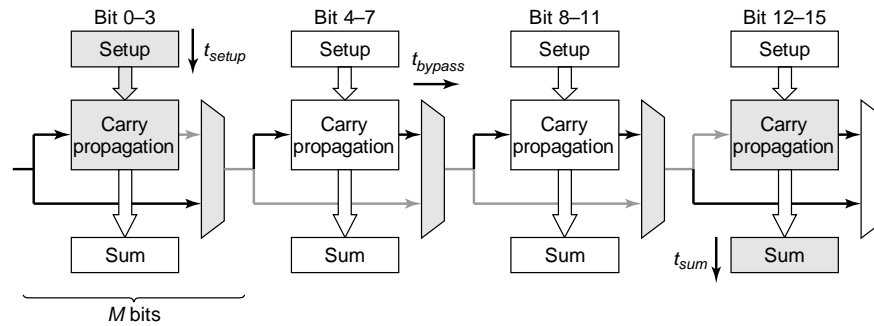

$$t_{adder} = t_{setup} + M t_{carry} + (N/M - 1) t_{bypass} + (M - 1) t_{carry} + t_{sum}$$


EECS151 L18 ADDERS II

Nikolić Fall 2021

9

9

Carry Ripple versus Carry Bypass

 

- Depends on technology, design constraints


EECS151 L18 ADDERS II

Nikolić Fall 2021

10

10

To Design a Faster Carry-Bypass Adder

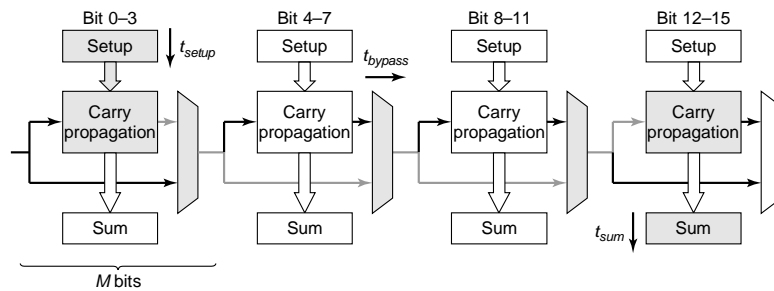

- a) Uniform groups of 4 are optimal
- b) Uniform groups >4 are optimal
- c) Uniform groups <4 are optimal
- d) Increasing group size with higher bit position
- e) Wider groups around mid bit positions are optimal

www.yellkey.com/ahead

Faster Carry-Bypass

Administrivia

- Homework 7 due this week
- Homework 8 due next week
 - In scope for midterm
- All labs need to be checked off by this week!
- Projects (ASIC and FPGA) started, first check point this week
- Midterm 2 is on November 4 at 7pm
 - Review session tonight at 7pm

EECS151 L18 ADDERS II

Nikolić Fall 2021

13

Berkeley



13



Carry-Select Adders

EECS151 L18 ADDERS II

Nikolić Fall 2021


14

Berkeley



14

Carry-Select Adder

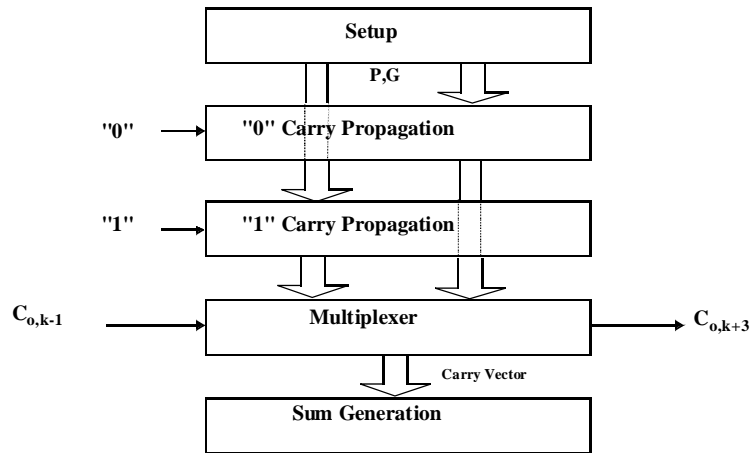


EECS151 L18 ADDERS II

Nikolić Fall 2021

15

15

Carry Select Adder: Critical Path

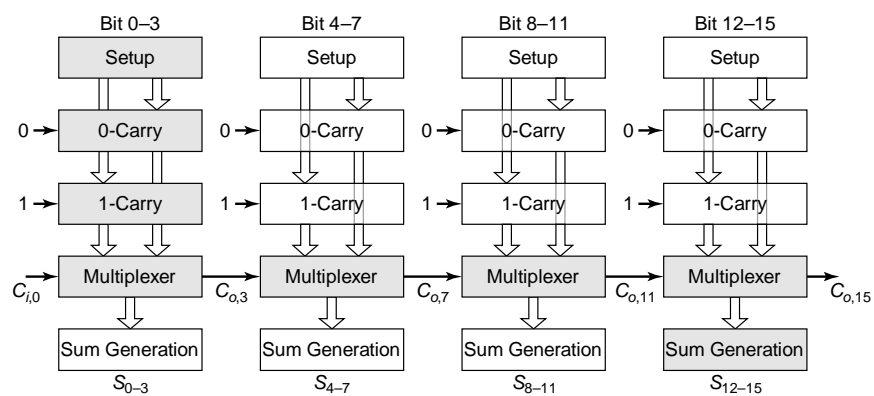


EECS151 L18 ADDERS II

Nikolić Fall 2021

16

16

Linear Carry Select

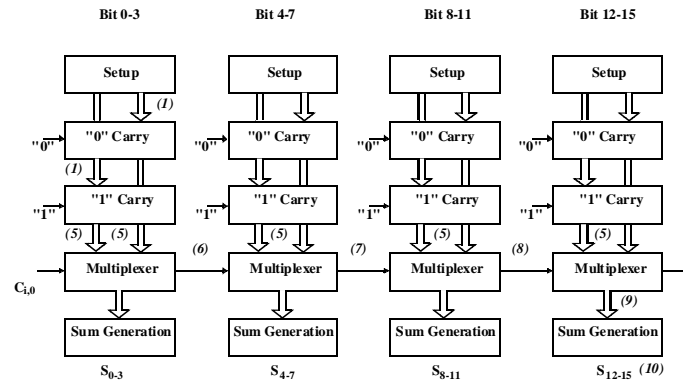

$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$


EECS151 L18 ADDERS II

Nikolić Fall 2021

17 Berkeley

17

Square Root Carry Select

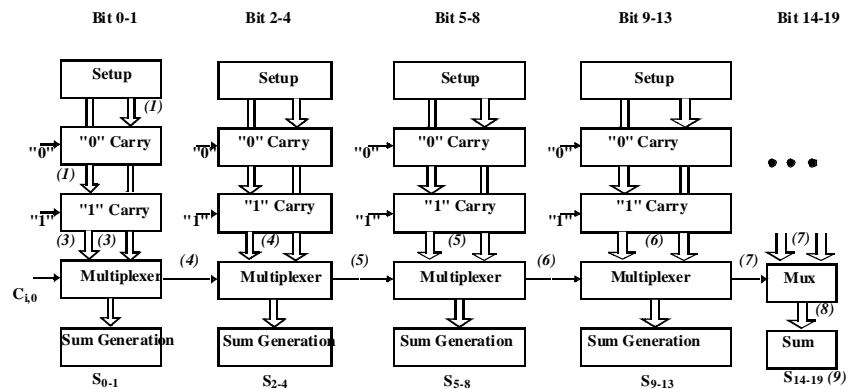

$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$


EECS151 L18 ADDERS II

Nikolić Fall 2021

18 Berkeley

18

Adder Delays - Comparison

 

EECS151 L18 ADDERS II

Nikolić Fall 2021

19

 Berkeley
 UNIVERSITY OF CALIFORNIA


19



Carry-Lookahead Adders

EECS151 L18 ADDERS II


Nikolić Fall 2021

20

 Berkeley
 UNIVERSITY OF CALIFORNIA


20

Lookahead - Basic Idea

 

$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$

EECS151 L18 ADDERS II

Nikolić Fall 2021

21

21

Lookahead: Topology

$$C_o = A B + B C_i + A C_i = G + P C_i$$

Expanding lookahead equations:

$$C_{o,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{i,1} = G_0 + P_0 C_{i,0}$$


Carry at bit k:

$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} C_{o,k-2})$$

Expanding at bit k:

$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} (\dots + P_1 (G_0 + P_0 C_{i,0}) \dots))$$

 Carry-lookahead gate grows at each bit position!



EECS151 L18 ADDERS II

Nikolić Fall 2021

22

22

Carry Lookahead Trees

Build the carrylookahead tree as a hierarchy of gates

$$C_{0,0} = G_0 + P_0 C_{i,0}$$

$$C_{0,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$\begin{aligned} C_{0,2} &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0} \\ &= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2,1} + P_{2,1} C_{0,0} \end{aligned}$$

Can continue building the tree hierarchically.

Logarithmic (Tree) Adders – Idea


- “Look ahead” across groups of multiple bits to figure out the carry

- Example with two bit groups:

$$P_{1:0} = P_1 \cdot P_0, G_{1:0} = G_1 + P_1 \cdot G_0, \rightarrow C_{out1} = G_{1:0} + P_{1:0} \cdot C_{0,in}$$


- Combine these groups in a tree structure:

- Delay is now $\sim \log_2(N)$

 

Rest of the Tree

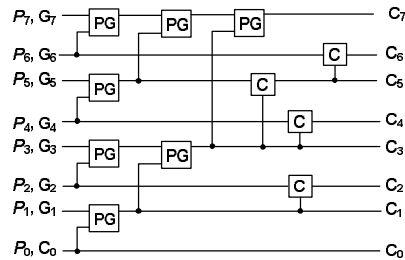- Previous picture shows only half of the algorithm
 - Need to generate carries at individual bit positions too



EECS151 L18 ADDERS II

Nikolić Fall 2021

 Berkeley
 UNIVERSITY OF CALIFORNIA

25

Many Kinds of Tree Adders


- Many ways to construct these tree (or “carry lookahead”) adders
 - Many of these variations named after the people who created them
- Most of these vary three basic parameters:
 - Radix: how many bits are combined in each PG gate
 - Previous example was radix 2; often go up to radix 4
 - Tree depth: stages of logic to the final carry. Must be at least $\log_{\text{Radix}}(N)$
 - Sparseness

EECS151 L18 ADDERS II


Nikolić Fall 2021

 Berkeley
 UNIVERSITY OF CALIFORNIA

26

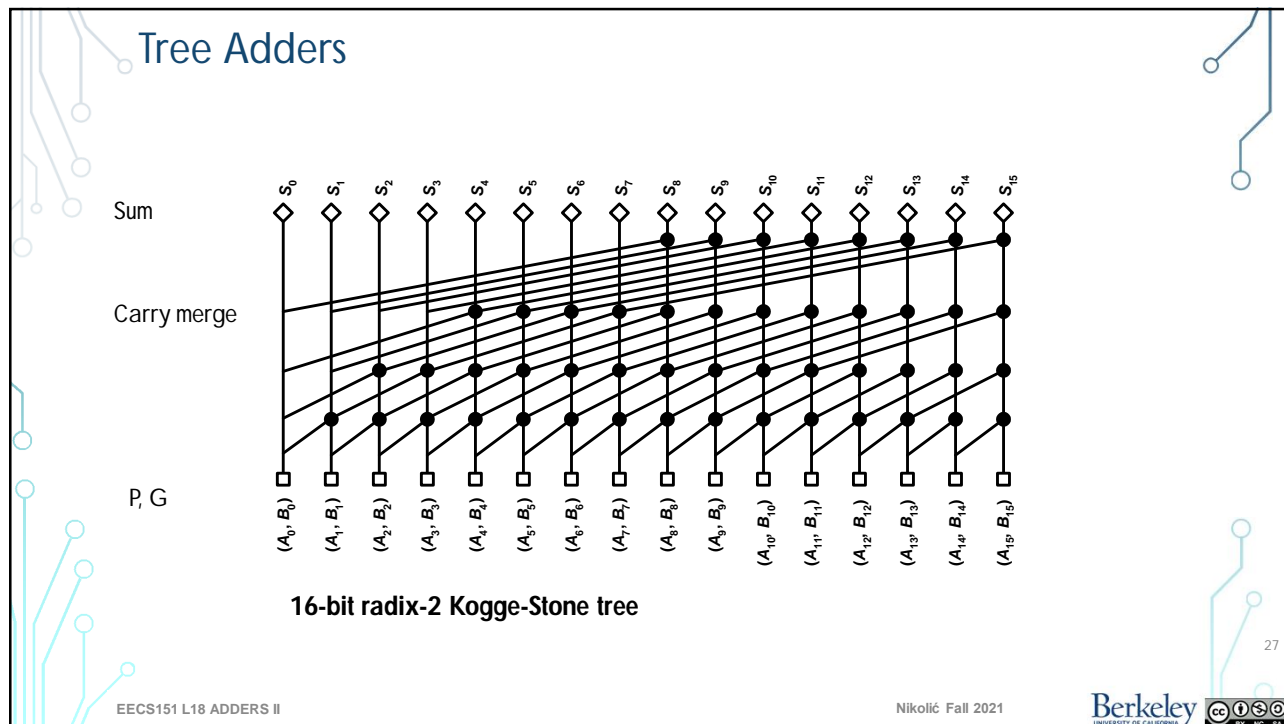


27

 

28

Sparse Trees

 

16-bit radix-2 sparse tree with sparseness of 2


EECS151 L18 ADDERS II

Nikolić Fall 2021



29

Tree Adders

 

Brent-Kung Tree

EECS151 L18 ADDERS II

Nikolić Fall 2021



30



Multipliers

EECS151 L18 ADDERS II

Nikolić Fall 2021

31

 Berkeley
 UNIVERSITY OF CALIFORNIA


31

Warmup

- Recall long multiplication of base-10 by hand:

$$\begin{array}{r} 12 \\ \times 56 \\ \hline \end{array}$$

- In base-2 (binary), we do the same thing:

$$\begin{array}{r} 011 \\ \times 101 \\ \hline \end{array}$$

EECS151 L18 ADDERS II

Nikolić Fall 2021

32

 Berkeley
 UNIVERSITY OF CALIFORNIA


32

Multiplication

$$\begin{array}{r}
 \begin{array}{cccc}
 a_3 & a_2 & a_1 & a_0 \\
 \times & b_3 & b_2 & b_1 & b_0
 \end{array}
 \end{array}
 \begin{array}{l}
 \leftarrow \text{Multiplicand} \\
 \leftarrow \text{Multiplier}
 \end{array}$$

$$\begin{array}{r}
 a_3b_0 \ a_2b_0 \ a_1b_0 \ a_0b_0 \\
 a_3b_1 \ a_2b_1 \ a_1b_1 \ a_0b_1 \\
 a_3b_2 \ a_2b_2 \ a_1b_2 \ a_0b_2 \\
 a_3b_3 \ a_2b_3 \ a_1b_3 \ a_0b_3
 \end{array}
 \left. \vphantom{\begin{array}{r} a_3b_0 \\ a_3b_1 \\ a_3b_2 \\ a_3b_3 \end{array}} \right\} \text{Partial products}$$

$$\dots \quad a_1b_0 + a_0b_1 \quad a_0b_0 \leftarrow \text{Product}$$

Many different circuits exist for multiplication.
 Each one has a different balance between *speed (performance)* and amount of *logic (energy, cost)*.

EECS151 L18 ADDERS II


Nikolić Fall 2021

33

 Berkeley
 UNIVERSITY OF CALIFORNIA


33

"Shift and Add" Multiplier

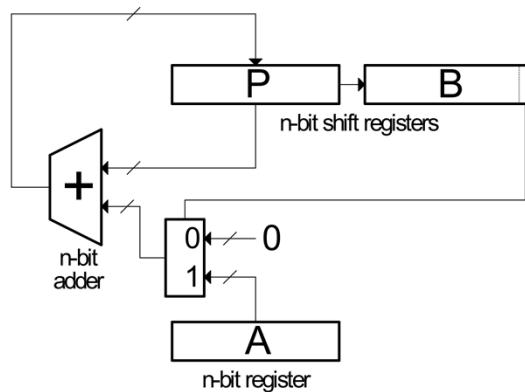

- Performance: N cycles of N -bit additions

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of A or 0 .

Control Algorithm:

1. $P \leftarrow 0$, $A \leftarrow$ multiplicand, $B \leftarrow$ multiplier
2. If LSB of $B = 1$ then add A to P
 else add 0
3. Shift $[P][B]$ right 1
4. Repeat steps 2 and 3 $(n-1)$ more times.
5. $[P][B]$ has product.

EECS151 L18 ADDERS II

Nikolić Fall 2021

34

 Berkeley
 UNIVERSITY OF CALIFORNIA


34

"Shift and Add" Multiplier

Signed Multiplication:

Remember for 2's complement numbers MSB has negative weight:

$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
 - a) subtract final partial product
 - b) sign-extend partial products
- Modifications to shift & add circuit:
 - a) adder/subtractor
 - b) sign-extender on P shifter register

35

Convince yourself

- What's -3×5 ?

$$\begin{array}{r} 1101 \\ \times 0101 \\ \hline \end{array}$$

36



Unsigned Parallel Multiplier

EECS151 L18 ADDERS II

Nikolić Fall 2021

37

 Berkeley
 UNIVERSITY OF CALIFORNIA


37


Parallel (Array) Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 & a_3 & a_2 & a_1 & a_0 \\
 * & b_3 & b_2 & b_1 & b_0 \\
 \hline
 & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 + & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 + & & & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 + & & & & a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 \\
 \hline
 p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0
 \end{array}
 \end{array}$$

 multiplicand
 multiplier

 Partial products, one for each bit in multiplier
 (each bit needs just one AND gate)

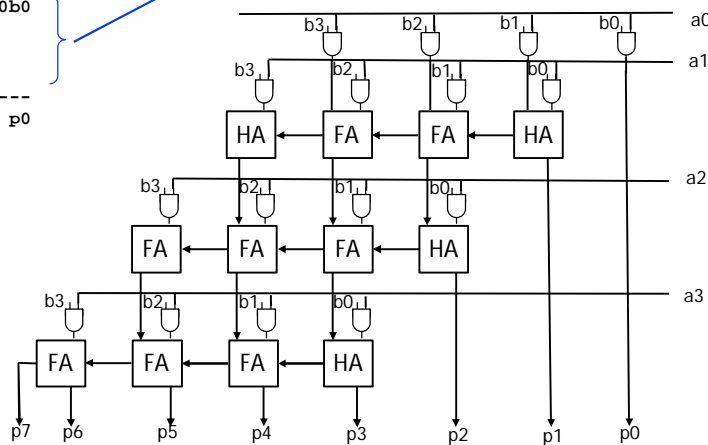- Performance: What is the critical path?



EECS151 L18 ADDERS II

Nikolić Fall 2021


38

 Berkeley
 UNIVERSITY OF CALIFORNIA


38

Parallel (Array) Multiplier

 Single cycle multiply: Generates all n partial products simultaneously.



39

Carry-Save Addition

- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- "Carry-save" addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.

Example: sum three numbers,


$$3_{10} = 0011, 2_{10} = 0010, 3_{10} = 0011$$

	3_{10}	0011	
	$+$	2_{10}	0010
		\hline	
	c	$0100 = 4_{10}$	} carry-save add
	s	$0001 = 1_{10}$	
carry-save add	$+$	3_{10}	0011
		\hline	
	c	$0010 = 2_{10}$	} carry-propagate add
	s	$0110 = 6_{10}$	
		$1000 = 8_{10}$	


- In general, *carry-save* addition takes in 3 numbers and produces 2: "3:2 compressor".
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition

40

Carry-Save Circuits

 

 - When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.
- Carry-save is fast (no carry propagation) and inexpensive (full adders)




EECS151 L18 ADDERS II

Nikolić Fall 2021

41 Berkeley

41

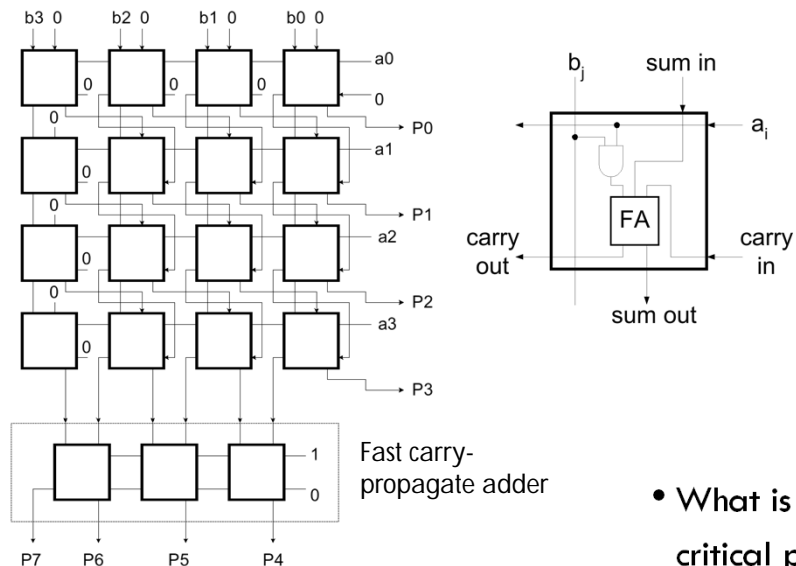Array Multiplier Using Carry-Save Addition



- What is the critical path?

EECS151 L18 ADDERS II

Nikolić Fall 2021


42 Berkeley

42

Carry-Save Addition

CSA is associative and commutative. For example:
 
$$((X_0 + X_1) + X_2) + X_3 = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay
- It doesn't matter where you add the carries and sums, as long as you eventually do add them
- This structure is the basis of the **Wallace Tree Multiplier**
- Partial products are summed with the CSA tree. Fast adder (ex: CLA) is used for final sum
- Multiplier delay $\propto \log_{3/2} N + \log_2 N$

EECS151 L18 ADDERS II

Nikolić Fall 2021

43




43


Wallace-Tree Multiplier

- Reduce the partial products in logic stages – 4 x 4 example


Partial products

 


First stage

 

Second stage

 

Final adder

 

EECS151 L18 ADDERS II


Nikolić Fall 2021

44



44

Wallace-Tree Multiplier

 

Note: Wallace tree is often slower than an array multiplier in FPGAs (which have optimized carry chains)

EECS151 L18 ADDERS II

Nikolić Fall 2021


45 Berkeley



45

Increasing Throughput: Pipelining

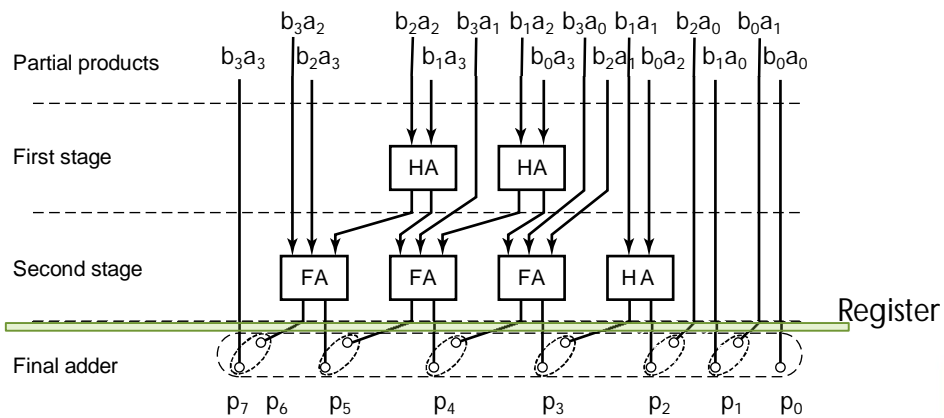- Multipliers have a long critical path: PP generation → reduction tree → final adder
 - Often pipelined before final adder (2x flip-flops for carry-save)



EECS151 L18 ADDERS II

Nikolić Fall 2021

46 Berkeley



46

Summary

- Adders

- Carry is in the adder critical path
- Mirror adders cells are commonly found in libraries
- Ripple-carry adder is the least complex, lowest energy
- Carry-bypass, carry-select are usually faster than ripple-carry for bitwidths > 8

- Multipliers

- Shift-and-add is the most compact
- Parallel multipliers