

inst.eecs.berkeley.edu/~eecs151

EECS151 : Introduction to Digital Design and ICs

Lecture 7 – Finite State Machines

Bora Nikolić



September 7, 2021, EETimes **5G Takes to the Stars**

Get ready to never have an excuse to be off the grid again. The latest update to the 5G New Radio (5G NR) standard will enable compatible devices to connect with 5G capable satellites anywhere in the world, without requiring specialist phones to get networked.



Artist's rendering of an Inmarsat-6 satellite, which will support 5G.
(Source: Inmarsat.)

EECS151 L07 FSMS

Nikolić, Fall 2021



1

Review

- Combinational logic:
 - The outputs only depend on the current values of the inputs (memoryless)
 - The functional specification of a combinational circuit can be expressed as:
 - A truth table
 - A Boolean equation
- Boolean algebra
 - Deal with variables that are either True or False
 - Map naturally to hardware logic gates
 - Use theorems of Boolean algebra and Karnaugh maps to simplify equations
- Finite state machines: Common example of sequential logic
- Common job interview questions 😊

EECS151 L07 FSMS

Nikolić, Fall 2021



2



Finite-State Machines

EECS151 L07 FSMS


Nikolić, Fall 2021

 3 Berkeley
 UNIVERSITY OF CALIFORNIA


3

Sequential logic

- **Combinational logic:**
 - Memoryless: the outputs only dependent on the current inputs.
- **Sequential logic:**
 - **Memory:** the outputs depend on both current and previous values of the inputs.
 - Distill the prior inputs into a smaller amount of information, i.e., states.
 - **State:** the information about a circuit
 - Influences the circuit's future behavior
 - Stored in Flip-flops and Latches
 - **Finite State Machines:**
 - Useful representation for designing sequential circuits
 - As with all sequential circuits: output depends on present and past inputs
 - We will first learn how to design by hand then how to implement in Verilog.

 

EECS151 L07 FSMS

Nikolić, Fall 2021



 4 Berkeley
 UNIVERSITY OF CALIFORNIA


4

FSM Example

• Cat Brain (Simplified...)

  - Inputs:
 - Feeding
 - Petting
- Outputs:
 - Eyes: open or close
 - Mouth: open or close
- States:
 - Eating
 - Sleeping
 - Annoyed...



EECS151 L07 FSMS


Nikolić, Fall 2021

5 Berkeley UNIVERSITY OF CALIFORNIA

5

FSM State Transition Diagram

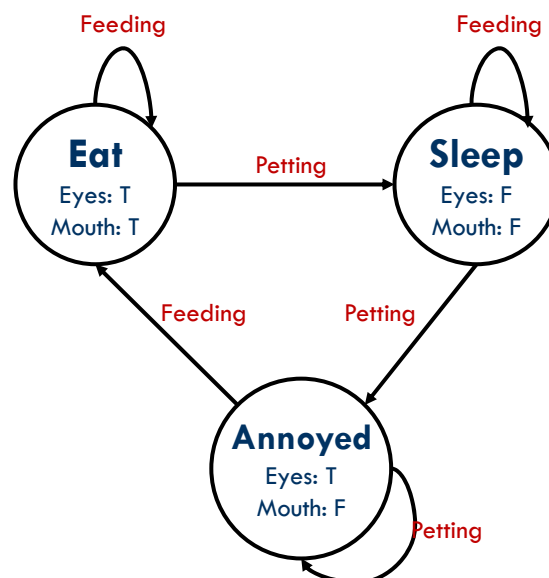- States:
 - Circles
- Outputs:
 - Labeled in each state
 - Arcs
- Inputs:
 - Arcs



EECS151 L07 FSMS


Nikolić, Fall 2021

6 Berkeley UNIVERSITY OF CALIFORNIA

6

FSM Symbolic State Transition Table

Current State	Inputs	Next State
Eat	Feeding	Eat
Eat	Petting	Sleep
Sleep	Feeding	Sleep
Sleep	Petting	Annoyed
Annoyed	Feeding	Eat
Annoyed	Petting	Annoyed

 

EECS151 L07 FSMS

Nikolić, Fall 2021

 7 Berkeley
 UNIVERSITY OF CALIFORNIA

7


FSM Encoded State Transition Table

State	Encoding
Eat	00
Sleep	01
Annoyed	10

Current State		Input	Next State	
S1	S0	X	S1'	S0'
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0

$$S0' = \overline{S1}S0X + \overline{S1}S0\bar{X} = \overline{S1}(S0X + S0\bar{X}) = \overline{S1}(S0 \oplus X)$$
 
$$S1' = \overline{S1}S0X + S1\overline{S0}X = (S1 \oplus S0)X$$




Current State	Inputs	Next State
Eat	Feeding	Eat
Eat	Petting	Sleep
Sleep	Feeding	Sleep
Sleep	Petting	Annoyed
Annoyed	Feeding	Eat
Annoyed	Petting	Annoyed

EECS151 L07 FSMS


Nikolić, Fall 2021

 8 Berkeley
 UNIVERSITY OF CALIFORNIA

8

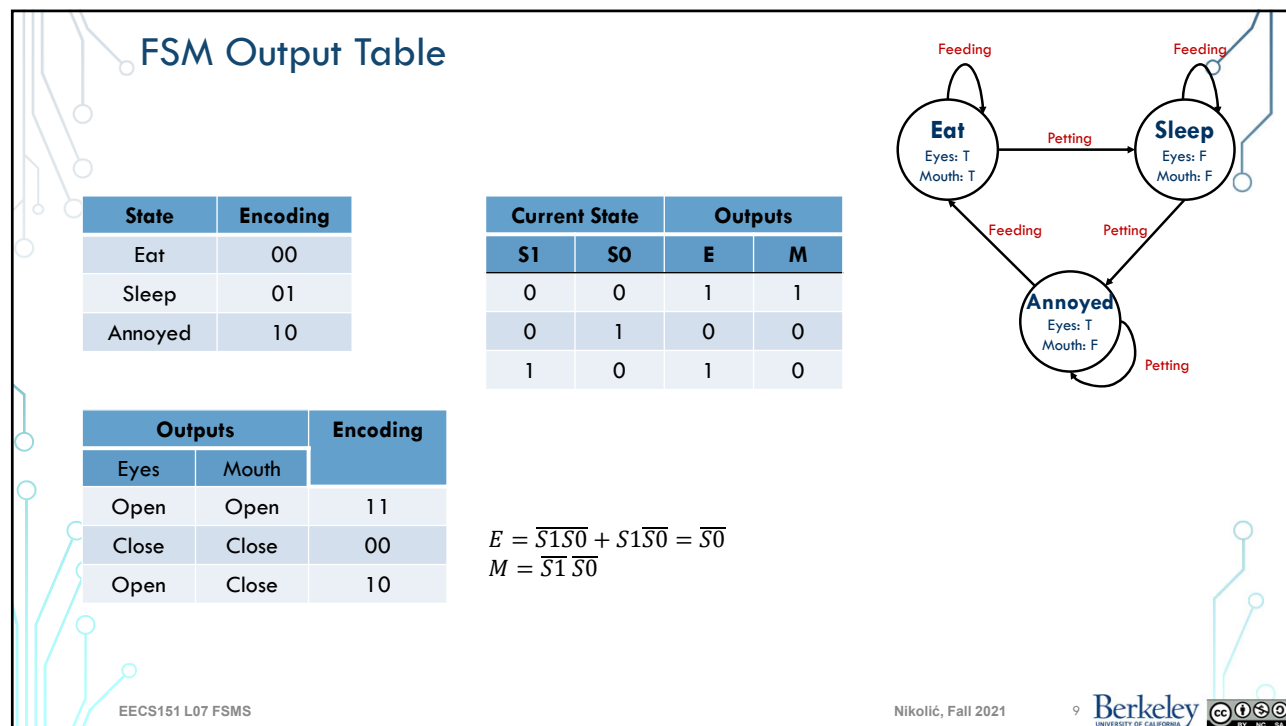

9

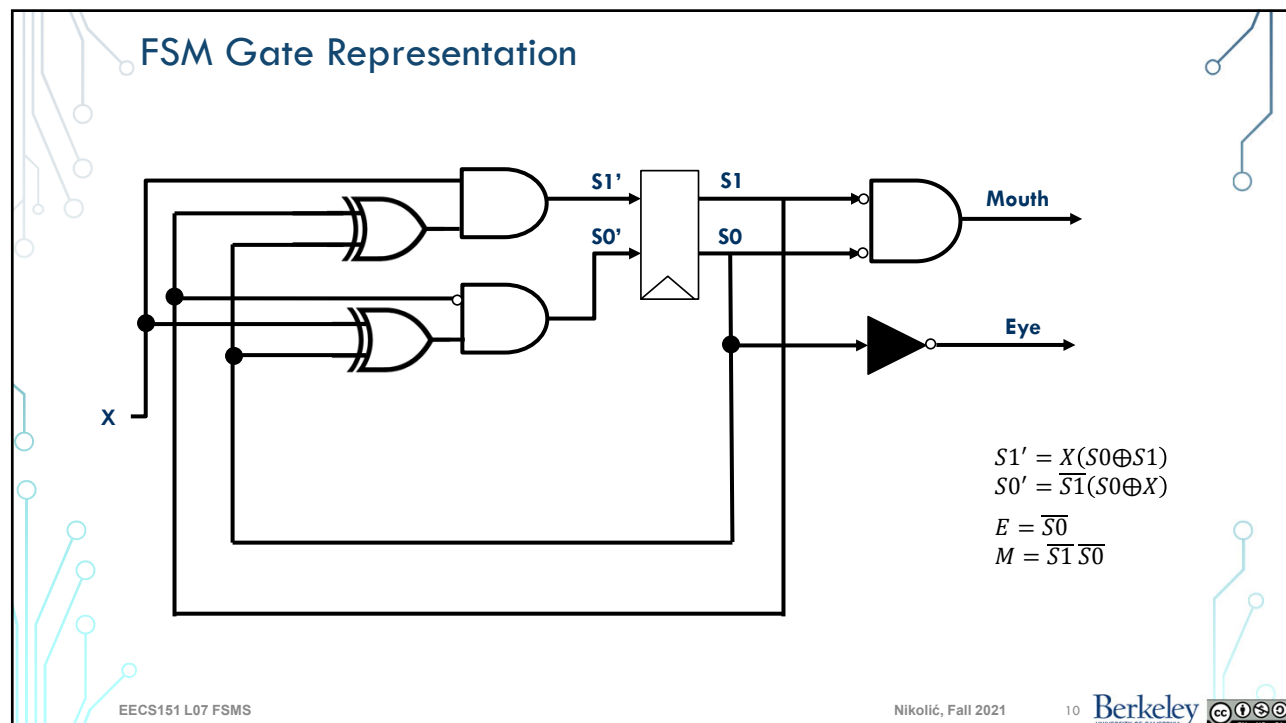

10

FSM Design Process

- Specify circuit function
- Draw state transition diagram
- Write down symbolic state transition table
- Write down encoded state transition table
- Derive logic equations
- Derive circuit diagram
 - Register to hold state
 - Combinational logic for next state and outputs

EECS151 L07 FSMS

Nikolić, Fall 2021

11




11

FSM State Encoding

- Binary encoding:
 - i.e., for four states, 00, 01, 10, 11
- One-hot encoding
 - One state bit per state
 - Only one state bit TRUE at once
 - i.e., for four states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic can be simpler

EECS151 L07 FSMS

Nikolić, Fall 2021

12




12

Administrivia

- Homework 3 is due next Monday
 - Homework 4 will be posted this week, due before midterm 1
- Lab 4 this week
- Lab 5 next week
- Midterm 1 on October 7, 7-8:30pm

EECS151 L07 FSMS

Nikolić, Fall 2021

13 Berkeley
UNIVERSITY OF CALIFORNIA

13



Moore and Mealy FSMs

EECS151 L07 FSMS

Nikolić, Fall 2021


14 Berkeley
UNIVERSITY OF CALIFORNIA

14


Moore's vs Mealy's FSMs

- Next state is always determined by current state and inputs
- Differ in output logic:
 - Moore FSM: outputs depend only on current state
 - Mealy FSM: outputs depend on current state and inputs

Moore FSM

 

Mealy FSM

 

EECS151 L07 FSMS

Nikolić, Fall 2021


15 Berkeley UNIVERSITY OF CALIFORNIA



15

 Example: Edge Detector

- Input:
 - A bit stream that is received one bit at a time.
- Output:
 - 0/1
- Circuit:
 - Asserts its output to be true when the input bit stream changes from 0 to 1.



EECS151 L07 FSMS


Nikolić, Fall 2021

16 Berkeley UNIVERSITY OF CALIFORNIA



16

State Transition Diagram Solution A

 

Input	Current State	Next State	Output
0	Zero (00)	Zero	0

EECS151 L07 FSMS

Nikolić, Fall 2021


17

Berkeley



17

State Transition Diagram Solution A

 

Input	Current State	Next State	Output
0	Zero (00)	Zero	0
1	Zero (00)	Change	0
0	Change (01)	Zero	1
1	Change (01)	One	1
0	One (11)	Zero	0
1	One (11)	One	0

EECS151 L07 FSMS

Nikolić, Fall 2021

18

Berkeley



18

State Transition Diagram Solution A

CS = {CS1, CS0}

	00	01	11	10
IN 0	0	0	0	-
IN 1	0	1	1	-

$NS_1 = \text{IN AND CS0}$


	00	01	11	10
IN 0	0	0	0	-
IN 1	1	1	1	-

$NS_0 = \text{IN}$

	00	01	11	10
IN 0	0	1	0	-
IN 1	0	1	0	-

$\text{OUT} = \text{NOT}(\text{CS1}) \text{ AND CS0}$

Input	Current State	Next State	Output
0	Zero (00)	Zero	0
1	Zero (00)	Change	0
0	Change (01)	Zero	1
1	Change (01)	One	1
0	One (11)	Zero	0
1	One (11)	One	0

 

EECS151 L07 FSMS


Nikolić, Fall 2021

19 Berkeley UNIVERSITY OF CALIFORNIA




19

State Transition Diagram Solution B

 

Input	Current State	Next State	Output
0	Zero (0)	Zero	0
1	Zero (0)	One	1
0	One (1)	Zero	0
1	One (1)	One	0

 

EECS151 L07 FSMS


Nikolić, Fall 2021

20 Berkeley UNIVERSITY OF CALIFORNIA



20

Edge Detection Timing Diagrams

 

- Solution A (Moore) : both edges of output follow the clock
- Solution B (Mealy) : output rises with input rising edge and is asynchronous wrt the clock, output falls synchronous with next clock edge

EECS151 L07 FSMS

Nikolić, Fall 2021

21




21

FSM Comparison


Solution A Moore Machine

 - output function only of current state
- maybe more states (why?)
- **synchronous** outputs
 - Input glitches not sent to output
 - one cycle "delay"
 - full cycle of stable output



Solution B Mealy Machine

 - output function of both current state & input
- maybe fewer states
- **asynchronous** outputs
 - if input glitches, so does output
 - output immediately available
 - output may not be stable long enough to be useful (below):



If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge (or violate setup time requirement)

EECS151 L07 FSMS


Nikolić, Fall 2021

22



22

 
Quiz: Which of the diagrams are **Moore** machines?




A.

B.

- A. AC
- B. BD
- C. AD
- D. BC

 

C.

 

D.

www.yellkey.com/oil

EECS151 L07 FSMS

Nikolić, Fall 2021

23 Berkeley



23



FSMs in Verilog

EECS151 L07 FSMS

Nikolić, Fall 2021

24 Berkeley



24

Implement FSM with Verilog

- Specify circuit function
- Draw state transition diagram
- Write down symbolic state transition table
- Assign encodings (bit patterns) to symbolic states
- Code as Verilog behavioral description
 - Use parameters to represent encoded states
 - Use separate always blocks for register assignment and combinational logic block
 - Use case statement for combinational logic.
 - Within each case section (state), assign outputs and next state based on inputs
 - Moore: outputs only dependent on states not on inputs

EECS151 L07 FSMS

Nikolić, Fall 2021

25


Berkeley



25


Finite State Machine in Verilog

State Transition Diagram

 

Holds a symbol to keep track of which bubble the FSM is in.

Circuit Diagram

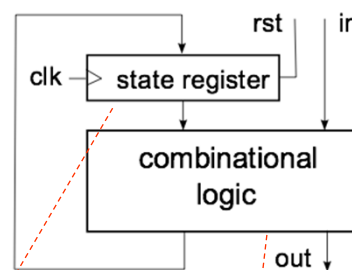

CL functions to determine output value and next state based on input and current state.

$out = f(in, \text{current state})$

$next\ state = f(in, \text{current state})$

EECS151 L07 FSMS

Nikolić, Fall 2021

26

Berkeley



26

Finite State Machine in Verilog

```

module FSM1(clk, rst, in, out);
  input clk, rst;
  input in;
  output out;

  // Defined state encoding:
  parameter IDLE = 2'b00;
  parameter S0 = 2'b01;
  parameter S1 = 2'b10;
  reg out;
  reg [1:0] current_state, next_state;

  // always block for state register
  always @(posedge clk)
    if (rst) current_state <= IDLE;
    else current_state <= next_state;

```


Must use reset to force to initial state.
reset not always shown in STD

Constants local to this module.

Combinational logic signals for transition.

THE register to hold the "state" of the FSM.

 A separate always block should be used for combination logic part of FSM. Next state and output generation. (Always blocks in a design work in parallel.)



EECS151 L07 FSMS

Nikolić, Fall 2021

27

Berkeley



27

Finite State Machine in Verilog (cont.)

```


// always block for combinational logic portion
always @(current_state or in)
  case (current_state)
    // For each state def output and next
    IDLE : begin
      out = 1'b0;
      if (in == 1'b1) next_state = S0;
      else next_state = IDLE;
    end
    S0 : begin
      out = 1'b0;
      if (in == 1'b1) next_state = S1;
      else next_state = IDLE;
    end
    S1 : begin
      out = 1'b1;
      if (in == 1'b1) next_state = S1;
      else next_state = IDLE;
    end
    default: begin
      next_state = IDLE;
      out = 1'b0;
    end
  endcase
endmodule

```

Each state becomes a case clause.

For each state define:
Output value(s)
State transition

 Use "default" to cover unassigned state. Usually unconditionally transition to reset state.



EECS151 L07 FSMS

Nikolić, Fall 2021

28

Berkeley



28

Finite State Machine in Verilog (cont.)

```

always @*
begin
  next_state = IDLE;
  out = 1'b0;
  case (state)
    IDLE : if (in == 1'b1) next_state = S0;
    S0   : if (in == 1'b1) next_state = S1;
    S1   : begin
              out = 1'b1;
              if (in == 1'b1) next_state = S1;
            end
    default: ;
  endcase
end
endmodule


```

* for sensitivity list

Nominal values: used unless specified below.

Within case only need to specify exceptions to the nominal values.

 Note: The use of "blocking assignments" allow signal values to be "rewritten" (evaluated immediately), simplifying the specification.



EECS151 L07 FSMS

Nikolić, Fall 2021

29


Berkeley




29

Edge Detector Example

Mealy Machine

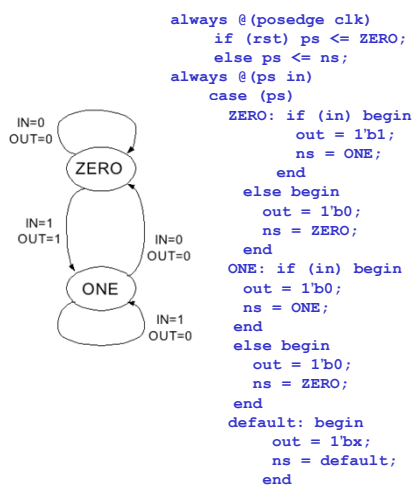

Moore Machine

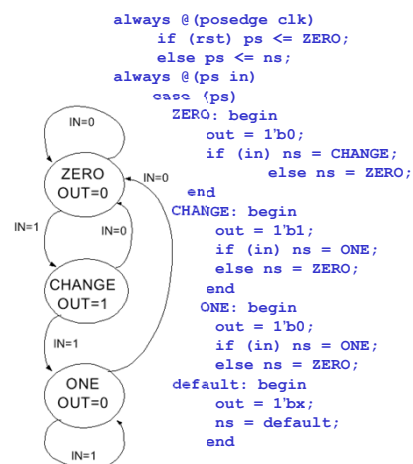

EECS151 L07 FSMS

Nikolić, Fall 2021

Berkeley



30

Summary

- Finite state machines: Common example of sequential logic
 - Moore's machine: Output depends only on the current state
 - Mealy's machine: Output depends on the current state and the input
- Large state machines can be factored
- Common Verilog patterns for FSMs
- Common job interview questions 😊