

<div style="text-align: center; font-size: 2em; color: blue; font-weight: bold;">SOLUTION</div> <hr/> Your Name (first last) <hr/> ← Name of person on left (or aisle)	UC Berkeley EECS151 EECS251A Fall 2021 Midterm 2 Room _____ <hr/> Lab TA name	<hr/> <div style="text-align: right;"><i>SID</i></div> <hr/> Name of person on right (or aisle) →

Fill in your student ID at the top of every page.

Question	1	2	3	4	5	6	Total
Minutes	16	10	12	12	12	13	75
Max Points (151)	12	8	12	12	6	11	61
Max Points (251A)	16	8	12	12	12	11	71
Points							

SID : _____

1) CMOS logic (16 points, 16 minutes)

A slightly unusual logic gate is shown in Figure 1.


 



Figure 1.

- a) (4 pts) For all the possible combinations of inputs A and B find the output voltage levels. Supply voltage is V_{DD} and transistors have a threshold of $|V_{Th}|$.


A	B	Y
0	0	V_{DD}
0	V_{DD}	0
V_{DD}	0	0
V_{DD}	V_{DD}	$V_{DD} - V_{Th} $

 

$A=0 \quad B=0$

 


$A=0 \quad B=V_{DD}$

 

$A=V_{DD} \quad B=0$

 - b) (4 pts) What logic function $Y = f(A, B)$ is implemented by this network?

$Y = \underline{\text{XNOR } (A \oplus B)}$



$A=V_{DD} \quad B=V_{DD}$

SID : _____

- c) (4 pts) As you are browsing a library of standard cells, you find one without any schematic or notes about its function. Being a curious person, you decide to investigate this mysterious layout, so you jot down the following stick diagram:


 


Figure 2.


 
Active-n and Active-p are n- and p-type diffusions, respectively, and Poly is the gate. What is the logic function of the circuit described by the stick diagram from Figure 2?



$$Y = (A + B + C) \cdot D \cdot E$$

SID : _____

  - d) (4 pts) (**EECS251A only**) You realize that someone who did not take this class made the layout in Figure 2, because it is clearly not optimal. Reorder the inputs A, B, D, E, C (for the exact same logic gate) such that the layout can be realized with no diffusion breaks while still having straight polysilicon gates.



Ordering: ABCE D

SID : _____

2) Logic delay (8 points, 10 minutes)

The delay of two logic gates, an inverter and a 2-input NOR, has been measured, and the results are plotted in Figure 3.

 


Figure 3.

- a) (4 pts) Inverter delay can be modeled as $\overset{\text{ps}}{\downarrow} t_{pinv} = \overset{\text{ps}}{\downarrow} t_{p0} (\overset{\text{unitless}}{\downarrow} p_{inv} + C_L/C_{in})$. Find the values of t_{p0} , and p_{inv} from the graph.

$$\text{slope} = t_{p0} = \frac{50 - 10}{4 - 0} = 10 \text{ ps}.$$

$$\text{When } C_L/C_{in} = 0, \quad 10 = 10 \cdot (p_{inv} + 0)$$

$$\Rightarrow p_{inv} = 1$$

$$t_{p0} = \underline{10 \text{ ps}}.$$

$$p_{inv} = \underline{1}.$$

SID : _____

b) (4 pts) Find the logical effort and the intrinsic delay of the NOR2 from the graph.

$$t_{p_{nor2}} = t_{p0} (p_{nor2} + g_{nor2} \frac{C_L}{C_{in}})$$

$$\text{slope} = t_{p0} \cdot g_{nor2} = 10 g_{nor2}$$

$$= \frac{75 - 25}{4 - 0} = 12.5$$

$$\Rightarrow g_{nor2} = 1.25$$

$$\text{When } C_L / C_{in} = 0, \quad 25 = 10(p_{nor2} + 1.25 \times 0)$$

$$\Rightarrow p_{nor} = 2.5$$

$$g_{NOR2} = \underline{1.25}$$

$$p_{NOR2} = \underline{2.5}$$

SID : _____

3) Fast circuits (12 points, 12 minutes)

A decoder logic path is shown in Figure 4. C_{in} , a and b are the capacitances of input pins of respective gates. Equally sized PMOS and NMOS transistors have equal on resistances and the self-loading capacitance per unit width equals the input capacitance ($\gamma = C_p/C_g = 1$).

 


Figure 4.

a) (4 pts) What is the path effort from In to Out?

$$F = 32$$
$$G = (2)(1)(2)$$
$$B = 4$$

$$g_{NAND3} = 2$$

$$GFB = (4)(32)(4)$$

Path effort: $H = 512$.

b) (4 pts) What effort per stage, h , minimizes the delay of this decoder?

$$3 \text{ stages} \rightarrow \sqrt[3]{512}$$

Effort per stage: $h = 8$.

SID : _____

c) (4 pts) Size the gates to minimize the delay from In to Out:

 


Figure 4, repeated for convenience

$$EF_{\text{stage}} = 8$$

$$EF_b = LE_b \cdot f_b$$

$$8 = 2 \cdot \frac{32C_{in}}{b}$$

$$b = 8C_{in}$$

$$EF_a = LE_a \cdot f_a \cdot 4$$

$$8 = 1 \cdot \frac{b}{a} \cdot 4$$

$$a = 4C_{in}$$

check:

$$8 = 2 \cdot \frac{4C_{in}}{C_{in}} \checkmark$$

Gate	Input capacitance, normalized to C_{in}
a	4
b	8

4) Energy (12 points, 12 minutes)

We would like to examine some properties of a single-cycle RISC-V datapath. The datapath has the following properties:

- Total capacitance of all gates: 10nF
- Max Frequency @ 1.0V: 200 MHz
- Supply voltage: 1.0V

The CPU runs a workload with the following properties:

- Activity factor α : 0.1
- Number of instructions: 1000

In this question, you may ignore leakage and short-circuit power (though this is unwise in a real design).

a) (2 pts) What is the dynamic power consumption?

$$0.1 * 10 \text{ nF} * (1.0 \text{ V})^2 * 200 \text{ MHz} = 200 \text{ mW}$$

P = _____ mW.

b) (2 pts) How much energy is consumed by this workload?

$$\begin{aligned} & 200 \text{ mW} * \frac{1 \frac{\text{cycle}}{\text{inst}}}{200 * 10^6 \frac{\text{cycle}}{\text{s}}} * 1000 \text{ inst} \\ &= 0.2 \frac{\text{J}}{\text{s}} * 0.5 * 10^{-8} \frac{\text{s}}{\text{inst}} * 1000 \text{ inst} \\ &= 0.1 * 10^{-8} \frac{\text{J}}{\text{inst}} * 1000 \text{ inst} \\ &= 0.1 * 10^{-5} \text{ J} = 1 \mu\text{J} \end{aligned}$$

E = _____ μJ .

c) (8 pts) If we lower the the supply to 0.9V:

- The new clock frequency will be (assuming that the drain current is linearly proportional to supply voltage):

$$200 \text{ MHz} * \frac{0.9 \text{ V}}{1.0 \text{ V}} = 180 \text{ MHz}$$

$$f_{\text{clk}} = \underline{\hspace{2cm}} \text{ MHz.}$$

- The compute time for the workload will be:

$$\begin{aligned} & 1000 \text{ inst} * 1 \frac{\text{cycle}}{\text{inst}} * \frac{1}{180 * 10^6 \frac{\text{cycle}}{\text{s}}} \\ &= 1000 \text{ cycle} * \frac{1}{180} * 10^{-6} \frac{\text{s}}{\text{cycle}} \\ &= \frac{1}{180} * 10^{-3} \text{ s} \\ &= \frac{1}{180} \text{ ms} \\ &= \frac{1000}{180} \mu\text{s} = \frac{50}{9} \mu\text{s} = 5.56 \mu\text{s} \end{aligned}$$

$$T = \underline{\hspace{2cm}} \mu\text{s.}$$

- The new total energy will be:

$$\begin{aligned} P &= 0.1 * 10 \text{ nF} * (0.9 \text{ V})^2 * 180 \text{ MHz} = 145.8 \text{ mW} \\ E &= P * T = 145.8 \text{ mW} * 5.56 \mu\text{s} = 0.81 \mu\text{J} \end{aligned}$$

$$E = \underline{\hspace{2cm}} \mu\text{J.}$$

SID : _____

5) Wires (6/12 points, 12 minutes)


 
 


Figure 5.

A pair of inverters are shown in Figure 5. The input inverter is unit-sized, with an on-resistance R and an input capacitance that equals self-loading capacitance of C ($\gamma = 1$). The second inverter has a size that is x times the unit inverter. A wire in between the two inverters has the resistance R and capacitance C that equals the input capacitance and on-resistance of a unit inverter. Output capacitance, C_L , is 10 times the unit capacitance. The delay of a fanout-of-1 inverter is 10ps.

- a) (6 pts) Find the propagation delay from input (In) to the output (Out), for $x = 1$. When calculating the delay, assume that both inverters have step transitions at their inputs.

① RC Circuit

 


② $\tau_d = C(R) + (2C)(2R) + (11C)(R)$
 $= RC + 4RC + 11RC = 16RC$

④ $t_d = \ln(2) \cdot \tau_d = \ln(2) \cdot 16RC$
 $= 2\ln(2)RC \cdot 8$
 $= 10ps \cdot 8$



F01 Inverter:

 


③ $t_{F01} = \ln(2)R(2C)$
 $= 10ps$

tp= 80 ps.

SID : _____

b) (6 pts) (EECS251A only) Find the size of the second inverter, x , that minimizes the propagation delay.

RC Circuit

 

$$\textcircled{1} \tau_d = C(R) + (C + Cx)(2R) + (Cx + 10C)\left(\frac{R}{x}\right)$$

$$= RC + 2RC + 2RCx + RC + 10RC/x$$

$$= 4RC + 2RCx + 10RC/x$$

$$\frac{\partial \tau_d}{\partial x} = 2RC - \frac{10RC}{x^2} = 0$$

$\textcircled{2}$

$$\frac{10RC}{x^2} = 2RC$$

$$x^2 = \frac{10RC}{2RC} = 5 \rightarrow x = \sqrt{5}$$

$\textcircled{3}$

$x = \underline{\sqrt{5}}$

SID : _____

6) Adders (11 points, 13 minutes)

- a) (4 pts) A single-bit full adder, with inputs A, B and C_i and outputs C_o and S, is shown in Figure 6. In this case, the propagate signal P, is defined as $P = A \oplus B$. Please fill in the boxes with signals (A, B, C_i), or their complements, that would make the adder operate correctly. Also, please label the corresponding multiplexed inputs as 0 or 1.

 


Figure 6

A	B	C_i	P	C_o
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

$$\begin{aligned}
 P &= A \oplus B \\
 &= \bar{A}B + \bar{B}A \\
 S &= A \oplus B \oplus C_i \\
 &= P \oplus C_i = \bar{P}C_i + \bar{C}_iP
 \end{aligned}$$

$$\begin{aligned}
 P &= A \oplus B \\
 C_o &= AB + (A + B)C_i
 \end{aligned}$$

SID : _____

- b) (6 pts) Consider a carry-bypass (sometimes called 'carry-skip') adder, shown in Figure 7. Each full adder cell (labeled as a '+' box in the diagram) can be assumed to have one multiplexer delay from C_i to C_{i+1} and one multiplexer delay from C_i to S_i . You can assume that the sum and carry paths have been realized by the circuits from part a) and therefore have equal delays. For an N-bit adder divided into k uniform b-bit groups, find the optimal b that minimizes the overall delay from $C_{i,0}$ to S_{N-1} (in terms of N).

 


Figure 7

$$t_{p_{C_{i,0} \rightarrow S_{N-1}}} = b \cdot t_{\text{carry}} + \left(\frac{N}{b} - 1\right) t_{\text{mux}} + (b-1) t_{\text{carry}} + t_{\text{sum}}$$

$$= b \cdot t_{\text{mux}} + \left(\frac{N}{b} - 1\right) t_{\text{mux}} + (b-1) t_{\text{mux}} + t_{\text{mux}}$$

$$\frac{dt_{p_{C_{i,0} \rightarrow S_{N-1}}}}{db} = t_{\text{mux}} - \frac{N}{b^2} t_{\text{mux}} + t_{\text{mux}}$$

$$0 = 2t_{\text{mux}} - \frac{N}{b^2} t_{\text{mux}}$$

$$\frac{N}{b^2} = 2, \quad b^2 = \frac{N}{2}, \quad b = \sqrt{N/2}$$

b = $\sqrt{\frac{N}{2}}$ bits.

- c) (1 pt) Evaluate part b) for N=128

b = $\sqrt{\frac{128}{2}}$ bits.

$$\sqrt{\frac{128}{2}} = \sqrt{64} = 8$$