

# EECS 151/251A

## Discussion 12

Zhaokai Liu


# Agenda

- SRAMs
  - Architecture
  - 6T SRAM Read
  - 6T SRAM Write
  - Multi-Voltage SRAM
- Memory decoding
  - Design example

# SRAMs


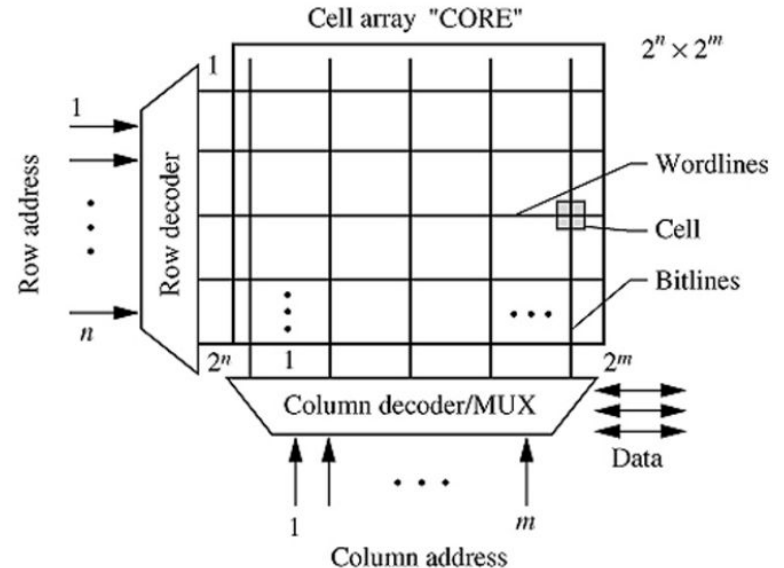
# SRAM Architecture

- Grid of SRAM bitcells:
  - width = word size
  - height = # of words
- **Bitlines** (vertical) are shared across cells in a column
  - Long wires with a large capacitive load (drains of access transistors, read/write circuits)
- **Wordlines** (horizontal) are shared across cells in a row
  - Also long with large capacitive load (gates of access transistors)
- Peripheral circuitry (bitline drivers, sense amp, decoders)
  - Need to reduce the total number of pins,  $N+M$  address lines for  $2^{(N+M)}$
  - Ex: if  $N+M=20 \rightarrow 2^{20} = 1 \text{ Mb}$



 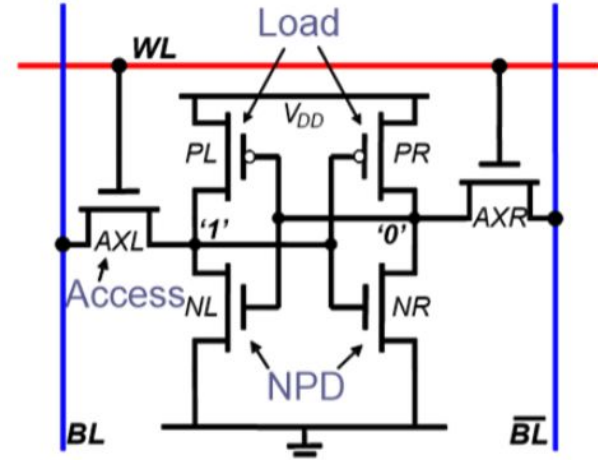
# The 6T SRAM Cell

- Inverters (PL NL and PR NR)
  - in positive feedback form the memory element (like a latch!)
- AXL and AXR are the access transistors
  - Allow the bitlines to access the memory nodes (Q, Qbar) when WL = 1
- Only 1 WL in an SRAM array is active at a time
  - Addresses an entire row of SRAM cells
- Bitlines are controlled differently for read and write




# 6T SRAM Cell: 3 Modes of Operation


*Write*

 

*Retention*

 



*Read*

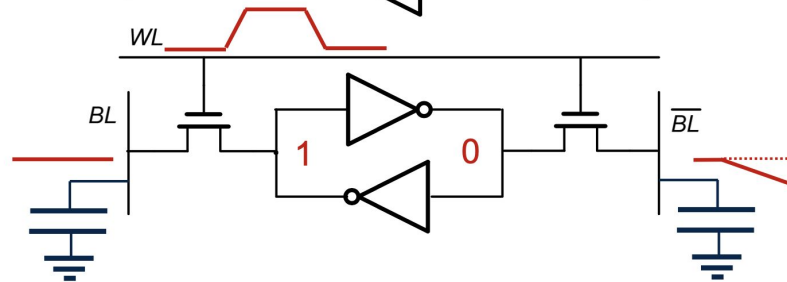
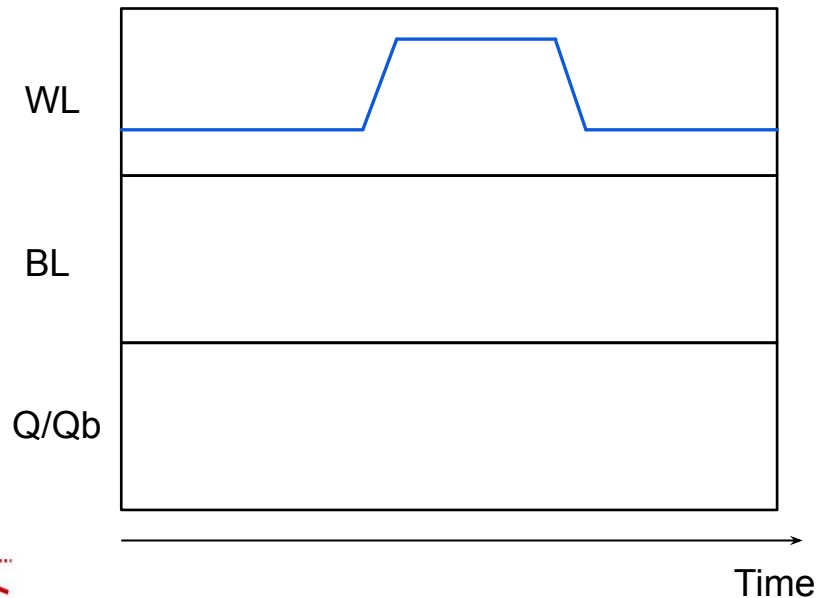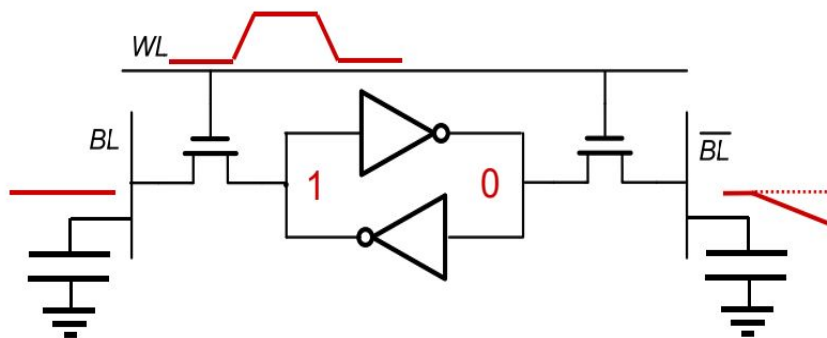
# SRAM Read Operation


- Procedure:

- Precharge BL and BLbar to VDD
- Raise WL
- Sense dip on one bitline with sense amp
- Lower WL
- Discharge bitlines



 
# SRAM Read Stability

- Read stability = reading doesn't corrupt the value stored in Q and Qbar
  - a. The access transistor shouldn't overpower the node storing a '0' and flip its state
  - b. Sizing: make the latch NMOS stronger than the access transistor = ( $W_n > W_{\text{access}}$ )



Equivalent Circuit


 


Read SNM



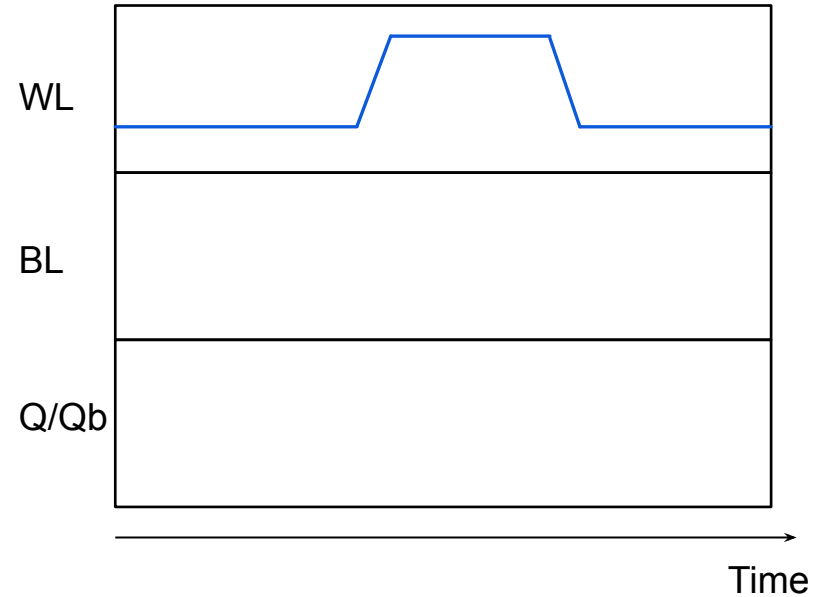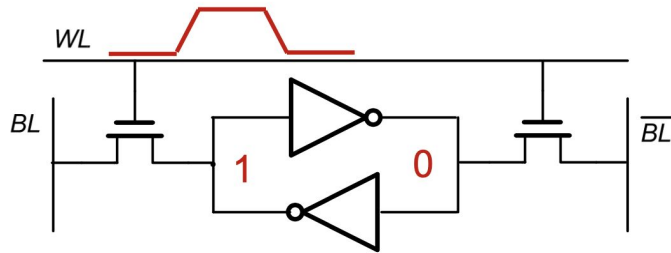
# SRAM Write Operation

- Procedure:
  - Drive BL and BLbar with data to write
  - Raise WL
  - Wait some amount of time (write time)
  - Lower WL
  - Discharge bitlines



 
# SRAM Write

- Write-ability = the cell's memory value can be changed
  - a. Access transistor must overpower latch
  - b. Assuming the cell is read stable ( $W_n > W_{\text{access}}$ ), the node with '0' can't be overpowered => so we must overpower PMOS ( $W_{\text{access}} > W_p$ ) and override the '1' node




Equivalent Circuit

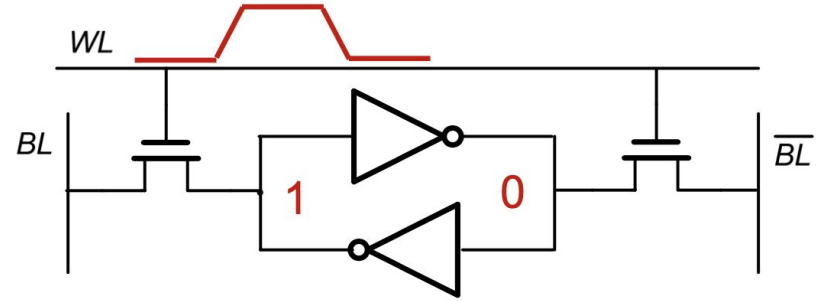


Write SNM
 
# Conflicts between read and write

Size 6T the SRAM cell for optimized read and write operation separately:




## Read optimized

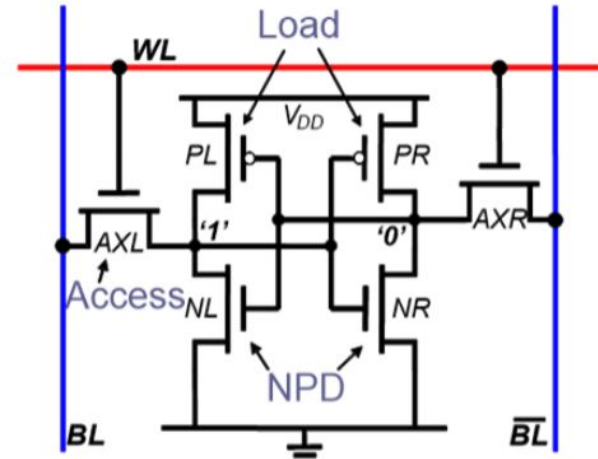

## Write optimized
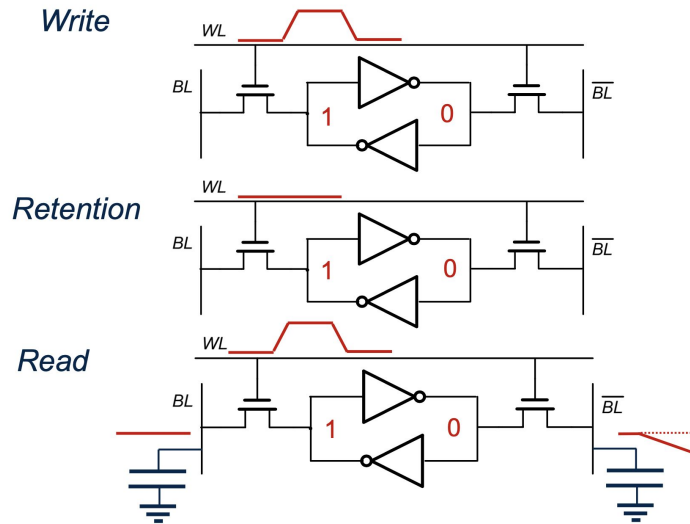
# Multi-Voltage SRAM

You have 3 high voltage levels to choose: 0.9V, 1.0V(ref), 1.1V;  
3 low voltages: -0.1V, 0V(ref), 0.1V  
Which voltage is preferred?



	Readability	Read Stability	Writability
WL			
BL			
VDD			
GND			

# Memory Decoders

# 2-Stage Decoding

- Problem: each distinct address  $\Rightarrow$  1 WL
  - Binary-to-thermometer conversion!
  - Naive method: each WL has its own NAND + inverter tree (a lot of load & logic!)
- 2-stage decoding: predecoders and final decoders
  - Decode some bits first, then the rest (MSB/LSB doesn't matter)
  - Larger predecode is better (this is just a path delay w/ branching problem)

