

# EECS151 : Introduction to Digital Design and ICs


## Lecture 11 – CMOS

**Bora Nikolić**


 
### Intel Unveils Second-Generation Neuromorphic Chip

October 5, 2021, Intel has unveiled its second-generation neuromorphic computing chip, Loihi 2, the first chip to be built on its Intel 4 process technology. Designed for research into cutting-edge neuromorphic neural networks, Loihi 2 brings a range of improvements. They include a new instruction set for neurons that provides more programmability, allowing spikes to have integer values beyond just 1 and 0, and the ability to scale into three-dimensional meshes of chips for larger systems.



Intel's Loihi 2 second-generation neuromorphic processor. (Source: Intel)

EETimes

# Review

- Core FPGA building blocks:
  - Configurable Logic Blocks (CLBs)
  - Configurable Interconnect
    - Switch boxes
- Modern FPGA Designs:
  - BRAMs, DSPs, and AI Engines
- CMOS process is used for producing chips
  - Planar bulk process used up to 28nm node
  - finFET and FDSOI used below the 22nm node




# MOS Transistors




# MOS Transistors

- Symbol

N-type  
NMOS

 




P-type  
PMOS

   




- Devices are symmetrical
  - NMOS: Drain is at higher voltage
  - PMOS: Source is at higher voltage

# Different Kinds of MOS Transistors


- Planar bulk CMOS

   

- FinFET

   

Intel 10nm  
IEDM 2017


 


# Transistor Dimensions are Quantized


- FinFET widths are discrete ( $W = kW_{\text{unit}}$ )
  - $k$  is an integer
- Lengths are quantized because of lithography
  - Also are quantized lower metal layers, contacts...

# Ohm's Law


- Resistors

  

- Physical resistors

 

- Variable resistors

 


$$R = \rho \frac{L}{TW}$$


- In a planar process, designer controls  $W$  and  $L$

# Series and Parallel


- With two identical resistors,  $R$

 

Equivalent to doubling length

 


Equivalent to doubling width

 




# An n-Channel MOS Transistor

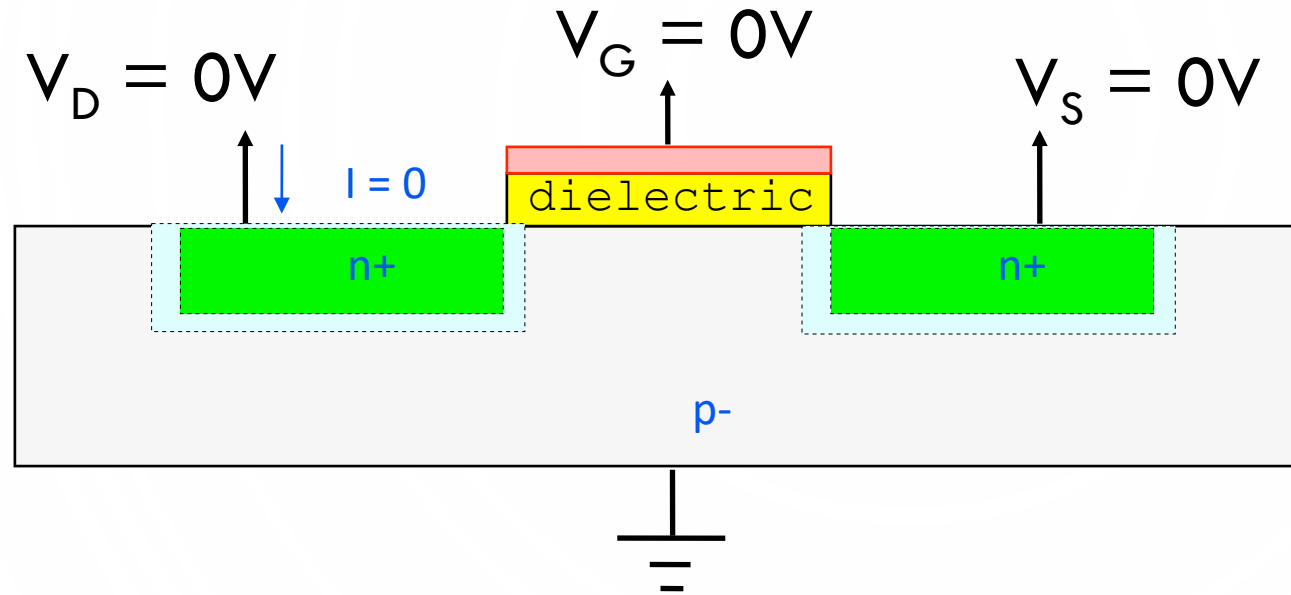


Polysilicon gate, dielectric, and substrate form a capacitor.

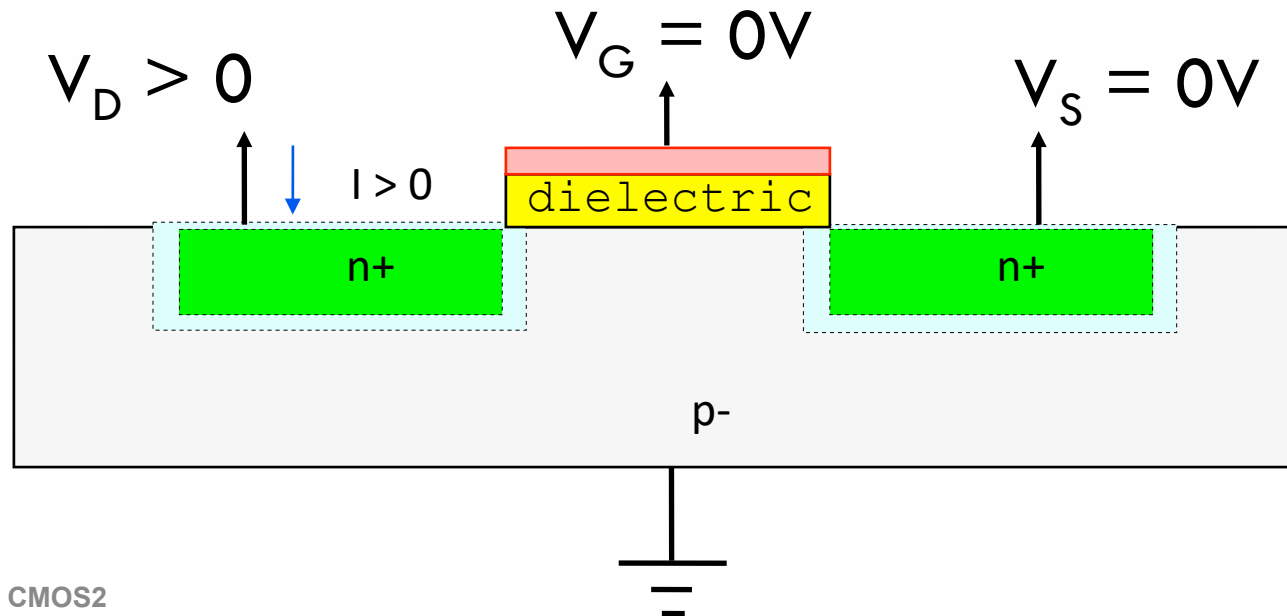When  $V_{GS} < V_{Th}$  transistor is off




$V_{DS} > 0$ , transistor leaks  
 $I_{DS} \sim nA$

# An n-Channel MOS Transistor

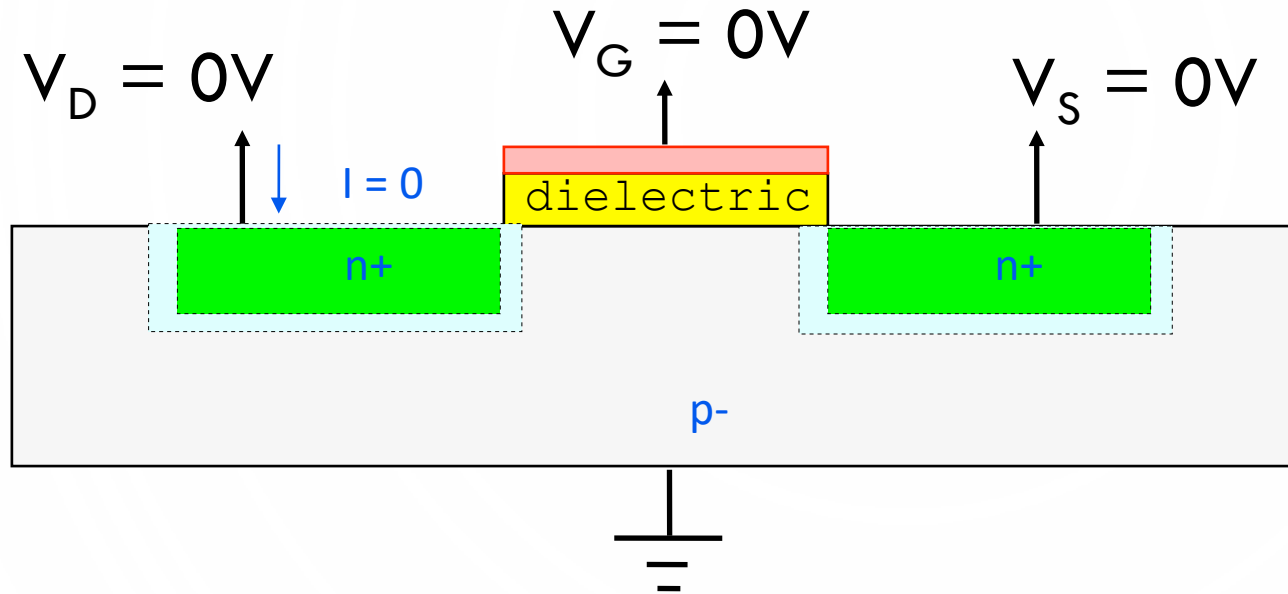

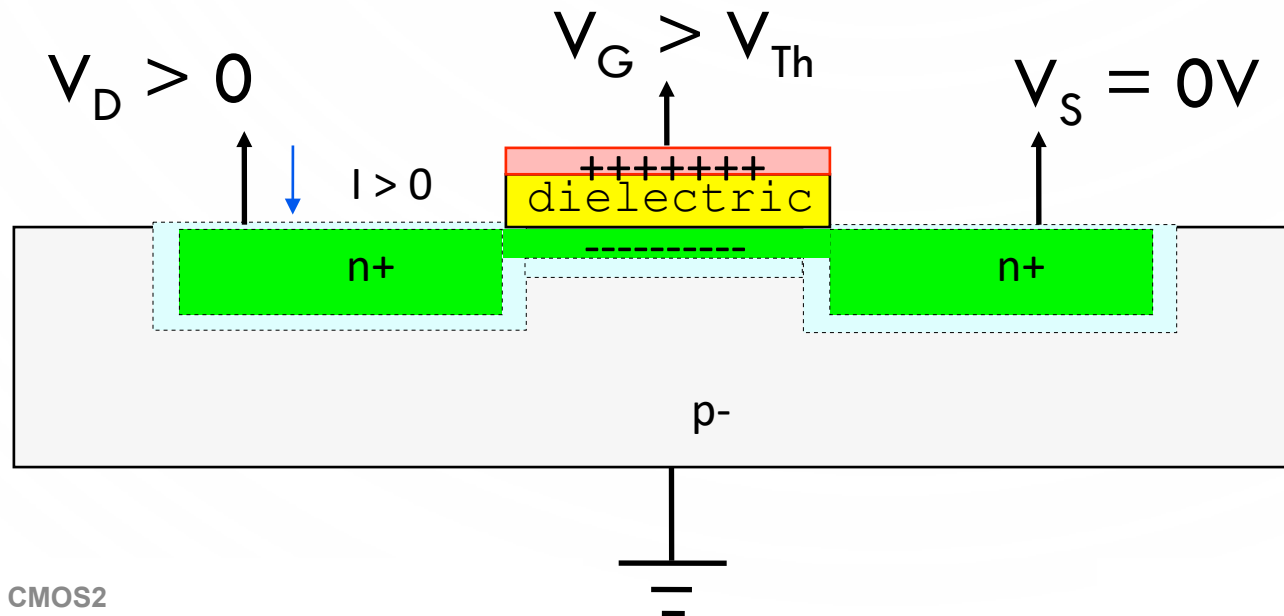When  $V_{GS} < V_{Th}$  transistor is off




$V_G > V_{Th}$ , small region near the surface turns from p-type to n-type.



nFet is on.

Current is proportional to  $V_{DS}$


# An n-Channel MOS Transistor

 

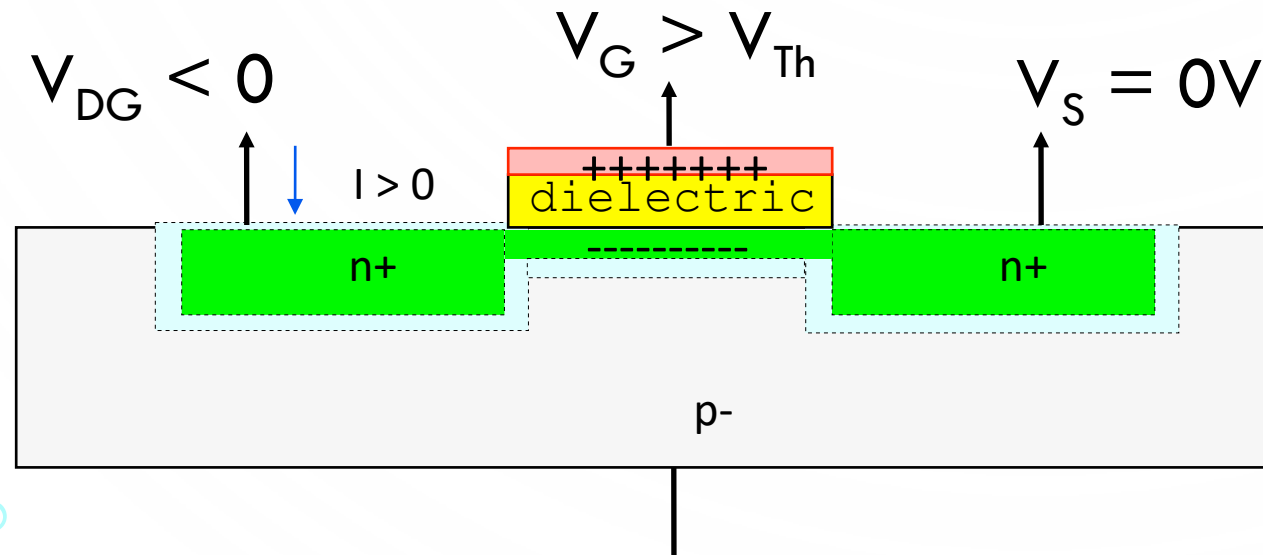 $V_{DS}$  and  $V_{GS}$  change  $I_{DS}$





 $V_{GD} < V_{Th}$  transistor saturates  
( $V_{DS} > V_{GS} - V_{Th}$ )



# MOS Transistors



- NMOS Transistor I-V characteristics

  



Nearly linear

$$I_{DS} \sim K(V_{GS} - V_{Th})$$

Old transistor

  


~7nm transistor

  


Variable resistor!
 
# Velocity Saturation

- Carrier velocity in the channel saturates



 - All submicron transistors are velocity saturated
- Other effects (drain-induced barrier lowering) cause  $I_{DS}$  to increase in saturation



# Administrivia

- Homework 5 will be posted later this week, due next week
- No lab this week
  - Lab 6 (last) after the midterm
- Midterm 1 on October 7, 7-8:30pm
  - You will be assigned a classroom
  - One double-sided page of notes allowed
  - Material includes FPGAs





# MOS Transistor as a Switch

# MOS Transistor as a Resistive Switch

MOS Transistor




A Switch!

  


- $V_{GS}$  controls the switch
  - (it also charges the channel capacitor)



# ON/OFF Switch Model of MOS Transistor

 


# A More Realistic Model

 

- It is a dimmer!


# A Logic Perspective

## NMOS Transistor

 

$Y = B$  if  $A = 1$


## PMOS Transistor

 

$Y = B$  if  $A = 0$


# AND and OR

- AND

 

$$F = AB$$
$$(F = AB + \overline{A} \cdot 0)$$

- OR

 


$$F = A+B$$
$$(F = A \cdot 1 + \overline{A}B)$$

- Keep in mind – single NMOS/PMOS transistors are imperfect switches!
  - Turns off when  $|V_{GS}| = |V_{Th}|$
 
# Peer Instruction

- Switch logic
- Which combination of inputs implements  $F = AB$ ?



	R1	R2	R3	R4
a)	1	X	X	X
b)	0	X	X	X
c)	1	0	0	0
d)	1	1	1	0
e)	1	1	1	1
f)	None of the above			

# Summary

- CMOS process is used for producing chips
  - Planar bulk process used up to 28nm node
  - finFET, FDSOI used below the 22nm node