



EECS151 : Introduction to Digital Design and ICs

Lecture 14 – Gate Delays

Bora Nikolić



Moore's Law Could Ride EUV for 10 More Years

September 30, 2021, EETimes - ASML plans to introduce new extreme ultraviolet (EUV) lithography equipment that will extend the longevity of Moore's Law for at least ten years, according to executives at the world's only supplier of the tools, which are crucial for the world's most advanced silicon.

Starting in the first half of 2023, the company plans to offer customers equipment that takes EUV numerical aperture (NA) higher to 0.55 NA from the existing 0.33 NA. The company believes that the new equipment will help chip makers reach process nodes well beyond the current threshold (2nm) for at least another 10 years, according to ASML vice president Teun van Gogh, in an interview with EETimes.



EETimes

Nikolić Fall 2021



EECS151 L13 DELAY

Review


- CMOS allows for convenient switch level abstraction
- CMOS pull-up and pull-down networks are complementary
 - Graph models for CMOS gates
- Transistor sizing affects gate performance

CMOS Sizing



Transistor Sizing

- Impact of W_p/W_n on VTC

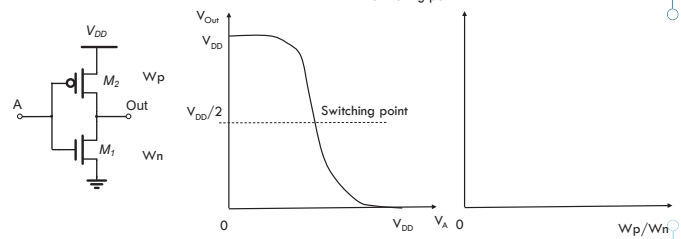


- In the past, $W_p > W_n$ (see Rabaey, 2nd ed)
- In modern processes (finFET), $W_p = W_n$
- Weak dependence on W_p/W_n

CMOS Delay



Capacitances

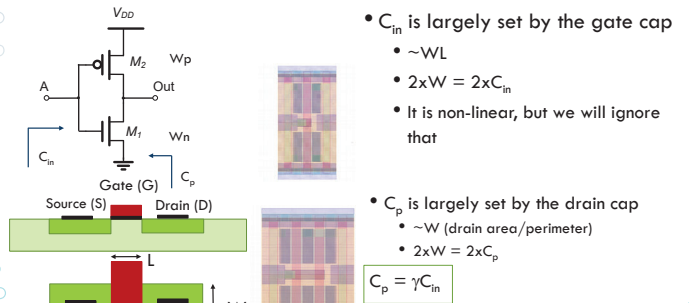


- C_{in} is largely set by the gate cap
 - $\sim WL$
 - $2xW = 2xC_{in}$
 - It is non-linear, but we will ignore that
- C_p is largely set by the drain cap
 - $\sim W$ (drain area/perimeter)
 - $2xW = 2xC_p$

$$C_p = \gamma C_{in}$$

Gate Sizing

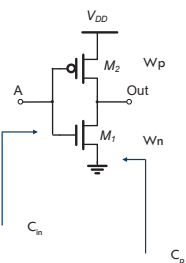
- Doubling the gate size (by doubling W_s):





- Doubles C_{in}
- Halves equivalent gate resistance
- Doubles C_p

Inverter Delay

- How to time this?


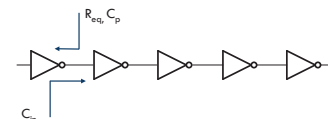


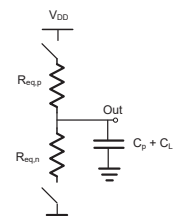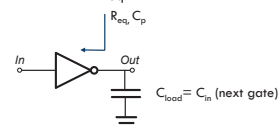- Each gate has an R_{eq} and drives C_{in} of the next gate



Inverter Delay

• High-to-low

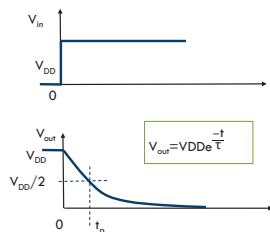
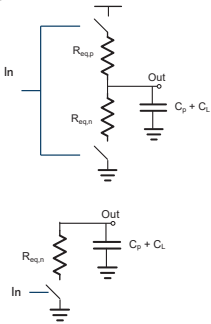


$$t_{p,HL} = (\ln 2)\tau = 0.7 R_{eq,n}(C_p + C_L)$$

$$\tau = R_{eq,n}(C_p + C_L)$$

Inverter Delay


• Low-to-high

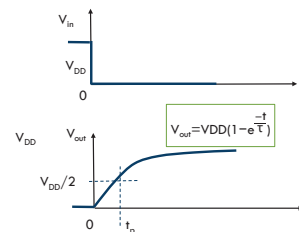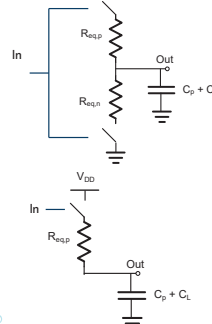

$$t_{p,LH} = (\ln 2)\tau = 0.7 R_{eq,p}(C_p + C_L)$$


Equivalent Resistances

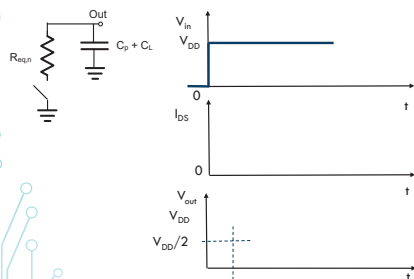- Transistor $I_{DS}-V_{DS}$ trajectory
- Averaging produces R_{eq}



Equivalent Resistances

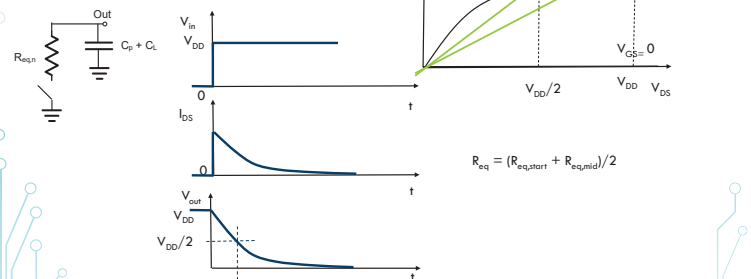- Transistor $I_{DS}-V_{DS}$ trajectory
- Averaging produces R_{eq}



$$R_{eq} = (R_{eq,start} + R_{eq,mid})/2$$


Optimal P/N Sizing

• Increasing W_p :

- Reduces R_p , increases $C_{in,p}$
- Reduces $t_{p,LH}$
- Increases $t_{p,HL}$


• Optimum

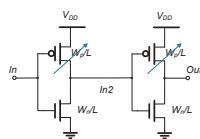- $W_p/W_n = 2$ in older technologies, with velocity saturation (like 130nm)
- $W_p/W_n = 1.6$ in technologies with strained silicon (e.g. 28nm)
- $W_p/W_n = 1$ in finFET technologies




Impact of Rise/Fall times

- Impacts the $I_{DS}-V_{DS}$ trajectory

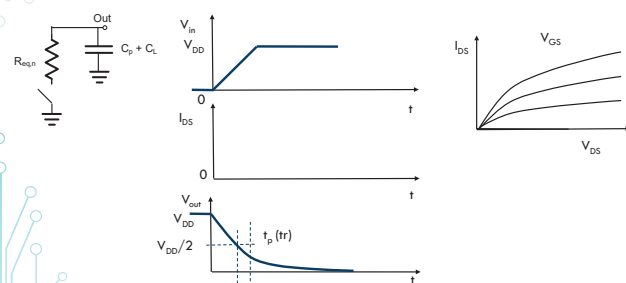


Impact of Rise/Fall times

- Impacts the $I_{DS}-V_{DS}$ trajectory

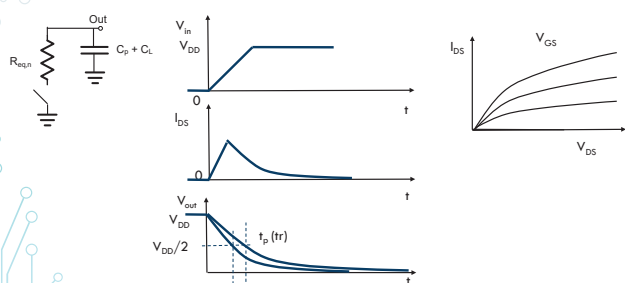



Impact of Supply Voltage

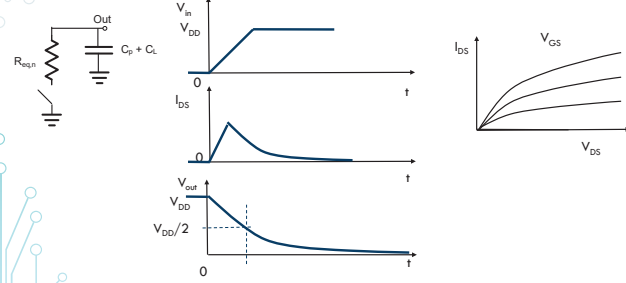- Lowering V_{DD} , slows down the circuit





Quiz: Inverter Delay

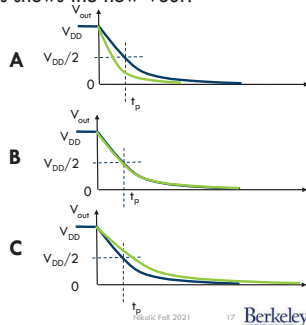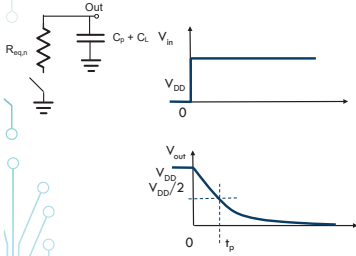- If we double the load capacitance, assuming the default V_{out} shown in blue, which of the following waveforms shows the new V_{out} ?





Sizing CMOS Gates

Sizing for equal output resistance

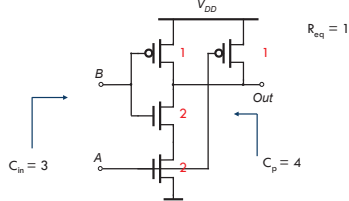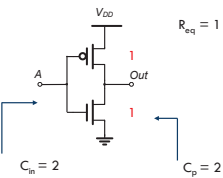


Other Gates, NOR2, NAND3

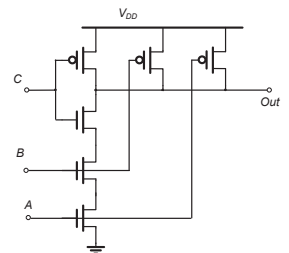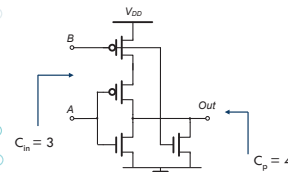

- In velocity-saturated devices I_{on} of a stack is $2/3$ (not a half) of two devices
 - So the correct upsizing factor is 1.5 (not 2)
- We will use 2, as it makes calculations easier

Stack Ordering

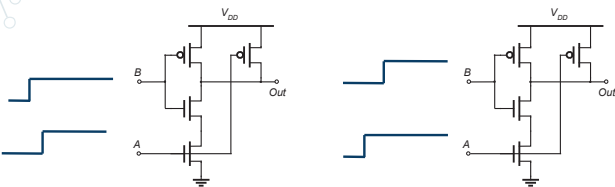

- Critical path goes on top of stack


Administrivia

- Homework 5 due this week
- Lab 6 (last) this week
- Projects start next week
- There is still time to apply for undergrad scholarships in SoC design!
- Have you thought about doing undergrad research?

Minimizing Logic Delay



Inverter RC Delay

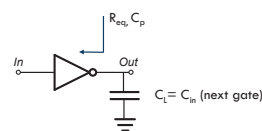

- $t_p = R_{eq}(C_p + C_L) = R_{eq}(\gamma C_{in} + C_L)$
 - $\gamma = 1$ (closer to 1.2 in recent processes)
- $t_p = R_{eq}C_{in}(1 + C_L/C_{in}) = \tau_{INV}(1 + f)$
 - Propagation delay is proportional to fanout
- Normalized Delay = $1 + f$


$$\text{Fanout} = f = C_L/C_{in}$$

$$t_p = \tau_{INV}(1 + f)$$

Generalizing to Arbitrary Gates


- Delay has two components: $d = f + p$
- f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
- g : logical effort
 - Measures relative ability of gate to deliver current
 - $g = 1$ for inverter
- h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
- p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

Inverter Delay

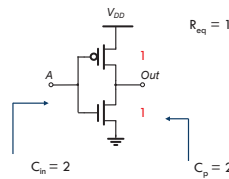


- Parasitic p is the ratio of intrinsic capacitance to an inverter
 - $p(\text{inverter}) =$
- Logical Effort g is the ratio of input capacitance to an inverter
 - $g(\text{inverter}) =$
- Electrical Effort h is the ratio of the load capacitance to the input capacitance
 - $h(\text{inverter}) =$
- Delay = $p + f = p + g * h = 1 + f$

NAND2 Gate

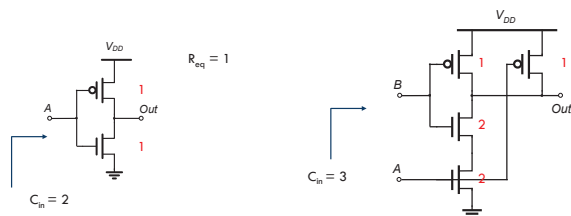


Logical Effort of NAND2 Gate

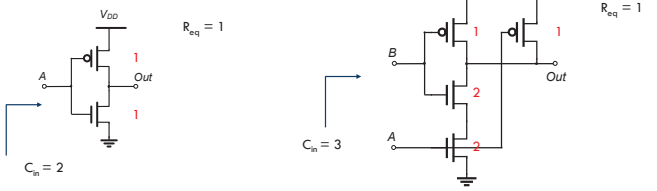


- In velocity-saturated devices I_{on} of a stack is $2/3$ (not a half) of two devices
 - So the correct upscaling factor is 1.5 (not 2)
- We will use 2, as it makes calculations easier

NOR2 Gate

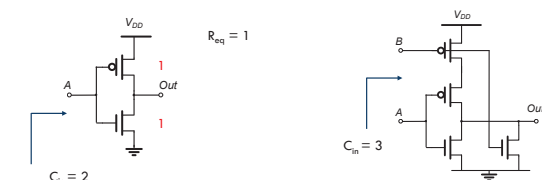


Example: Inverter Chain

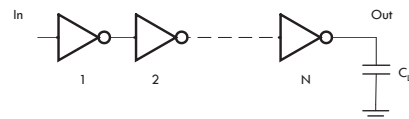

- Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$
 Total Delay: $d_{total} =$


Example: Inverter Chain

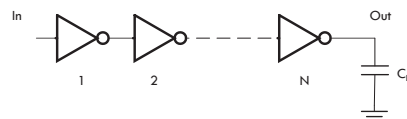

- Logical Effort: $g = 1$
 Electrical Effort: $h = 1$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = 2$
 Total Delay: $d_{total} = 2 * N$

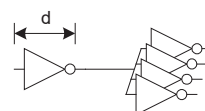Example: FO4 Inverter


- Estimate the delay of a fanout-of-4 (FO4) inverter



- Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$

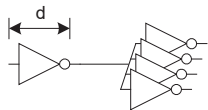Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$
 Electrical Effort: $h = 4$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = 5$

EECS151 L13 DELAY


Multi-stage Logic Networks

- Logical effort generalizes to multistage networks

Path Logical Effort $G = \prod g_i$

Path Electrical Effort $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

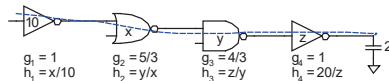Path Effort $F = \prod f_i = \prod g_i h_i$



EECS151 L13 DELAY

EECS151 L13 DELAY


EECS151 L13 DELAY

EECS151 L13 DELAY

Branching Effect

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}} \quad B = \prod b_i$$

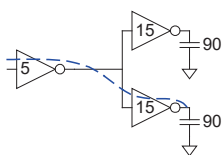$G = 1$
 $H = 90 / 5 = 18$
 $GH = 18$
 $h_1 = (15 + 15) / 5 = 6$
 $h_2 = 90 / 15 = 6$
 $B = 2$
 $F = g_1 g_2 h_1 h_2 = 36 = BGH$



EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{1/N}$$

- Thus minimum delay of N stage path is

$$D = NF^{1/N} + P$$

- This is a **key** result of logical effort


- Find fastest possible delay
- Doesn't require calculating gate sizes

Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

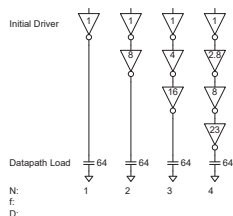

EECS151 L13 DELAY

EECS151 L13 DELAY


EECS151 L13 DELAY

Example: Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter


$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

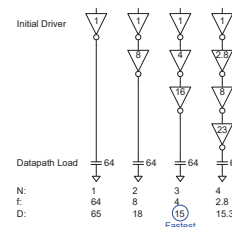

Best Stage Effort

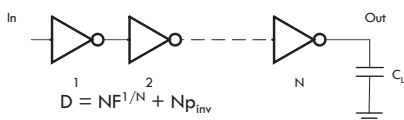- How many stages should a path use?
 - To drive given capacitance



$$D = NF^{1/N} + Np_{\text{inv}}$$

- Define best stage effort
- Neglecting parasitics ($p_{\text{inv}} = 0$), we find $\rho = e = 2.718$
- For $p_{\text{inv}} = 1$, solve numerically for $\rho = 3.59$
- Choose 4 – less stages, less energy

EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY

Logical Efforts Method

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{1/N} + P$$

$$\hat{f} = F^{1/N}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY

EECS151 L13 DELAY



Summary



- Delay is a linear function of R and C
- Delay optimization is critical to improve the frequency of the circuit.
- The dimensions of a transistor affect its capacitance and resistance.
- We use RC delay model to describe the delay of a circuit.
- Two delay components:
 - Parasitic delay (p)
 - Effort delay (F)
 - Logical effort (g): intrinsic complexity of the gate
 - Electrical effort (h): load capacitance dependent