

inst.eecs.berkeley.edu/~eecs151

EECS151 : Introduction to Digital Design and ICs


Lecture 4 – Verilog II

Bora Nikolić



The Berkeley Remix Podcast, Season 4,
Episode 2, “Berkeley Lightning: A Public
University’s Role in the Rise of Silicon Valley”

 IC chip from Hewlett Packard 34C Calculator, 1979-83. Some
of the calculator’s revolutionary features were designed by
UC Berkeley computer scientist William M. Kahan



EECS151/251A L04 VERILOG II

1 Berkeley UNIVERSITY OF CALIFORNIA

1

Review

- Electronic systems can be realized by using embedded processors, FPGAs and ASICs
- Verilog is a common design entry for synthesis
- Design flows for FPGAs and ASICs differ
 - But also have similarities
 - LA labs: ASIC
 - LB labs: FPGA

EECS151/251A L04 VERILOG II

2 Berkeley UNIVERSITY OF CALIFORNIA

2



Verilog

EECS151/251A L04 VERILOG II

3 Berkeley UNIVERSITY OF CALIFORNIA

3

Verilog Introduction

- A **module** definition describes a component in a circuit
- Two ways to describe module contents:
 - **Structural Verilog**
 - List of sub-components and how they are connected
 - Just like schematics, but using text
 - tedious to write, hard to decode
 - You get precise control over circuit details
 - May be necessary to map to special resources of the FPGA/ASIC
 - **Behavioral Verilog**
 - Describe what a component does, not how it does it
 - Synthesized into a circuit that has this behavior
 - Result is only as good as the tools
- Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).


EECS151/251A L04 VERILOG II

4 Berkeley UNIVERSITY OF CALIFORNIA

4

Logic Synthesis

- Verilog and VHDL started out as simulation languages but soon programs were written to automatically convert Verilog code into low-level circuit descriptions (netlists)
- Synthesis converts Verilog (or other HDL) descriptions to a logic mapping by using technology-specific primitives:
 - For FPGA: LUTs, flip-flops, and BRAMs
 - For ASICs: standard cells and memory macros
- In addition, synthesis algorithms optimize the implementation for delay and power

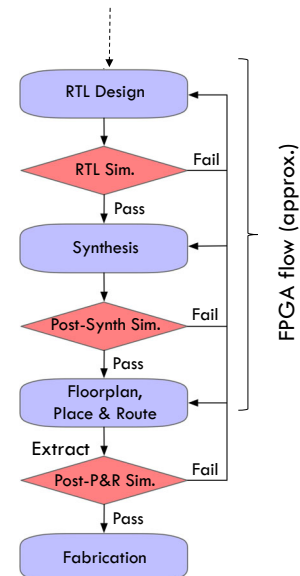

EECS151/251A L04 VERILOG II

5

Verilog Modules and Instantiation

- Modules define circuit components.
- Instantiation defines hierarchy of the design.

```

      name          port list
    module addr_cell (a, b, cin, s, cout);
      keywords      input  a, b, cin;
                   output  s, cout;
      module body
    endmodule
    module adder (A, B, S);
      addr_cell ac1 ( ... connections ... );
    endmodule
  
```

port declarations (input, output, or inout)

Instance of addr_cell

Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.
Testbench is typically the top-level module

EECS151/251A L04 VERILOG II

6



Structural Verilog

EECS151/251A L04 VERILOG II

7 Berkeley UNIVERSITY OF CALIFORNIA

7

Structural Model - XOR example

```

module xor_gate ( out, a, b );
  input  a, b;
  output out;
  wire  aBar, bBar, t1, t2;

```

Built-in gates

```


  not invA (aBar, a);
  not invB (bBar, b);
  and and1 (t1, a, bBar);
  and and2 (t2, b, aBar);
  or  or1 (out, t1, t2);

```

endmodule

Instance name

Interconnections (note output is first)

 

- Notes:


- The instantiated gates are not “executed”. They are active always.
- xor gate already exists as a built-in (so really no need to define it).
- Undeclared variables assumed to be wires. Don’t let this happen to you!

EECS151/251A L04 VERILOG II


8 Berkeley UNIVERSITY OF CALIFORNIA

8

Structural Example: 2-to1 mux

 

a) 2-input mux symbol

 

b) 2-input mux gate-level circuit diagram

```

/* 2-input multiplexer in gates */
module mux2 (in0, in1, select, out);
  input in0,in1,select;
  output out;
  wire s0,w0,w1;

  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or  (out, w0, w1);

endmodule // mux2

```

C++ style comments

Built-ins don't need instance-names

Multiple instances can share the same "main" name.

Built-ins gates can have > 2 inputs. Ex:


```
and (w0, a, b, c, d);
```

EECS151/251A L04 VERILOG II


9 Berkeley UNIVERSITY OF CALIFORNIA

9

Instantiation, Signal Array, Named ports

 

a) 4-input mux symbol

 

b) 4-input mux implemented with 2-input muxes

```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
  input in0,in1,select;
  output out;
  wire s0,w0,w1;
  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or  (out, w0, w1);

endmodule // mux2

```

```

module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  wire w0,w1;

  mux2
    m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
    m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
    m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));

endmodule // mux4

```

Signal array. Declares select[1], select[0]

Named ports. Highly recommended.

EECS151/251A L04 VERILOG II

10 Berkeley UNIVERSITY OF CALIFORNIA

10

Aside: Netlists

- **Netlist** is a description of the connectivity of an electronic circuit
 - Netlist consists of a list of components in a circuit and a list of the nodes they are connected to. A wire (net) connects two or more components
- Structural Verilog is one form of describing a netlist
- Most common netlist format is EDIF (Electronic Design Exchange Format)
 - Established in 1985, still in use

EECS151/251A L04 VERILOG II

 11  

11

Administrivia

- Lab 2 this week
 - Lab 3 starts next week
- Homework 1 due this Friday.
- Homework 2 out this Thursday.
 - More involved!

EECS151/251A L04 VERILOG II

 12  

12



Behavioral Verilog

EECS151/251A L04 VERILOG II

 13 Berkeley
 UNIVERSITY OF CALIFORNIA


13

Simple Behavioral Model

```
module foo (out, in1, in2);
  input    in1, in2;
  output   out;
```

```
    assign out = in1 & in2;
```

```
endmodule
```

“continuous assignment”

Connects out to be the logical “and” of in1 and in2.

Short-hand for explicit instantiation of bit-wise “and” gate (in this case).

The assignment continuously happens, therefore any change on the RHS is reflected in **out** immediately (except for the small delay associated with the implementation of the practical &).

Not like an assignment in C that takes place when the program counter gets to that place in the program.

EECS151/251A L04 VERILOG II

 Berkeley
 UNIVERSITY OF CALIFORNIA


14

Example - Ripple Adder


```

module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci | a&b | b&cin;

endmodule

```

 


```

module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

  wire c1, c2, c3;
  FullAdder
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );

endmodule

```

 

EECS151/251A L04 VERILOG II

15


Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
~ & ~& ~ ^ ~^ or ^~	logical negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{ }	concatenation	Concatenation
{ { } }	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

>	greater than	Relational
>=	greater than or equal to	Relational
<	less than	Relational
<=	less than or equal to	Relational
==	logical equality	Equality
!=	logical inequality	Equality
===	case equality	Equality
!==	case inequality	Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Values

Logic	Description
0	Logic '0' or false
1	Logic '1' or true
x	Don't care or unknown value
z	High impedance state

 

EECS151/251A L04 VERILOG II

16

Verilog Numbers

Constants:

- 14** ordinary decimal number
- 14** 2's complement representation
- 12'b0000_0100_0110** binary number ("_" is ignored)
- 12'h046** hexadecimal number with 12 bits

Signal Values:

By default, values are unsigned

e.g., `C[4:0] = A[3:0] + B[3:0];`

if $A = 0110$ (6) and $B = 1010$ (-6)

$C = 10000$ (not 00000)

i.e., B is zero-padded, not sign-extended

`wire signed [31:0] x;`

Declares a signed (2's complement) signal array.

EECS151/251A L04 VERILOG II



17



Verilog Assignment Types

EECS151/251A L04 VERILOG II



18

Continuous Assignment Examples

```

wire [3:0] A, X,Y,R,Z;
wire [7:0] P;
wire r, a, cout, cin;

assign R = X | (Y & ~Z);
assign r = &X;
assign R = (a == 1'b0) ? X : Y;
assign P = 8'hff;
assign P = X * Y;
assign P[7:0] = {4{X[3]}, X[3:0]};
assign {cout, R} = X + Y + cin;
assign Y = A << 2;
assign Y = {A[1], A[0], 1'b0, 1'b0};

```

use of bit-wise Boolean operators
 example reduction operator
 conditional operator
 example constants
 arithmetic operators (use with care!)
 (ex: sign-extension)
 bit field concatenation
 bit shift operator
 equivalent bit shift

EECS151/251A L04 VERILOG II



19

Non-Continuous Assignments

A bit unusual from a hardware specification point of view.
Shows off Verilog roots as a simulation language.

“always” block example:

```

module and_or_gate (out, in1, in2, in3);
  input  in1, in2, in3;
  output out;
  reg    out;
  always @(in1 or in2 or in3) begin
    out = (in1 & in2) | in3;
  end
endmodule

```

“reg” type declaration. Not really a register in this case. Just a Verilog idiosyncrasy.
 keyword
 “sensitivity” list, triggers the action in the body.
 brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | in3;`?

Why bother?

EECS151/251A L04 VERILOG II



20

Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  reg out;

  always @ (in0 in1 in2 in3 select)
    case (select)
      2'b00: out=in0;
      2'b01: out=in1;
      2'b10: out=in2;
      2'b11: out=in3;
    endcase
endmodule // mux4
```

keyword

The statement(s) corresponding to whichever constant matches "select" get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

EECS151/251A L04 VERILOG II

Berkeley UNIVERSITY OF CALIFORNIA

21

Always Blocks

Nested if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  reg out;

  always @ (in0 in1 in2 in3 select)
    if (select == 2'b00) out=in0;
    else if (select == 2'b01) out=in1;
    else if (select == 2'b10) out=in2;
    else out=in3;
endmodule // mux4
```

Nested if structure leads to "priority logic" structure, with different delays for different inputs (in3 to out delay > than in0 to out delay).

Case version treats all inputs the same.

EECS151/251A L04 VERILOG II

Berkeley UNIVERSITY OF CALIFORNIA

22

Verilog and SystemVerilog Data Types

- Verilog nets

reg – can ‘hold’ a value. Often, but not always represents registers

LHS of signals assigned within ‘**always**’ statement

wire – cannot hold a value, has to be driven. Represents connections.

LHS of signals assigned outside ‘**always**’ statements (continuous assignment)

- SystemVerilog

logic – generic data type

net – can have multiple drivers

EECS151/251A L04 VERILOG II

23




23

Review – Ripple-Carry Adder Example


```
module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

   assign r = a ^ b ^ ci;
  assign co = a&ci + a&b + b&cin;
endmodule
```



```
module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

   wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule
```



EECS151/251A L04 VERILOG II



24

Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);
  parameter N = 4;
  input [N-1:0] A;
  input [N-1:0] B;
  output [N:0] R;
  wire [N:0] C;

  genvar i;
  generate
    for (i=0; i<N; i=i+1) begin:bit
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
    end
  endgenerate

  assign C[0] = 1'b0;
  assign R[N] = C[N];
endmodule
```

Declare a parameter with default value.

Note: this is not a port. Acts like a “synthesis-time” constant.

Replace all occurrences of “4” with “N”.

variable exists only in the specification - not in the final circuit.

Keyword that denotes synthesis-time operations

For-loop creates instances (with unique names)

```
Adder adder4 ( ... );
Adder #(.N(64))
adder64 ( ... );
```

Overwrite parameter N at instantiation.

EECS151/251A L04 VERILOG II



25

More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
module gray2bin1 (bin, gray);
  parameter SIZE = 8;
  output [SIZE-1:0] bin;
  input [SIZE-1:0] gray;

  genvar i;
  generate for (i=0; i<SIZE; i=i+1)
  begin:bit
    assign bin[i] = ^gray[SIZE-1:i];
  end endgenerate
endmodule
```

variable exists only in the specification - not in the final circuit.

Keywords that denotes synthesis-time operations

For-loop creates instances of assignments

Loop must have constant bounds

generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

EECS151/251A L04 VERILOG II




26

Defining Processor ALU in 5 mins

- Modularity is essential to the success of large designs
- High-level primitives enable direct synthesis of behavioral descriptions (functions such as additions, subtractions, shifts (<< and >>), etc.

Example: A 32-bit ALU

 

Function Table

F2	F1	F0	Function
0	0	0	$A + B$
0	0	1	$A + 1$
0	1	0	$A - B$
0	1	1	$A - 1$
1	0	X	$A * B$

EECS151/251A L04 VERILOG II

27



27

Module Definitions

2-to-1 MUX

```

module mux32two(i0,i1,sel,out);
input [31:0] i0,i1;
input sel;
output [31:0] out;

assign out = sel ? i1 : i0;

endmodule

```

32-bit Adder

```

module add32(i0,i1,sum);
input [31:0] i0,i1;
output [31:0] sum;

assign sum = i0 + i1;

endmodule

```

32-bit Subtractor

```

module sub32(i0,i1,diff);
input [31:0] i0,i1;
output [31:0] diff;

assign diff = i0 - i1;

endmodule

```

3-to-1 MUX

```

module mux32three(i0,i1,i2,sel,out);
input [31:0] i0,i1,i2;
input [1:0] sel;
output [31:0] out;
reg [31:0] out;

always @ (i0 or i1 or i2 or sel)
begin
case (sel)
2'b00: out = i0;
2'b01: out = i1;
2'b10: out = i2;
default: out = 32'bx;
endcase
end
endmodule

```

16-bit Multiplier

```

module mul16(i0,i1,prod);
input [15:0] i0,i1;
output [31:0] prod;

// this is a magnitude multiplier
// signed arithmetic later
assign prod = i0 * i1;

endmodule

```

EECS151/251A L04 VERILOG II



28


Top-Level ALU Declaration

- Given submodules:

```
module mux32two(i0,i1,sel,out);
module mux32three(i0,i1,i2,sel,out);
module add32(i0,i1,sum);
module sub32(i0,i1,diff);
module mul16(i0,i1,prod);
```

- Declaration of the ALU Module:

```
module alu(a, b, f, r);
input [31:0] a, b;
input [2:0] f;
output [31:0] r;
wire [31:0] addmux_out, submux_out;
wire [31:0] add_out, sub_out, mul_out;
mux32two addmux(.io(b), .i1(32'd1), .sel(f[0]), .out(addmux_out));
mux32two submux(.io(b), .i1(32'd1), .sel(f[0]), .out(submux_out));
add32 our_adder(.i0(a), .i1(addmux_out), .sum(add_out));
sub32 our_subtractor(.i0(a), .i1(submux_out), .diff(sub_out));
mul16 our_multiplier(.i0(a[15:0]), .i1(b[15:0]), .prod(mul_out));
mux32three output_mux(.i0(add_out), .i1(sub_out), .i2(mul_out), .sel(f[2:1]), .out(r));
endmodule
```

 

intermediate output nodes

module names (unique) instance names corresponding wires/regs in module alu

EECS151/251A L04 VERILOG II


Berkeley UNIVERSITY OF CALIFORNIA

29

Top-Level ALU Declaration, take 2

- No Hierarchy:
- Declaration of the ALU Module:
 
```
module alu(a, b, f, r);
input [31:0] a, b;
input [2:0] f;
output [31:0] r;
always @ (a or b or f)
case (f)
3'b000: r = a + b;
3'b001: r = a + 1'b1;
3'b010: r = a - b;
3'b011: r = a - 1'b1;
3'b100: r = a * b;
default: r = 32'bx;
endcase
endmodule
```



Will this synthesize into 2 adders and 2 subtractors or 1 of each?

EECS151/251A L04 VERILOG II

Berkeley UNIVERSITY OF CALIFORNIA

30



Sequential Logic, Take 2

EECS151/251A L04 VERILOG II

31

Berkeley
UNIVERSITY OF CALIFORNIA

31


Latches and Flip-Flops

- Flip-flop is edge-triggered, latch is level-sensitive

- D Flip-flop


- Rising edge

Signifies 'edge triggered'

 


- D Latch

- Transparent
HIGH

 Level sensitive if there
is no 'edge'

- Transparent
LOW

 

EECS151/251A L04 VERILOG II


32

Berkeley
UNIVERSITY OF CALIFORNIA


32

Timing



• Combinational logic timing

 

 A is arriving late
(is in the critical path)



  B is arriving late
(is in the critical path)



HL and LH transition differ

t_{A-Out} and t_{B-Out} differ

In CMOS, propagation delay depends on:

- Gate type, size (output resistance)
- Capacitive loading
- Input slope

EECS151/251A L04 VERILOG II

33

Berkeley





33

Timing


• Flip-flop timing

(latch timing will be covered later)

  

• Setup and hold times

 - Data cannot change in the interval of setup time **before** the clock edge to hold time **after** the clock edge



EECS151/251A L04 VERILOG II

34


Berkeley




34

Register

- 4-bit register

 

- Accumulator

 

EECS151/251A L04 VERILOG II

35 Berkeley UNIVERSITY OF CALIFORNIA

35

Summary

- Verilog is the most-commonly used HDL
- We have seen combinatorial constructs
 - Assign statement
 - Always blocks
 - Sequential – next week
- Practice is the best way to learn a new language...

EECS151/251A L04 VERILOG II

36 Berkeley UNIVERSITY OF CALIFORNIA

36